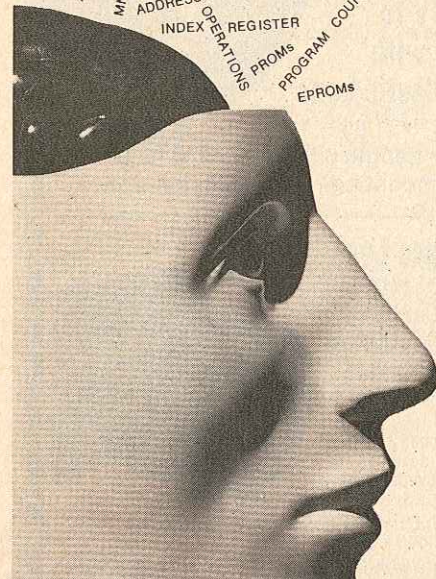


THE BOOK YOU'VE WAITED FOR IS HERE!

HEXADECIMAL
MEMORY
BITS
ROMS
MNEMONICS
ADDRESSING MODE
INDEX REGISTER
BOOLEAN LOGIC OPERATIONS
PROGRAM COUNTER
PROMS
EPROMs



UNDERSTANDING MICRO COMPUTERS AND SMALL COMPUTER SYSTEMS

Here, at last, is a profusely illustrated, easy-reading, "must" book explaining fundamental concepts behind operation of almost all microcomputers... in simple English... giving you that extra knowledge to read and understand computer magazines and manufacturer's literature... and feel "at home" around computers. Things like:

- How a CPU is organized; how it follows sequences of orders to solve problems
- Illustrates basic instructions from almost every microcomputer
- Discusses common memory addressing modes
- Illustrates typical uses
- What to know to tell a computer what to do when using machine language programming
- Use of flow charts; program worksheets; hand assembly of source codes into object codes; memory maps; purpose of Editor, Assembler, Monitor.


only \$995. Order your copy today!

- How a computer communicates
- Commonly used I/O devices and operational concepts
- Practical aspects of selecting a small computer system
- Plus, hundreds of other practical facts and information! If you're curious about small computers, you must own this 300 page no-nonsense easy-reading text. Includes easy-to-use glossary of key microcomputer-oriented words.

UNDERSTANDING MICROCOMPUTERS. The name says it all! Only \$9.95 ppd. Order your copy today!

SCELBI COMPUTER CONSULTING INC.
P.O. Box 133 — PP STN, Dept. PE
Milford, CT 06460

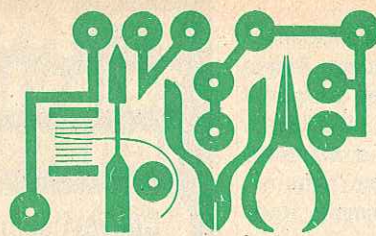Price shown for North American customers. Master Charge, Postal and Bank Money Orders preferred. Personal checks delay shipping up to 4 weeks. Pricing, specifications, availability subject to change without notice. SCELBI Books are available in many fine Computer Stores.



Experimenter's Corner

By Forrest M. Mims

READ/WRITE MEMORIES (RAM's), PART 1

LAST MONTH, we built a read-only memory (ROM) with some diodes and a BCD-to-decimal decoder. Now, we're going to experiment with the 7489 IC, a factory-produced read/write memory that can store sixteen 4-bit words.

As you know, ROM's store information without the need for electrical power and are called *non-volatile* memories. Most RAM's, on the other hand, are *volatile* memories; turn off the power and they forget whatever information is stored in them. You've probably seen read/write memories labeled RAM's and R/WM's. RAM, random access memory, is a fancy way of saying that any bit or word stored in the memory can be addressed as fast as any other. This contrasts with a *serial* memory like magnetic tape where a time-consuming search may be required to find a particular bit or word.

Since both ROM's and RAM's are random access memories, R/WM is a better label for the read/write memory than RAM. But "RAM" is pronounceable and R/WM isn't, so most people use RAM.

The 7489 RAM. The storage capacity of the 7489 is a far cry from that of the 4k (4,096 8-bit bytes) RAM's used by hobby computer enthusiasts, but the 7489 does have some interesting applications. It will help you understand some basic microprocessor terminology and operations.

Fig. 1. The 7489 RAM pin outline.

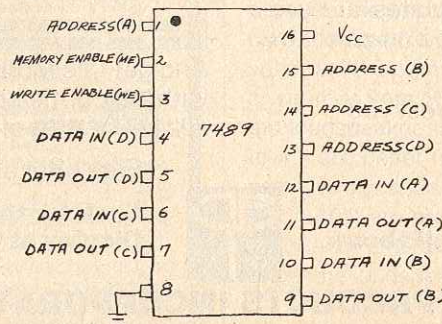


Figure 1 shows the pin diagram for the 7489. Here's a table that organizes the pins according to function:

Function	Pins			
	D	C	B	A
Address lines	13	14	15	1
Data in	4	6	10	12
Data out	5	7	9	11

The 7489 also has a couple of *enable* inputs. The Memory Enable (ME) input, pin 2, is connected to ground (logic 0) during read and write operations. The Write Enable (WE) input, pin 3, must be at logic 0 when data is written into the RAM. Data can be read from the RAM when WE is at logic 1.

The 7489 has 16 storage slots designated by the addresses 0000-1111. Thanks to a built-in address decoder, writing a word into a memory slot is a simple matter of applying the appropriate BCD number to the address lines, placing both ME and WE at logic 0, and presenting the bits to be stored at the data input lines.

Reading a word from the RAM is even simpler. First, the word's storage slot address bits are applied to the address lines. Then ME is placed at logic 0 and WE at logic 1. The *complement* of the word in the selected address will then appear at the output.

Complementing a word means changing its 0's to 1's and its 1's to 0's. Thus, the complement of 1010 is 0101. This means you have to complement a word you want to store before writing it into the memory if you want it to appear in uncomplemented form at the output. In other words, if you want to retrieve 1100, store 0011 instead.

There are two points to keep in mind in using a 7489. First, it is a volatile memory, so you must keep power applied as long as you want to save the data stored in it. It's also a *non-destructive* memory. That is, the selected word is not lost when it's read out; it stays in the memory until replaced by a new word.

RAM Demonstration Circuit. You can learn a lot about RAM's by plugging the 7489 into a solderless breadboard along with some LED's to indicate the output data and jumper wires to select addresses and apply input data. Use the arrangement shown in Fig. 2. Take a few minutes to label each jumper with a marked square of masking tape. This will save lots of time later. Connect jumpers you want to be at logic 0 to ground and those at logic 1 to +5 volts. Try loading each storage slot with its binary address for practice.

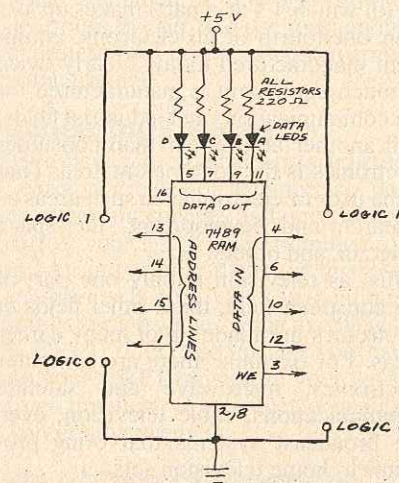


Fig. 2. A RAM demonstration circuit.

In this circuit a glowing LED indicates logic 0 and a dark LED, logic 1. You can automatically invert words stored in the memory by mentally assuming that a glowing LED signifies a logic 1. This means you don't have to load the complement of a word you want to save.

Automated RAM Demonstrator. A much better way to learn about RAM's as well as some microprocessor basics is to connect a binary counter to the address inputs of the 7489. Figure 3 is a block diagram that shows how everything goes together.

Here's how the circuit works using microprocessor terminology. Clock pulses enter the counter, and the 4-bit BCD count is applied to the address inputs of the RAM. The counter acts like a *pointer* as it sequentially selects first one address, then the next, and so forth.

In the READ mode (WE = 1; ME = 0), the data output LED's flash each word in succession as the pointer cycles through the memory. In the WRITE mode (WE and ME = 0), the LED's are extinguished, and the data on the input lines is written into the RAM. This means, of course, that the input data has to be



You can build a better organ than you can buy!

A magnificent Schober Electronic Organ

What a marvelous way to put your special talents to work! With our Schober Electronic Organ Kits and your skill, you can build yourself some very special satisfaction, and a lifetime of great music!

Schober Organs are literally far superior to comparably-priced "ready-made" units. You could actually pay twice as much and get no better organ...and miss the fun of assembling it yourself. A PC board at a time, component by component, you'll assemble your own "king of instruments." And when you're done, you'll wish there was more to do. And there is! For then, Schober will help you learn to play, even if you've never played a note before!

Schober Organ Kits range from \$650 to \$2850, and you can purchase in sections to spread costs out...or have two-year time payments. Combine the incomparable quality of Schober components with your talent...and produce a far better organ than you can buy!

Thousands of others have, ever since 1955. You can have all the details, without cost or obligation. Just send the coupon for the fascinating Schober color catalog (or enclose \$1 for a record that lets you hear as well as see Schober quality.) Why not clip it right now, before you forget?

The Schober Organ Corp., Dept. PE-74
43 West 61st Street, New York, N.Y. 10023

Please send me Schober Organ Catalog.
 Enclosed please find \$1.00 for 12-inch L.P. record of Schober Organ music.

NAME _____
ADDRESS _____
CITY _____ STATE _____ ZIP _____

CIRCLE NO. 55 ON FREE INFORMATION CARD

The leading magazine in the personal computer field



BYTE is the magazine for the creative home computer experimenter. BYTE tells you everything you want to know about personal computers, including how to construct and program your own system.

Home computers are now practical and affordable. Low cost peripherals have resulted in more hardware and software, more applications than you could imagine. BYTE brings it all to you. Every issue filled with stimulating, timely articles by professionals, computer scientists and serious amateurs.

Fill in the coupon today. Read your first copy of BYTE; if it's everything you expected, honor our invoice. If it isn't, just write "CANCEL" across the invoice and mail back. You won't be billed, and the copy is yours. Allow 6 to 8 weeks for processing.

© Byte Publications, Inc. 1977

BYTE Subscription Dept. 07F
P.O. Box 361 Arlington, Mass. 02174 U.S.A.


Please enter my subscription for:

- One year U.S. \$12 (12 issues) Two years U.S. \$22 Three years U.S. \$32
- Canada or Mexico \$17.50 Europe (Air Delivered) \$25
- Surface delivery to all other countries except Europe, Canada or Mexico \$25 (Air delivery available on request) Please remit in U.S. funds.
- Check enclosed (Bonus: one extra issue) Bill me Bill Bank Americard
- Bill Master Charge

Card Number _____ Expiration date _____
Signature _____ Name (please print) _____
Address _____
City _____ State/Country _____ Code _____

CIRCLE NO. 6 ON FREE INFORMATION CARD

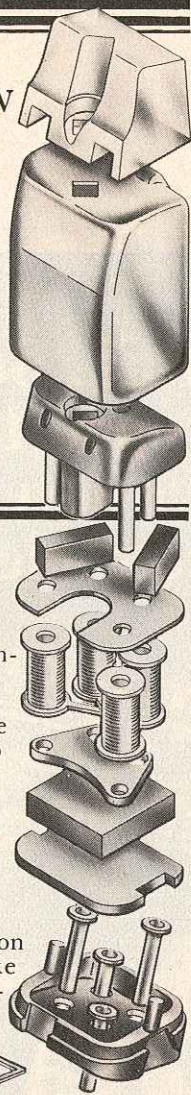The Best Way To Show You What You'll Get Out Of An Empire Phono Cartridge Is To Show You What Goes Into One.



At Empire we make a complete line of phono cartridges. Each one has slightly different performance characteristics which allow you to choose the cartridge most compatible to your turntable.

There are, however, certain advantages, provided by Empire's unique design, that apply to all our cartridges.

One is less wear on your records. Unlike other magnetic cartridges, Empire's moving iron design allows the diamond stylus to float free of its magnets and coils, imposing much less weight on your record's surface and insuring longer record life.

Another advantage is the better channel separation you get with Empire cartridges. We use a small, hollow iron armature which allows for a tighter fit in its positioning among the poles. So, even the most minute movement is accurately reproduced to give you the space and depth of the original recording.

Finally, Empire uses 4 coils, 4 poles, and 3 magnets (more than any other cartridge) for better balance and hum rejection.

The end result is great listening. Audition one for yourself or write for our free brochure, "How To Get The Most Out Of Your Records". After you compare our performance specifications we think you'll agree that, for the money, you can't do better than Empire.

Empire Scientific Corp.
Garden City, New York 11530

EMPIRE
Already your system sounds better.

changed between clock pulses or the pointer will load all the storage slots in the RAM with the same word.

The complete circuit for the automated demonstrator is shown in Fig. 4. It

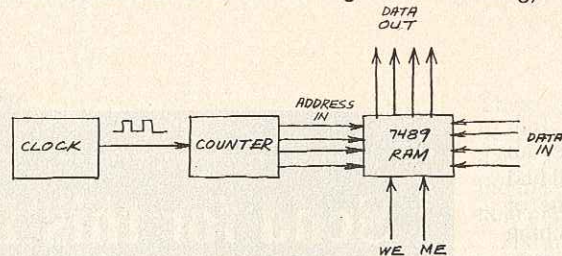


Fig. 3. Block diagram of automated RAM demonstrator.

makes a great fully programmable light flasher so you'll want to build it just to watch it flash.

The role of the clock is filled by a 555 timer, and a 7490 decade counter serves as the address pointer. The 7490 is a BCD counter so it recycles to 0000 after 1001 (decimal 9). This means it can address only ten of the 7489's storage slots. To address all 16 memory slots, you can use a full 4-bit counter (0000-1111) such as a 7493, 74161, or 74191. I've specified the 7490 because its operation has been covered previously here. It's also very inexpensive and readily available.

Notice the various switches and LED's in the circuit. Closing S1 allows clock pulses to reach the counter. The CLOCK LED provides a handy visual indication that the clock is running and, below about 20 Hz, a rough idea of its rate.

The pointer LED indicates when the counter has recycled back to 0000. It's on when the count is 0000 through 0111 and off when the count is 1000 and 1001. This means the counter is pointing to address 0000 in the RAM the moment the pointer LED flashes on after being off for two pulses.

Toggle switches S2 through S5 let

you form words to store in the RAM by simply flipping switches (much like a microcomputer designed for front-panel machine language program and data loading). Closing S6 loads the word


formed by the data input switches into the address slot selected by the pointer.

Of course, you don't have to use switches if you build the circuit on a solderless breadboard. Just remove and reinsert jumpers labeled with masking tape to simulate the on-off action of switches. Real switches, however, make the circuit much easier to use, particularly if you mount them on a small panel and identify them with labels.

Programming the automated RAM demonstrator is a straightforward procedure of loading words into the RAM one at a time until ten address slots are filled. Switch S1 is turned off to disable the clock while a word is being loaded and turned on for one clock pulse to advance the pointer to the next address. It's easy when you slow the clock rate to about a pulse per second (by setting R1 for maximum resistance) and keep an eye on the clock LED.


To Be Continued. Next month we'll discuss programming procedures in more detail. We'll also expand the demonstrator by adding an automatic pseudo-random data loader, and cover some ways to address all sixteen data storage slots in the 7489. ◊

Fig. 4. Automated Ram demonstrator.

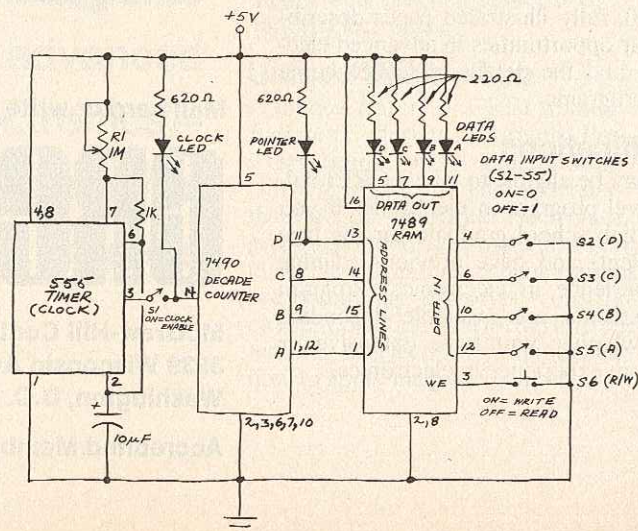

What's Happening...

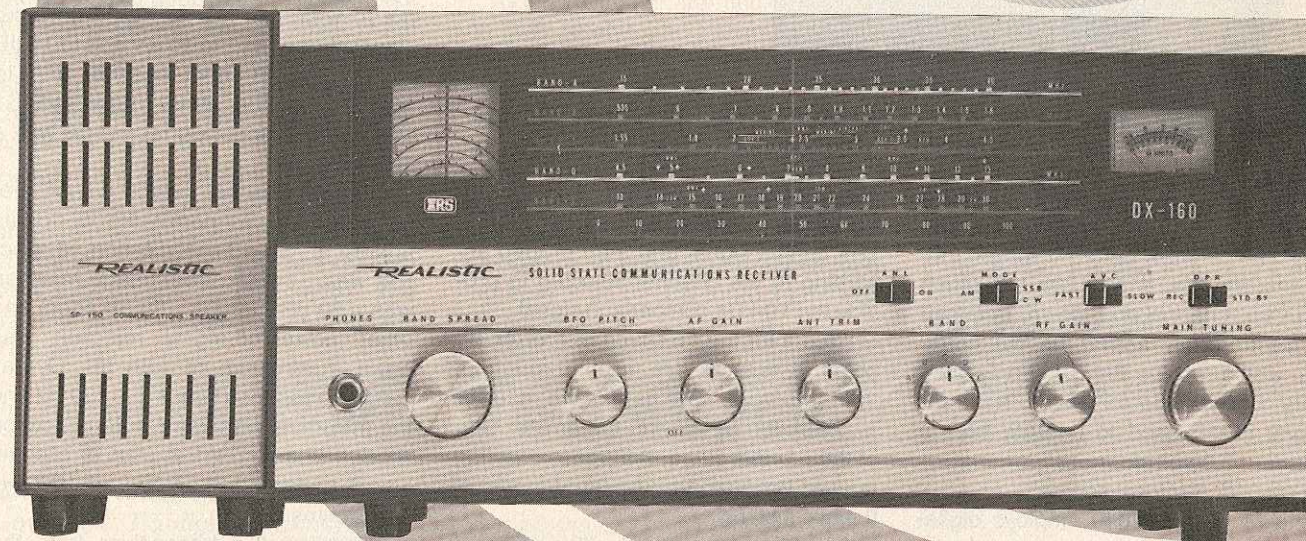in Helsinki,
Nairobi, Tel Aviv,
Capetown, Moscow, Saigon
or a thousand other places?



Find out with the Realistic® DX-160

A pro-feature receiver for HAM/SWL CB/SSB/AM listening.

The modern world really is a "global village" when you own the versatile DX-160. Five bands covering 130 kHz to 30 MHz let you monitor transmissions from all over the world. Listen in on all 120 CB channels, AM and single-sideband. Hear world news as it develops by tuning in local programs in faraway cities. Receive code as well as voice transmissions. You'll be amazed at the DX-power you can get even on the standard AM broadcast band! Eleven controls and switches really let you "pull out" those distant stations. Main tuning control plus precision bandspread tuning calibrated for the Amateur bands. Switchable noise limiter. Multiple controls for CW and SSB reception. A built-in receive/standby switch lets you use the DX-160 with a Ham transmitter. High-performance FET's in all critical stages. With matching speaker, headphone jack, AC and DC power cords. The DX-160 — what a way to travel! Only 169.95*.



FREE! New '78 Catalog

Come in for your copy and see what's really new in electronics. 164 pages — 100 in full color. 2000 exclusive items.

Ham Radio Starter Set

Bought Separately 232.4

Special Price* 21.00



Prepares you to join the action as a Ham operator. Learn theory and code technique with instruction cassette tape, programmed textbook, practice oscillator, and high-speed brass hand key.

SOLD ONLY WHERE YOU SEE THIS SIGN:

Radio Shack®

A TANDY COMPANY • FORT WORTH, TX 76102 • 6000 LOCATIONS IN 9 COUNTRIES

*Price may vary at individual stores and dealers. Prices and products may vary in Canada.