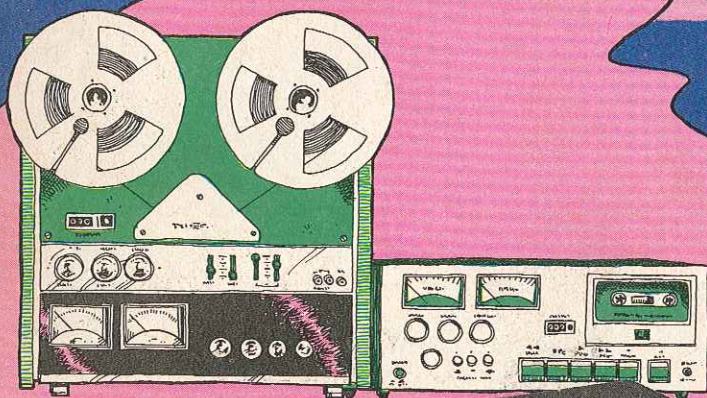



PE RATES THE NEW CASSETTE TAPES

Popular Electronics®

WORLD'S LARGEST-SELLING ELECTRONICS MAGAZINE NOVEMBER 1977/\$1.25



HOW TO BUILD AN AUDIO COMPANDER

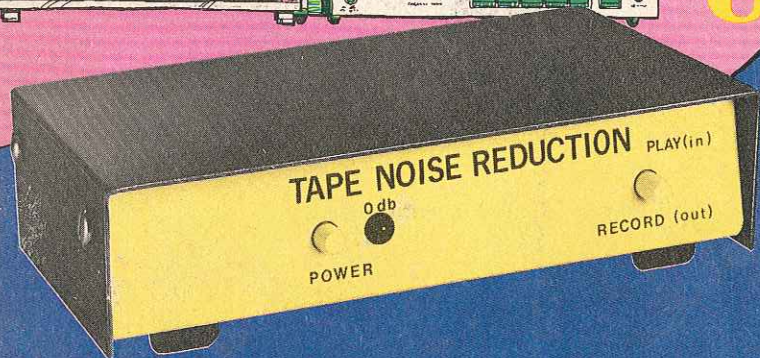

- Improves dynamic range of tapes
- Reduces noise level

How To Dress Up Your Projects

- Tips on making projects attractive

A Field-Disturbance Sensor for Security Systems

Add Voltage Regulation to Color Enlargers

Piracy On The Airwaves

TESTED THIS ISSUE: Dual 1245 Automatic Turntable

- Burwen DNF 1201A Noise Reduction

shi DA-A15 Audio

A-P10 Preamp

49 AM/SSB CB Mobile

Transceiver ● North Star Floppy Disk



Popular Electronics

6XG H9N NO
11
625ED 0142 0608098 741D DEC 79

LONDON
30 BISCAY RD
F C CHOD

14024-14278
14024-14278
14024-14278

Popular Electronics Reprint series

Many important articles covering a variety of interests in the broad field of electronics are published in POPULAR ELECTRONICS. Reprints of selected articles and test reports are now available in the event that you missed some you would like to have for reference or study purposes—or for projects you wish to build. Reprints in this series are only \$1 each (*75¢ for those marked with an asterisk.) Minimum order is \$2.

SPECIAL ARTICLES

AUDIO

1. How The New FTC Hi-Fi Rules Affect You
2. How To Evaluate Tape Recording Specs
3. A New Standard For FM Tuner Measurements

COMPUTER

7. How To Select A Microcomputer
8. Ins & Outs Of Computers For Beginners
- COSMAC "ELF" SERIES (Reprint #'s 4, 5, 6, & 17)
4. Low Cost Experimenter's Microcomputer
5. Experimenter's Microcomputer/With Hardware Improvements & More Programming Details
6. Microcomputer/How To Expand Memory, Plus More Programs
17. Build The Pixie Graphic Display

CB RADIO

9. CB Specifications Made Easy
10. How To Choose CB Base Station Antennas

OTHER

14. How To Design Your Own Power Supplies
15. The Care & Feeding Of NiCd Batteries
16. Build A Gas & Fume Detector
- LEARNING ELECTRONIC THEORY WITH CALCULATORS SERIES (Reprint #'s 11, 12, & 13)
11. Basic Equations and OHM's Law
12. Reactance, Time Constants And AC Calculations
13. RC Coupling, Basic Amplifier Calculations, and RLC Relationship

TEST REPORTS

AUDIO

18. ADC Accutrac 4000 Record Player
- 19.*Empire Model 698 Manual Turntable
20. Kenwood Model 600 Integrated Stereo Amplifier
- 21.*MXR Stereo Graphic Equalizer

*REPRINTS MARKED WITH ASTERISK 75¢; ALL OTHERS \$1.00. MINIMUM ORDER \$2.00.

Popular Electronics Information Center, Consumer Products Division, 595 Broadway, New York, N.Y. 10012.

Please send the reprints listed below:
75¢ Each

Reprint #	Quan.	Reprint #	Quan.

\$1.00 Each

Reprint #	Quan.	Reprint #	Quan.

Print Name _____

Address _____

City _____

State _____

Zip _____

†Residents of CA, CO, FL, IL, MI, MO, NY STATE, DC and TX add applicable sales tax. Outside U.S.A. add \$1.00 per order.


NUMBER OF REPRINTS ORDERED:

@ 75¢ _____ @ \$1.00 _____

TOTAL ENCLOSED \$ _____†

(MINIMUM ORDER \$2.00)

PE-117

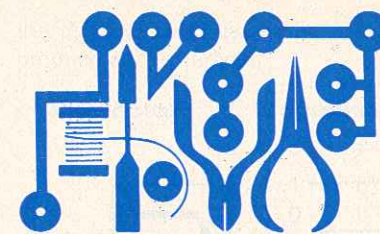

Experimenter's Corner

By Forrest M. Mims

PROGRAMMABLE READ-ONLY MEMORIES

SEMICONDUCTOR memories are among the most important electronic circuits. They are found in almost all digital devices, ranging from pocket calculators to computers. Besides their obvious application in the storage of information, these memories can be used in the synthesis of unusual waveforms, music, and even human speech.

There are two basic types of semiconductor memories. *Read-only memories* (ROM's) are those from which data is normally only retrieved. *Read/write memories* (R/WM's) or *Random-access memories* (RAM's) are those into which data can be loaded or from which information can be retrieved, each with equal facility. ROM's are factory programmed with fixed data which cannot be changed.

Some ROM's, called PROM's, can be permanently programmed by the user. Others, called EPROM's, can be programmed by the user and then erased by exposure to ultraviolet light. After

erasure, EPROM's can be reprogrammed. RAM's can be loaded with information, read, or reloaded electronically, depending on the logic states of the memory cell's READ and WRITE control lines.

Both types of semiconductor memories store information in the form of binary digits, abbreviated as bits, which have two possible states—logic 0 or logic 1. The stored data can be arranged as hundreds or even thousands of bits or combinations of bits called words. Words comprising four bits (*nibbles*) or eight bits (*bytes*) are the most common, but many other word lengths are also used.

Programmable Diode ROM's. An excellent way for the novice to learn more about ROM's is to assemble a programmable ROM or PROM that uses diode memory elements. A PROM of this type consists of a grid or array of input and output wires called *lines*. A logic 1 is loaded into the ROM by bridging the intersection of an input and output line with a diode. The absence of a diode at an intersection yields a logic 0.

You can use a simple diode PROM to simulate logic gates and combinational logic networks. The first step in designing a PROM for this purpose is to write

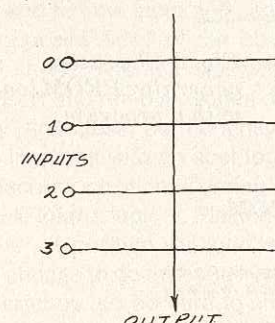


Fig. 1. PROM grid that can be used to simulate a NAND gate.

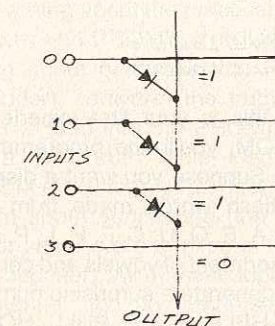


Fig. 2. 4X1 PROM programmed for 2-input NAND gate.

NOVEMBER 1977

the truth table for the gate you want to simulate. The truth table for a two-input NAND gate, for example, is

	Inputs		Output
	A	B	
0	0	0	1
1	0	1	1
2	1	0	1
3	1	1	0

This truth table has four possible input combinations and only one output for each set of inputs. Therefore, our PROM will be a 4 by 1 grid of lines as shown in Fig. 1. The truth table is loaded (programmed) into the PROM by placing a

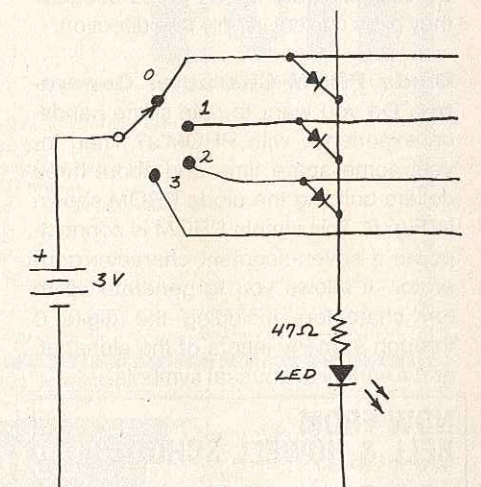


Fig. 3. Circuit to demonstrate the PROM in Fig. 2.

diode at the intersection of the output line and the line for each input, which results in a logic-1 output. The programmed array is shown in Figure 2. Figure 3 shows how to demonstrate the operation of the PROM with the help of a

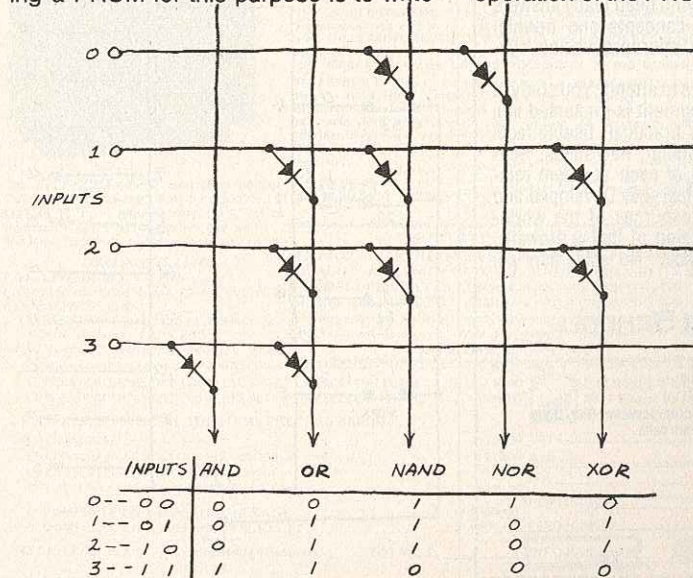


Fig. 4. Multiple function diode PROM.

battery, a LED, and a four-position switch.

Of course, our simple PROM version of the NAND gate is a trivial example of a read-only memory application. This is particularly true because the diodes aren't even necessary! Logic 1's can be represented simply by connecting the appropriate input lines to the output line. However, diodes are essential when the PROM becomes more sophisticated. For example, Fig. 4 shows a diode PROM that simulates the AND, OR, NAND, NOR, and EXCLUSIVE OR gates. Mass confusion would result without diodes because electrical current would thread its way through the wrong sections of the PROM via *sneak paths*. Diodes eliminate sneak paths because they pass current in only one direction.

Diode PROM Character Generator. Do you want to gain some hands-on experience with PROM's? Then invest some spare time and about three dollars building the diode PROM shown in Fig. 5. This simple PROM is connected as a seven-segment character generator. It allows you to generate up to ten characters including the digits 0 through 9, many letters of the alphabet, and a variety of unusual symbols.

NOW FROM BELL & HOWELL SCHOOLS! ALL NEW SELF-STUDY PROGRAM ON MICRO-PROCESSING

Completely up to date, thoroughly practical. Designed for professionals (engineers, technicians or advanced hobbyists) who need ready answers to basic programming concepts and troubleshooting techniques in microprocessing systems.

No classes or seminars to attend. You study at your own pace. Each segment is presented in a way that communicates practical, usable facts... stimulates new thinking, new ideas. Self-grading quiz at the end of each segment reinforces the major points learned. Developed and compiled through the resources of the world-famous educational division of Bell & Howell.

Send for complete facts. No salesman will call.

BELL & HOWELL SCHOOLS

Write: Bell & Howell Schools
2201 West Howard Street
Evanston, Illinois 60202

Send me complete facts on Microprocessing Self-Study Program. No obligation. No sales calls.

Name _____
Address _____
City _____
State _____ Zip _____

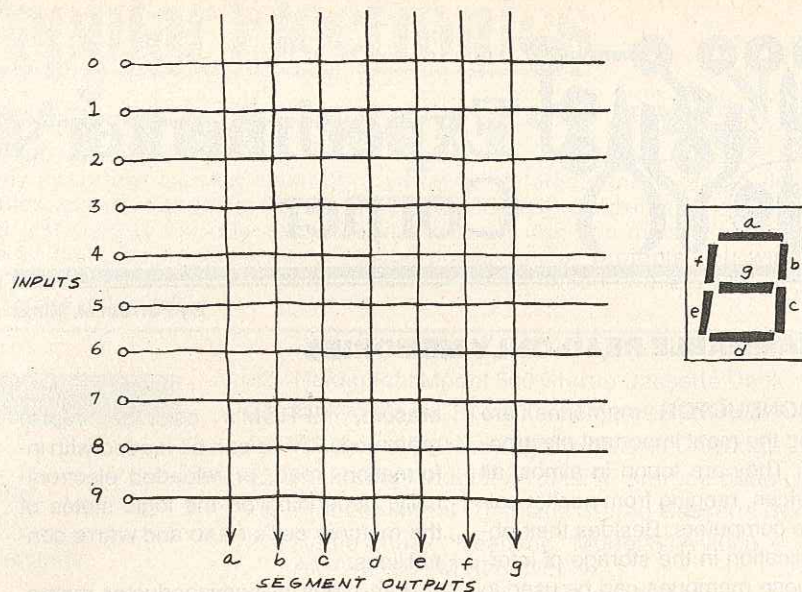


Fig. 5. Seven-segment display character generator diode PROM.

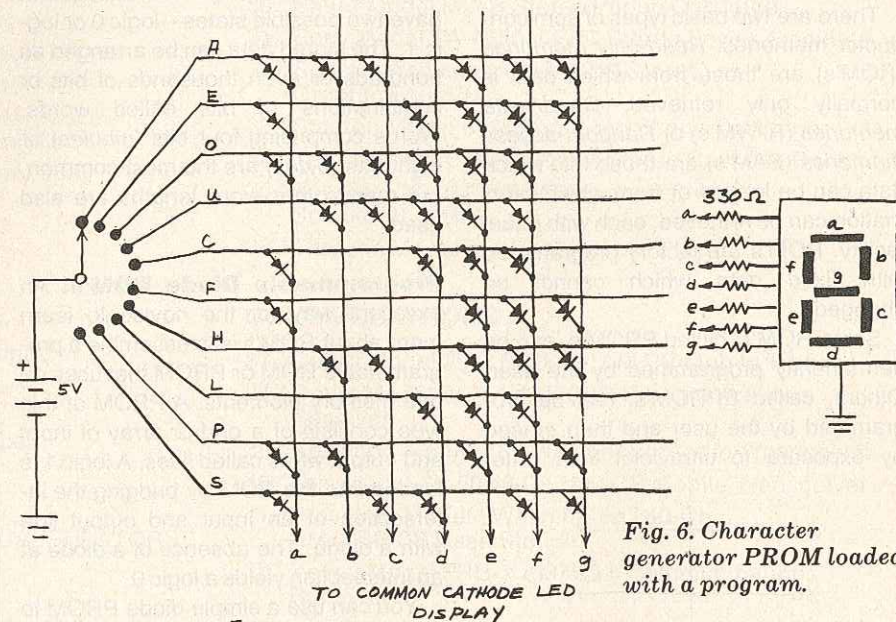


Fig. 6. Character generator PROM loaded with a program.

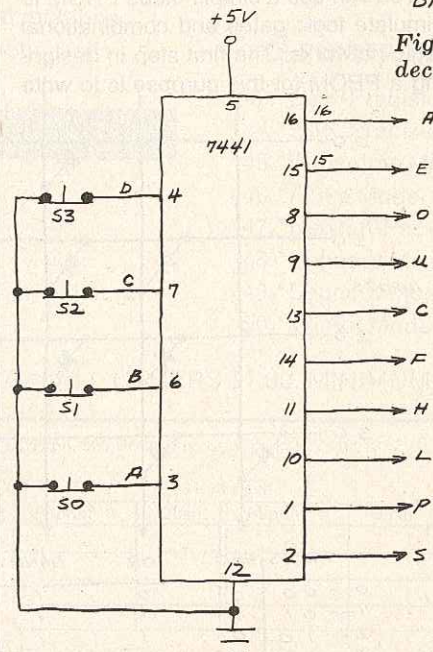


Fig. 7. Adding a decoder to the PROM.

NOTE:
1. REVERSE POLARITY OF DIODES IN PROM
2. USE COMMON ANODE LED DISPLAY

50-53:
SWITCH ON = LOGIC 0
SWITCH OFF = LOGIC 1

Even if this is your first experience with a PROM, you'll find programming very easy. Suppose you want a display that can flash words made from the characters A, E, O, U, C, F, H, L, P, and S. This assortment of vowels and consonants can generate a surprising number of words—HELP, POLE, PULL, HOLE, COOL, SELL, CAP, etc. First, you write a truth table that shows the segments of

the display that must be illuminated to produce each character.

Character	Segments
	a b c d e f g
A	1 1 1 0 1 1 1
E	1 0 0 1 1 1 1
O	1 1 1 1 1 1 0
U	0 1 1 1 1 1 0
C	1 0 0 1 1 1 0
F	1 0 0 0 1 1 1
H	0 1 1 0 1 1 1
L	0 0 0 1 1 1 0
P	1 1 0 0 1 1 1
S	1 0 1 1 0 1 1

This prom has ten input and seven output lines, so it requires a grid of 10 by 7 wires. The PROM is programmed by inserting a diode at the intersection of each character and segment line where a logic 1 exists in the truth table (Fig. 6). Simple, isn't it? If you're not convinced, try designing the same character generator with logic gates!

We can improve the character generator PROM by replacing the manual selector switch with a BCD-to-decimal decoder. True, this adds an IC, but reduces the number of input lines from ten to four and makes it possible to interface the PROM with other circuits. Figure 7 shows how the decoder is connected to the PROM.

You can assemble a working version of this diode PROM on a perforated board. Insert flea clips at each bit position and run the input and segment lines on opposite sides of the board to prevent shorts. The flea clips will allow you to insert and remove diodes. If you want to go first class, permanently wire a diode in series with an spst toggle switch at each bit position. Turning the switch on will load a logic 1. Placing the switch in the off position will load a logic 0. If you choose to do this, you'll need seventy switches, so be sure to shop around for a good price.

In any event, I hope you'll build a working diode PROM if you're interested in learning about the practical aspects of ROM's and PROM's. You'll learn something about *hardware* (the PROM and decoder), *software* (the truth table you plan to load into the PROM), and *firmware* (the truth table loaded in the PROM in the form of diodes). You'll also learn about *addressing* (the 4-bit character select word applied to the input of the decoder). All of these topics are fundamental to an understanding of advanced digital logic devices like microprocessors, calculators, and hobby computers.

The leading magazine in the personal computer field

BYTE is the magazine for the creative home computer experimenter. BYTE tells you everything you want to know about personal computers, including how to construct and program your own system.

Home computers are now practical and affordable. Low cost peripherals have resulted in more hardware and software, more applications than you could imagine. BYTE brings it all to you. Every issue filled with stimulating, timely articles by professionals, computer scientists and serious amateurs.

Fill in the coupon today. Read your first copy of BYTE; if it's everything you expected, honor our invoice. If it isn't, just write "CANCEL" across the invoice and mail back. You won't be billed, and the copy is yours. Allow 6 to 8 weeks for processing.

© Byte Publications, Inc. 1977

BYTE Subscription Dept. 07E
P.O. Box 361 Arlington, Mass. 02174 U.S.A.

Please enter my subscription for:

☐ One year U.S.-\$12 (12 issues) ☐ Two years U.S.-\$22 ☐ Three years U.S.-\$32

☐ Canada or Mexico-\$17.50 ☐ Europe (Air Delivered)-\$25

☐ Surface delivery to all other countries except Europe, Canada or Mexico-\$25

(Air delivery available on request) Please remit in U.S. funds.

☐ Check enclosed (Bonus: one extra issue) ☐ Bill me ☐ Bill Bank Americard

☐ Bill Master Charge

Card Number _____ Expiration date _____

Signature _____ Name (please print) _____

Address _____

City _____ State/Country _____ Code _____

CIRCLE NO. 7 ON FREE INFORMATION CARD

BUILD YOUR OWN

BIG SCREEN COLOR TV!

YOU ASKED FOR IT!

WE HAVE RECEIVED THOUSANDS OF INQUIRIES!

YOU REQUESTED PLANS FOR A BIG SCREEN TV THAT WOULD: utilize any portable TV as an image source — require a minimum of floor space — be a beautiful piece of furniture.

NOW — EXTRON IS HAPPY TO ANNOUNCE THE ORIGINAL LIFESCREEN I



THE NEW LIFESCREEN II

The LIFESCREEN was designed for the Do-It-Yourself enthusiast who wishes to have the enjoyment and excitement of a professional Big Screen TV — but refuses to pay the \$1500 to \$4000 that most manufacturers charge for this luxury.

FACTS

The special LIFESCREEN Lens and Front Surface mirror supplied by Extron are the same type used by major Big Screen TV manufacturers (Sony, Muntz, etc.). THESE PROFESSIONAL COMPONENTS SHOULD NOT BE CONFUSED WITH THE CHEAP PLASTIC MAGNIFYING IMITATIONS NOW FLOODING THE MARKET BECAUSE OF THE POPULARITY OF BIG SCREEN TV.

The EXTRON TV Screen — the same used by the major Big Screen TV manufacturers — is 16 TIMES BRIGHTER than a flat matte surface and 6 TIMES BRIGHTER than most flat beaded movie screens. Its parabolic shape rejects extraneous light, concentrating a highly efficient and directionally selective television image that is exceptionally sharp and colorful.

COMPLETE LIFESCREEN I PACKAGE:

YOU SUPPLY PARTS: BOARD & FORMICA FINISH

YOU SUPPLY PARTS: BOARD & FORMICA FINISH

YOU SUPPLY PARTS: BOARD & FORMICA FINISH

YOU SUPPLY PARTS: BOARD & FORMICA FINISH

YOU SUPPLY PARTS: BOARD & FORMICA FINISH

YOU SUPPLY PARTS: BOARD & FORMICA FINISH

YOU SUPPLY PARTS: BOARD & FORMICA FINISH

YOU SUPPLY PARTS: BOARD & FORMICA FINISH

YOU SUPPLY PARTS: BOARD & FORMICA FINISH

YOU SUPPLY PARTS: BOARD & FORMICA FINISH

YOU SUPPLY PARTS: BOARD & FORMICA FINISH

YOU SUPPLY PARTS: BOARD & FORMICA FINISH

YOU SUPPLY PARTS: BOARD & FORMICA FINISH

YOU SUPPLY PARTS: BOARD & FORMICA FINISH

YOU SUPPLY PARTS: BOARD & FORMICA FINISH

YOU SUPPLY PARTS: BOARD & FORMICA FINISH

YOU SUPPLY PARTS: BOARD & FORMICA FINISH

YOU SUPPLY PARTS: BOARD & FORMICA FINISH

YOU SUPPLY PARTS: BOARD & FORMICA FINISH

YOU SUPPLY PARTS: BOARD & FORMICA FINISH

YOU SUPPLY PARTS: BOARD & FORMICA FINISH

YOU SUPPLY PARTS: BOARD & FORMICA FINISH

YOU SUPPLY PARTS: BOARD & FORMICA FINISH

YOU SUPPLY PARTS: BOARD & FORMICA FINISH

YOU SUPPLY PARTS: BOARD & FORMICA FINISH