

Popular Electronics®

WORLD'S LARGEST-SELLING ELECTRONICS MAGAZINE

FEBRUARY 1978/\$1

HOW TO ADD

- A Cassette Interface to an Elf Computer
- An Audio Blend Control to a Hi-Fi Receiver

The New Micro/Mini Cassette Tape Formats

Now: Transfer PC Guides Without Film or Chemicals!

"Oscar": Communications Satellites for Everyone

TESTED THIS ISSUE


Garrard GT25 Turntable

Sansui AU-717 Stereo Integrated Amplifier

Sherwood Micro/CPU 100 Stereo FM Tuner

Ten-Tec Century/21 CW Transceiver

BUILD A
LOW-COST
EPROM
PROGRAMMER

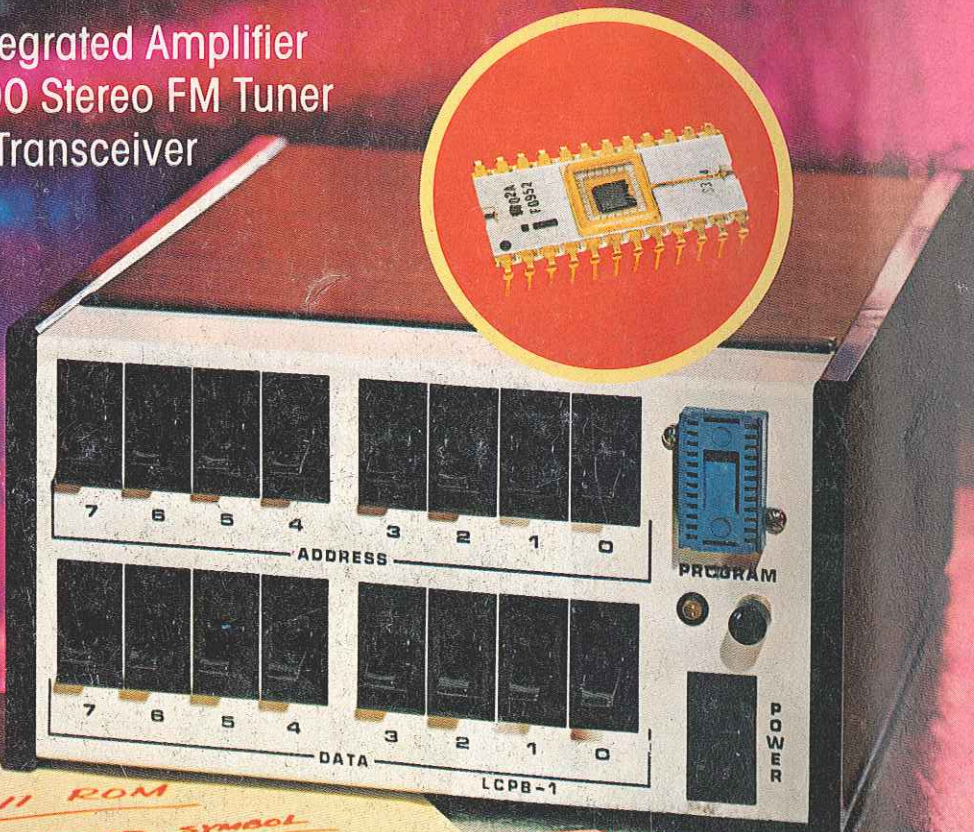

HEX/ASCII ROM

ADDRESS	INPUT	NEEDED	SYMBOL
0	00000	00110000	0
1	00001	00110001	1
2	00		

720484 CEM 02755091 141D MAY79
WILLIAM CLEMENCE
APT 3
375 ST PAUL ST
BURLINGTON VT 05401



FEBRUARY 1978

Using Existing House Wiring For Computer Remote Control PART 3

Construction and Software

BY DAN SOKOL, GARY MUHONEN, AND JOEL MILLER

THIS concludes the series of articles on computer remote control.

Data Recovery and Clock Generator. This circuit (Fig. 4) is also similar to its counterpart in the controller except that, in this case, the frequency-adjust potentiometer, *R15*, is a 10-turn potentiometer that is used for accurately synchronizing the frequencies of the controller and the remote.

UART. The data received from the controller is decoded and "unformatted" in this circuit (Fig. 5). Data is also put into the proper format to be sent to the con-

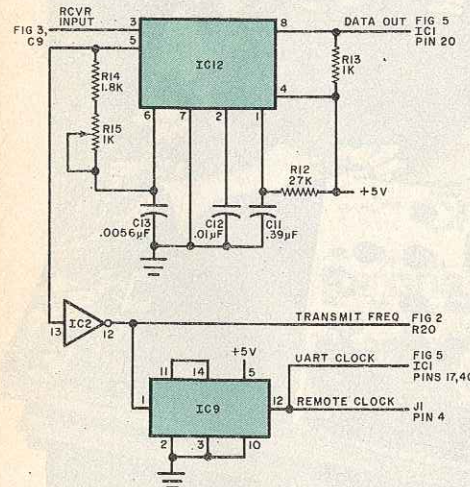


Fig. 4. Data-clock recovery is made by a PLL that delivers data output and a clock signal. The latter is divided by 16 for use in the UART.

Fig. 5. UART (IC1) decodes data received by remote and formats it to be sent to controller. It also provides interface signals for other parts of circuit.

troller. The receiver section of the UART accepts the serial input data from the phase-locked loop (IC12 in Fig. 4), and converts it to parallel data and status information.

The status information is used by the address and decode logic (Fig. 6) to indicate when data is available and if any errors occurred. Data at the receiver output is looped back to provide the first six bits of the transmit data word. The seventh and eighth bits of the transmit data word are originated by the address and command decode logic. The transmit side of the UART responds with data to the controller when the address and command logic gets a poll command.

The data word sent from the computer through the controller has a specific meaning to the remote. The first five bits (Table I) contain the address of the remote to be controlled while the sixth and seventh bits contain the command information. If the seventh bit is a zero, all remotes (up to 32 in the system) ignore the word. However, if the seventh bit is a one, the word is defined as a command to the remote whose address is contained in the first five bits. The sixth bit contains the actual command; and if it is a one, it toggles the remote channel addressed. If the sixth bit is a zero, the remote responds with poll information that

informs the computer of its status (on or off). Bit 6 of the transmitted word contains the on or off information about the remote being polled (1 is on, 0 is off). Bit 7 is always a 0 during a poll.

Address, Command Logic. In the circuit shown in Fig. 6, the incoming data word is compared with that formed by the user-selected address jumpers to determine that it, and no other remote, is being addressed. The circuit then decodes one of the four possible commands and executes the decoded information. In IC3 and IC7, the address is decoded and checked for errors, while IC4 and IC5 decode the specific command. Flip-flop IC6 controls the state of outputs A and B, while portions of IC8 provide the transmit side of the UART with correct poll information on the status of each side of the remote—circuits A and/or B.

Relay drivers Q6 and Q7 convert the outputs of the CMOS circuits to a sufficient power level.

Construction. Due to the complexity of the circuit, it is best to use a double-sided pc board as shown in Fig. 7. Note that, on the component layout guide, diodes are designated "CR" instead of "D" and integrated circuits are "U" in-

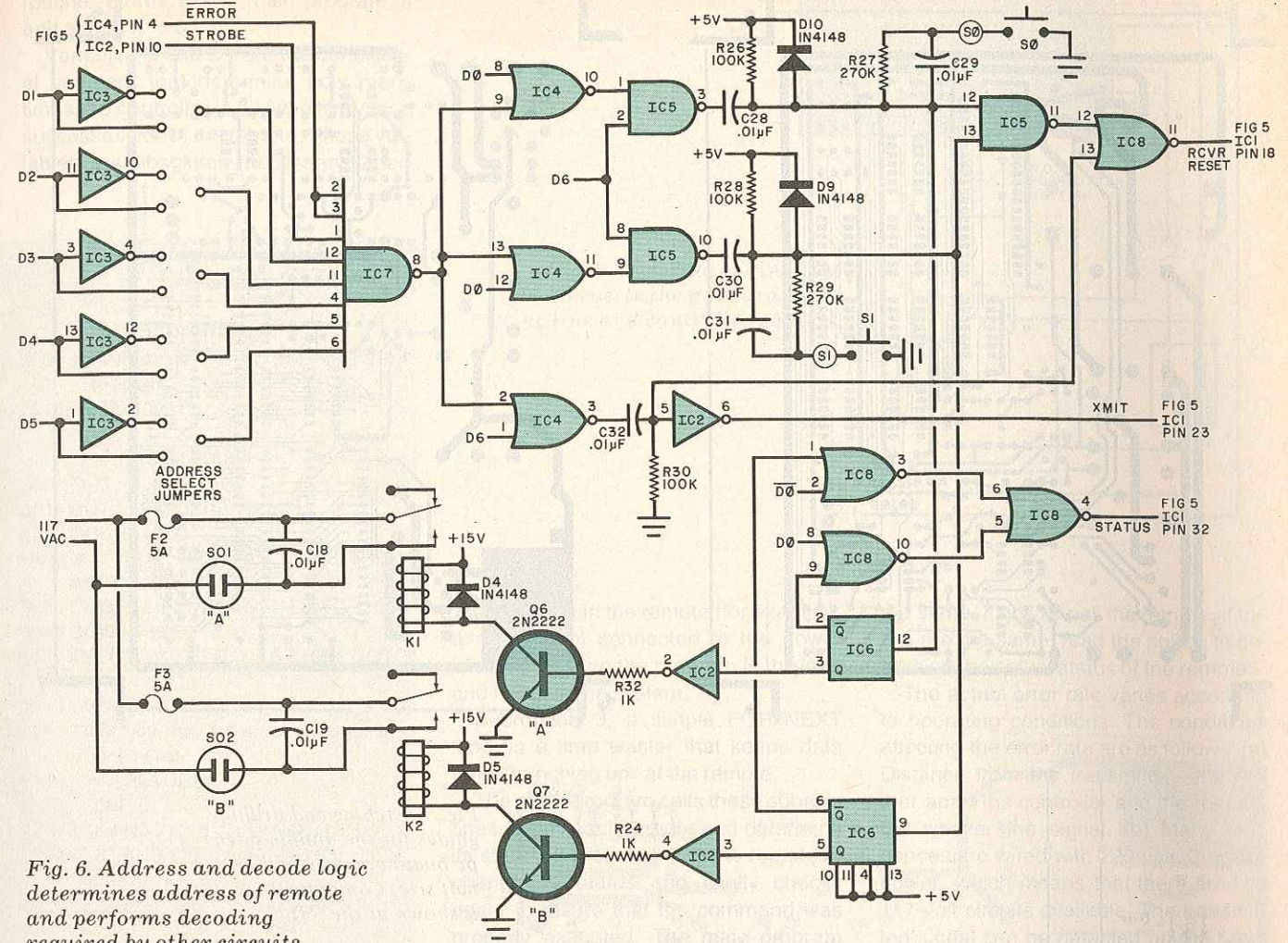
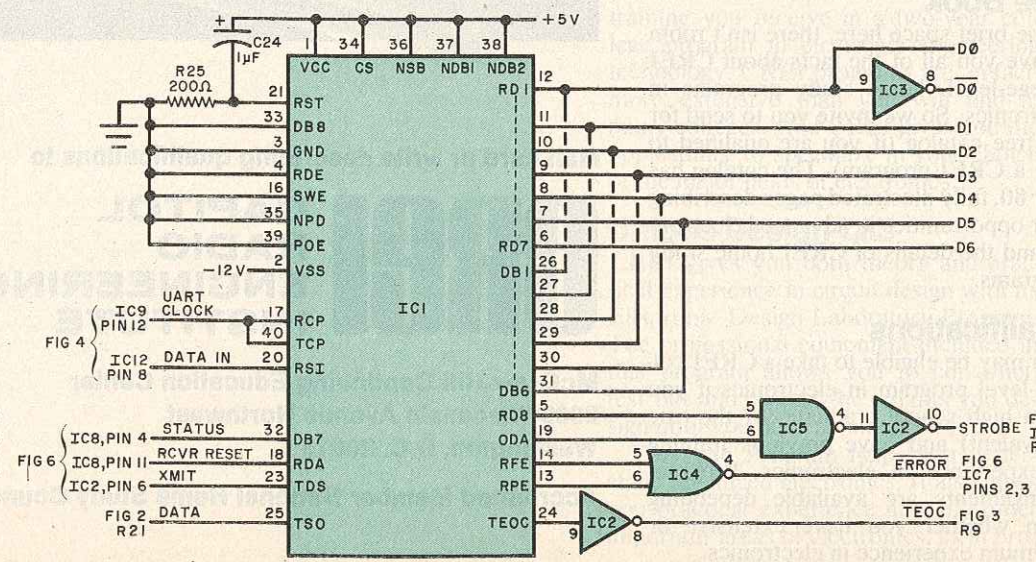


Fig. 6. Address and decode logic determines address of remote and performs decoding required by other circuits.

TABLE I

Information available at status port:

Bit	MSB	LSB
7	7	7
6	6	6
5	5	5
4	4	4
3	3	3
2	2	2
1	1	1
Use	not used	T B D O F P
	(always=1)	E A R E E
Decimal	224	16 8 4 2 1
Octal	340	40 10 4 2 1
Hex	EO	10 8 4 2 1

RPE = receive parity error. If this bit is a 1, then the character at the input port was received with a parity error. This bit clears when a word is received without error.

RFE = receive framing error. If this bit is a 1, then the character at the input port did not have the correct number of bits when it was received. This bit clears when a word is received without error.

ROR = receiver overrun error. If this bit is a 1, then the character at the input has overwritten the previous word (that is, the previous word was not read out prior to receiving this word).

ODA = output data available. When this bit is a 1, there is a character waiting to be

read at the input data port. This bit clears when the input port is addressed.

TBE = transmitter buffer empty. This bit is a 0 during the time that the output port is busy. When it is a 1, data can be presented to the output port.

MSB **LSB**
7 6 5 4 3 2 1 0
P C address
O T 0-63
L R
L L

The first six bits contain the address of the remote being contacted. The poll and control bits will determine how the data is interpreted as follows:

Bit	7	6
toggle this remote	1	1
poll this remote	1	0
ignore this data	0	x

(x = don't care)

A toggle command will cause the remote to turn on (or off) depending on its previous state. For example, to toggle remote 41 (decimal) output 233 (decimal) to the controller's output port.

stead of "IC." Sockets may be used for all IC's. Regulator *VR1* is mounted with a conventional heat sink and *VR2* can be mounted directly on the board with the seven transistors. Observe the polarity of the capacitors and diodes and make sure of the orientation of the IC's before installation. Note also that the conductive pot covering transformer *T1* should be electrically isolated from the foil traces beneath it by means of an insulating mica washer.

External wiring is made in accordance with Fig. 8, which shows the connections to be made to the two manual override pushbutton switches and the two sockets to be controlled. These parts are mounted on the rear apron of the selected chassis.

The pc board can be installed in any convenient chassis. If a metal chassis is used, be sure the pc board and other components are well insulated from the metal structure. Keep in mind that there is 117 volts ac on the pc board.

Software. The Intelligent Remote

