

Popular Electronics®

WORLD'S LARGEST-SELLING ELECTRONICS MAGAZINE


MARCH 1978/\$1

How To Build a Digital Phototachometer
A Practical Guide to Multitrack Tape Recording
Microprocessor Microcourse, Part I

Test Reports: *Sony PS-X5 Turntable,*
JVC P-3030 Stereo Preamplifier, Dahlquist DQ-1W
Low-Bass Module, B&K 1820 Frequency Counter

Experimenting with Circular Sweep





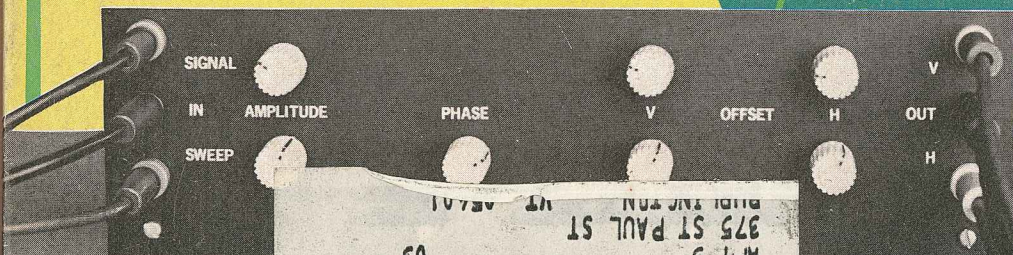
Create Exciting
Graphic Designs On
Any Oscilloscope



720484 CEM 03755091 141D MAY79
WILLIAM CLEMENCE
APT 3
375 ST PAUL ST
10780



14024 14278
Popular Electronics

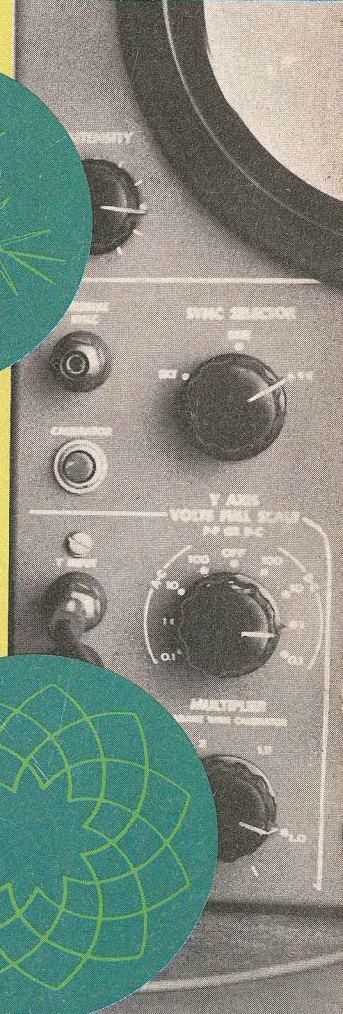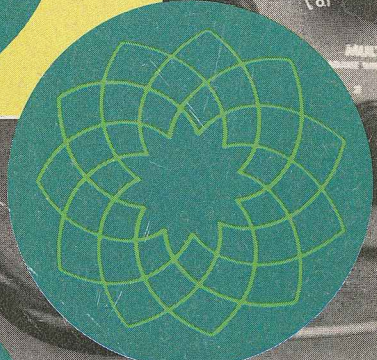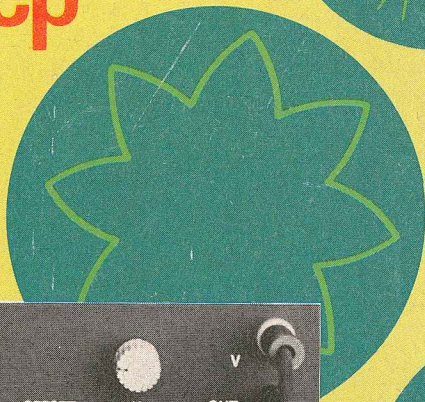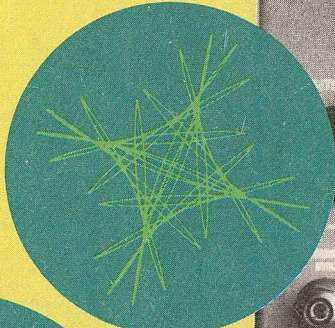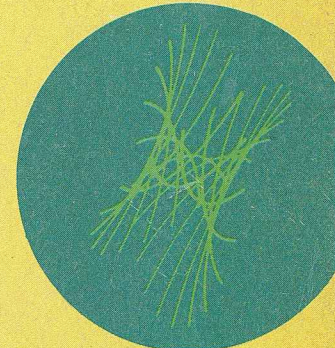

MONITOR PROGRAM

```

00 90 A1 B3 B4 B5 B6 B7 F8 FF A2 E2 21 81 B2 80 52
10 F3 3A 0B F8 38 A3 F8 29 A4 F8 33 A5 D3 3F 1D 22
20 8A 52 64 37 23 6C 30 1C D3 3F 29 37 2B 6C 64 22
30 30 28 D3 22 52 64 30 32 D4 F8 4D F4 A6 02 FD 05
40 33 47 F8 EE D5 7B 00 D4 BA D4 AA 06 A3 53 58 5D
50 78 C8 F6 9A B0 8A A0 E0 D0 4A D5 30 58 7B D0 D5
60 5A 1A 30 5D D3 7B F8 1D 3B 6D F8 07 1D 52 FF 01
70 33 6E 39 64 7A 02 30 6E F8 8D A1 D4 73 D4 8A F5
80 AC 12 9A 75 FC 01 BC D0 F8 65 A6 81 A3 F8 80 BD
90 FF 00 D6 9D 3A 90 8A D5 7B 4A BB FC 00 F8 09 AB
A0 AD D6 2B 8B 32 AB 9B FE BB 30 A1 8D F6 D6 2C 9C
B0 3A 96 D6 D6 D6 D6 30 38 1D D3 F8 0D 35 BC 35 B8
C0 FF 01 33 BE 3D C4 30 B9 F8 CD A1 30 7B F8 BA A7
D0 F8 F9 BD D7 3B D0 9D 3A D3 D7 33 D9 F8 01 BD AD
E0 D7 9D 7E BD 3B E0 D7 8D F6 33 45 9D 5A 8A D5 1A
F0 2C 9C 3A D9 30 38 D4 4A F3 3A F7 2A 9A D5 30 58
    
```

PARTS LIST

C1, C3—0.1- μ F, 100-V Mylar capacitor
 C2—0.005- μ F Mylar capacitor
 D1, D2—1N4148 diode
 IC1—74C174 hex latch
 IC2—74S471 256x8 PROM
 IC3—74C20 dual 4-input NAND gate
 IC4, IC5, IC9—4050 hex buffer
 IC6—1853 N-line decoder
 IC7, IC8—1852 8-bit I/O port
 IC10—LM3900 quad op amp
 Q1, Q3—2N5232 transistor
 Q2, Q4—2N5306 transistor
 The following are $\frac{1}{4}$ -W, 5% resistors unless otherwise noted:
 R1—200,000 ohms
 R2—100 ohms
 R3, R11, R18—3900 ohms
 R4—330 ohms
 R5, R6, R10, R14—15,000 ohms
 R7—300,000 ohms
 R8, R9, R15, R16, R17, R34—1000 ohms
 R12—47 to 250 ohms (value for 20 mA current loop)
 R13—2200 ohms
 R19 through R27, R30—22,000 ohms
 R28, R29—1 megohm
 R31, R32—100,000 ohms
 R33—10,000 ohms
 Misc.—Pc board with edge connectors to match Elf II bus, 86-pin connector, optional sockets for IC's, etc.
 Note—The following are available from Neronics R&D Ltd., 333 Litchfield Rd., New Milford, CT 06776: complete set of parts including pc board, pre-programmed monitor PROM, less 86-pin connector for \$39.95 plus \$2 postage and handling; PROM IC2 available separately for \$25 plus \$1.50 postage and handling; 86-pin connectors for \$5.70 each plus 30 cents postage and handling.

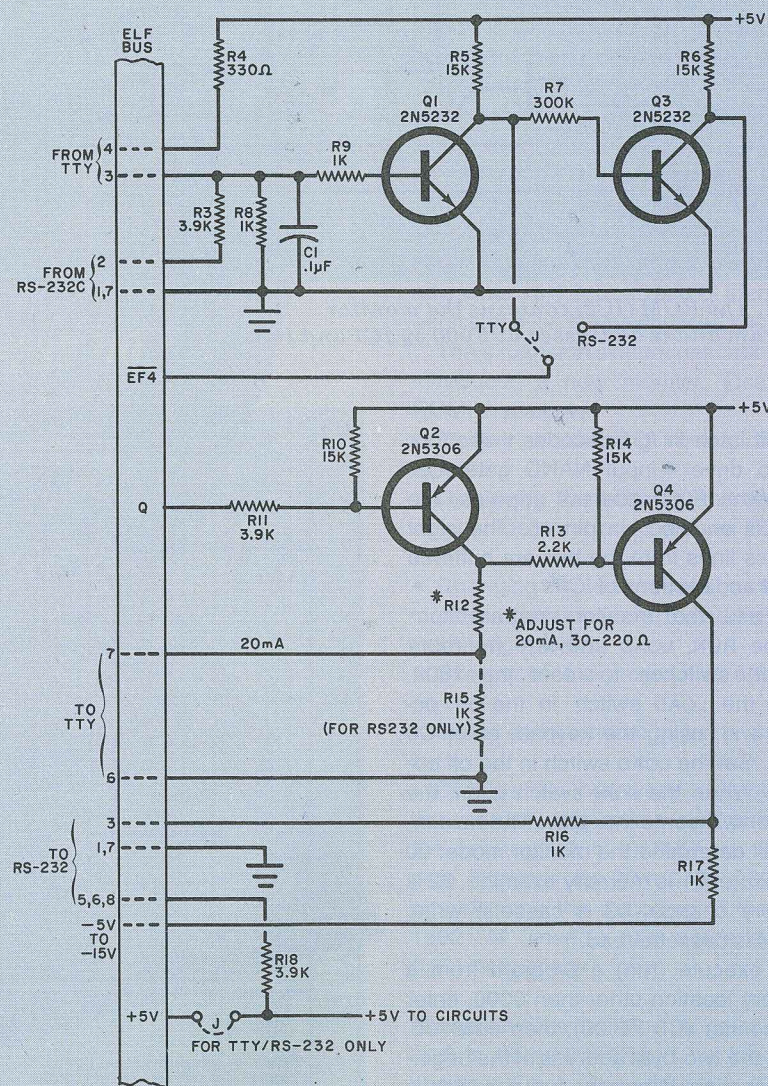


Fig. 3. Transistors Q1 and Q2 form the 20-mA current loop with Q3 and Q4 added to make up the RS-232 loop.

tape recorder has an auxiliary (high-level) input, omit R2. You may have to experiment with the value of R34 to arrive at the correct recording level.

When reading from a cassette, the serial data is fed to the EF2 line. Using an oscilloscope between the EF2 line and ground, adjust the volume control of the tape recorder until a good square wave is obtained on the EF2 line. If you get the square wave, note the position of the volume control for future use. If you cannot get a good square wave, adjust the recording level by decreasing the value of R34 (in the tape write circuit).

If the read function does not work, it may be due to the cassette recorder's inverting the polarity of the signal. This can be corrected by removing jumpers J1 and J2 and connecting the Q signal to R32 through J3.

20-mA/RS-232 Interface. This circuit (Fig. 3) requires an external dc supply of -5 to -15 volts for the RS-232 section. To receive data from a 20-mA current-loop peripheral (such as a TTY), and if the peripheral requires an external current source, then connect the R4 line to the external device (on the TTY, this should be terminal 4). The current from the device (on the TTY, terminal 3) is fed to the Q1 input circuit. The output of Q1 is jumper-selected to drive the EF4 line on the bus.

To transmit data to the current-loop peripheral, the signal from the Q line drives constant current (20mA) source Q2. Resistor R12 is adjusted to deliver a 20-mA current into the peripheral. Note that R15 is not used in the current mode. On the TTY, the two terminals would be 6 and 7.

When using the RS-232 input mode, the signal is applied to Q1 through Q3. The EF4 jumper is then set to the RS-232 position at the output of Q3.

To transmit data to the external RS-232 device, R15 is inserted between R12 and ground, and Q4 is added to produce the correct output. Note that a negative voltage supply is required for RS-232 operation. A jumper, or switch, is optionally used to remove or turn power on to this circuit.

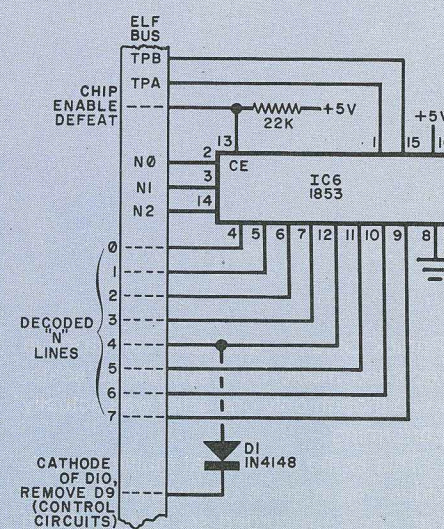


Fig. 4. The N-line decoder expands three lines from 1802 into eight.

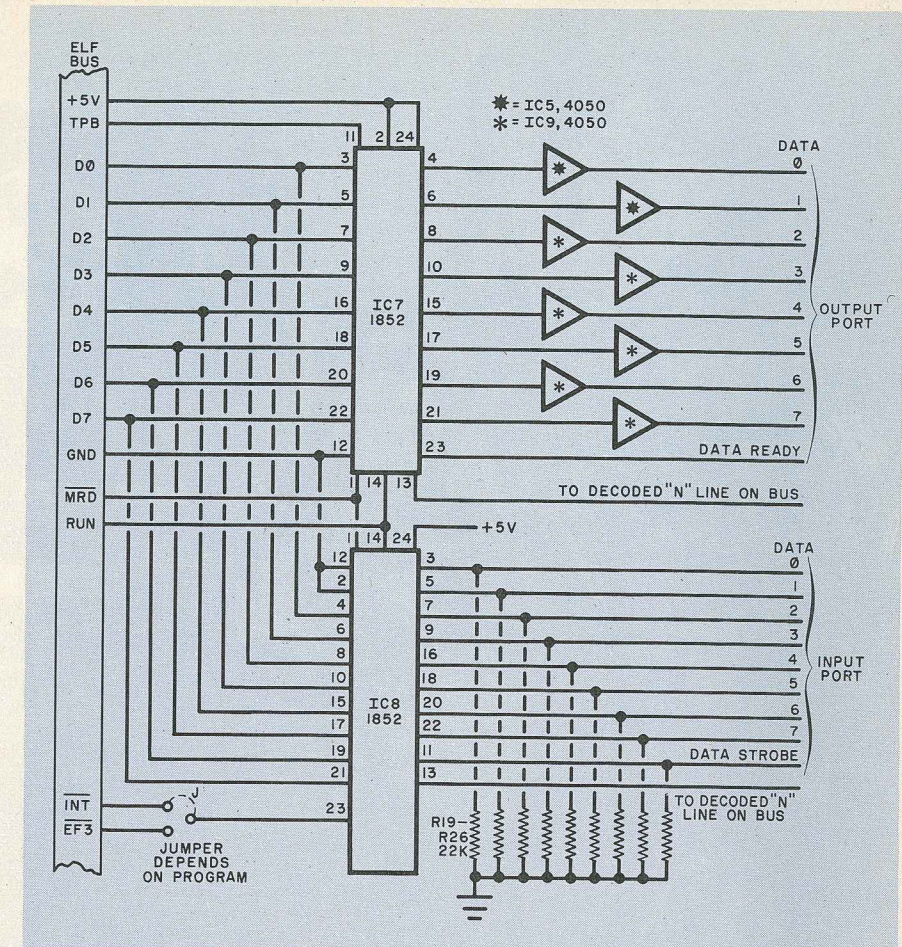


Fig. 5. Two IC's form 8-bit parallel input/output port. They use N-line from Fig. 4 determined by program.

N-Line Decoder. The three N-lines (N0, N1, N2) of the 1802 can be decoded into eight separate instructions that can be used to control eight I/O (input/output) ports using the circuit shown in Fig. 4. The decoded outputs can be connected to unused lines on the bus for easy connection to any future I/O control inputs. Control line 4 is connected to the cathode of D10 in the Elf-II (D3 in the original Elf) with D9 (D4 on the original) removed. This will allow the 6C and 64 instructions in the original programs to be executed properly.

I/O Ports. If you have a need to interface the Elf II to an external peripheral that requires parallel data (ASCII keyboard, for example), use the circuit shown in Fig. 5. Output port IC7 has its data output lines buffered by IC9 and sections of IC5. Pin 13 (CS2) of this stage can be connected to any of the decoded N-lines. When pin 2 (mode control) is high, the 1852 is configured into an output port. Data is strobed into the output port when pins 11 and 1 are high.

The three-state output drivers are enabled at all times when the 1852 is used as an output port. The service request signal at pin 23 is generated at the termination of the pin 1 and pin 13 signals and will be present (high) until the following negative high-to-low transition of the clock pulse at pin 11. The signal at pin 14 resets the port's register and service request flip-flop.

The input port is formed by IC8 with pin 2 low. The data input lines are held low by resistors R19 through R25. Pin 13 is tied to the desired decoded N-line.

Data is strobed into the port's 8-bit register by a high on the clock (pin 11) line. The negative high-to-low transition of the clock sets the service request (pin 23) flip-flop to latch the data into the register. The service-request output at pin 23 signals the 1802 that data is ready to be transferred to the bus and can be connected to either the EF3 or INT lines, depending on program requirements. The 8-bit parallel input port can service an ASCII keyboard with use of the proper software control. \diamond