

THANDAR INSTRUMENTS

ORDER ANY TWO INSTRUMENTS & TAKE A 3% DISCOUNT

-  3 1/2 Digit LED Multimeter
DM 235 \$ 69.95
-  3 1/2 Digit LED Multimeter
SC 110 99.95
-  3 1/2 Digit LED Multimeter
PDM 35 39.95
-  8 Digit LED Hand Held Freq Meter
PFM 200 99.95
-  Single Trace Portable Oscilloscope
SC 110 259.00
-  8 Digit LCD Frequency Meter
TF 040 199.00
-  8 Digit LCD Hand Held Freq Meter
TF 200 299.00
-  100 KHz Function Generator
TG 100 159.00
-  2 MHz Function Generator
TG 105 299.00
-  5 MHz Pulse Generator
TG 105 199.00
-  3 1/2 Digit LCD Bench Multimeter
TM 351 199.00
-  3 1/2 Digit LCD Bench Multimeter
TM 353 159.00
-  3 1/2 Digit LCD Hand Held Multimeter
TM 354 79.00
-  600 MHz Prescaler
TP 600 79.00

Introducing the full featured, expandable color computer!



Commodore only
VIC-20 \$299.95



ANCRONA

STORES DO NOT ACCEPT MAIL ORDERS

MAIL ORDER

P.O. BOX 2208 P. CULVER CITY, CA 90230

Minimum Order \$10.00. Add \$2.00 to cover postage and handling. Master Charge and Visa welcomed. Please include your charge card number, interbank number and expiration date. Some items are subject to prior sale. Not responsible for typos. Store pricing may vary from Mail Order pricing. We reserve the right to substitute manufacturer.

PHONE ORDERS
(213) 641-4064

ATLANTA
3330 Piedmont Rd. N.E.
Atlanta, GA 30305
(404) 261-7100

CULVER CITY
11080 Jefferson Blvd.
Culver City, CA 90230
(213) 390-3595

HOUSTON
2649 Richmond
Houston, TX 77098
(713) 529-3489

PORTLAND
1125 N.E. 82nd Ave.
Portland, OR 97220
(503) 254-5541

SANTA ANA
1300 E. Edinger Ave.
Santa Ana, CA 92705
(714) 547-8424

SUNNYVALE
1054 E. El Camino Real
Sunnyvale, CA 94087
(408) 243-4121

TUCSON
4518 E. Broadway
Tucson, AZ 85711
(602) 881-2348

CIRCLE NO. 4 ON FREE INFORMATION CARD

PROJECT OF THE MONTH

Simple BCD Keyboard Encoder

By Forrest M. Mims

THE November 1978 "Project of the Month" was a hexadecimal keyboard encoder assembled from four TTL chips (a 7400, a 74173 and a 74193). Many circuits require only one decade of decimal entry (0 through 9). The circuit in Fig. 1 implements this function with only three readily available CMOS chips. Because this new circuit is a CMOS design, its power consumption is considerably less than the TTL circuit presented earlier.

In operation, an astable oscillator made from two cross-coupled inverters (*IC1A* and *IC1B*) supplies clock pulses to *IC2*, a 4017 decade counter/decoder, and to *IC3*, a 4518 dual BCD counter. Initially, both counters are disabled by the application of appropriate logic levels to their respective enable inputs (a logic 1 at pin 13 of *IC2* and a low at pin 10 of *IC3*). The LED readout, therefore, displays the status of the outputs of *IC3* immediately after power is applied.

The keyboard is activated by closing any of the ten input switches *S0* through *S9* and then toggling RESET switch *S10* from ground to +*V_{DD}* and back to ground. If desired, the BCD output can be cleared to 0000 (all LEDs glowing) by toggling RESET switch *S10* prior to selecting a data input switch.

Assume *S3* is closed. All inactive outputs of the 4017 are low, so the keyboard (*S0* through *S9*) bus goes low and enables both *IC2* and, via *IC1C*, *IC3*. Both counters then begin a synchronized count of the pulses, applied to their CLOCK inputs.

When the fourth clock pulse has been counted, pin 7 of *IC2* goes to logic 1 and, via closed switch *S3*, disables both counters. The LEDs then display the BCD equivalent of the se-

lected switch: 0100. Counter *IC3* stores and presents at its outputs the BCD equivalent of the selected switch, even if the selected switch is opened and another is closed. Only after *S10* has been momentarily toggled will a new switch closure be detected and indicated by the output LEDs.

What happens if two or more input switches are closed when *S10* is toggled? The first closed to be scanned by the 4017 is selected. This is a form of *priority encoding*. The October 1978 "Experimenter's Corner" described the operation and use of the 74147 priority encoder. This TTL chip accepts up to ten inputs and presents at its outputs the BCD equivalent of the highest priority or most significant input while ignoring all others.

Going Further. The output LEDs shown in Fig. 1 are optional. They permit the operation of the circuit to be verified but are unnecessary in many practical applications. Of course, they can be retained. Alternatively, the outputs can be decoded by a BCD-to-seven-segment decoder/driver such as the 4511 or 4543 for display on a LED or liquid-crystal readout.

The basic circuit shown in Fig. 1 can also be modified for different applications. For example, recall that the 4518 contains *two* BCD counters, only one of which is used. The second counter can be clocked in parallel with the first (and the 4017) to provide a storage register which can remember a previous keystroke.

Other modifications may require the addition of one or more chips. For example, a 4066 quad bilateral switch can be connected to the outputs of the second counter to provide a 3-state output. ♦

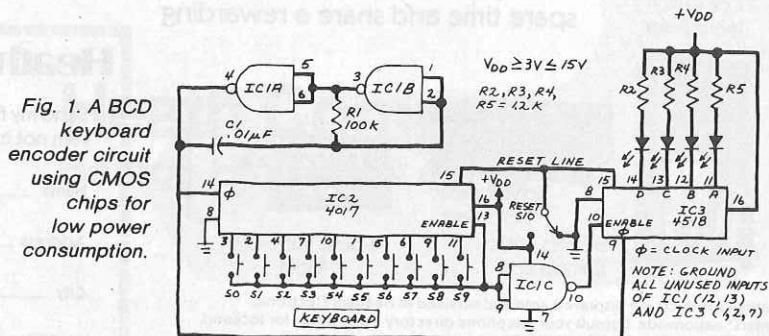


Fig. 1. A BCD keyboard encoder circuit using CMOS chips for low power consumption.