

JANUARY 1982/\$1

- Safe, Convenient Shutoff to Smoke Detectors
- "Real World" Signal Handling to TRS-80 Computers
- Overseas Broadcast Reception to Any AM Radio

Enjoy 20-dB Noise Reduction From In-The-Groove Encoding




EPI Model A300 Speaker

Cassette Recorder

ANALOG-DIGITAL CONVERTER FOR TRS-80 INTERFACING

An 8-bit, 8-channel digital circuit that allows you to connect analog voltages to your TRS-80 microcomputer

BY ADOLPH MANGIERI

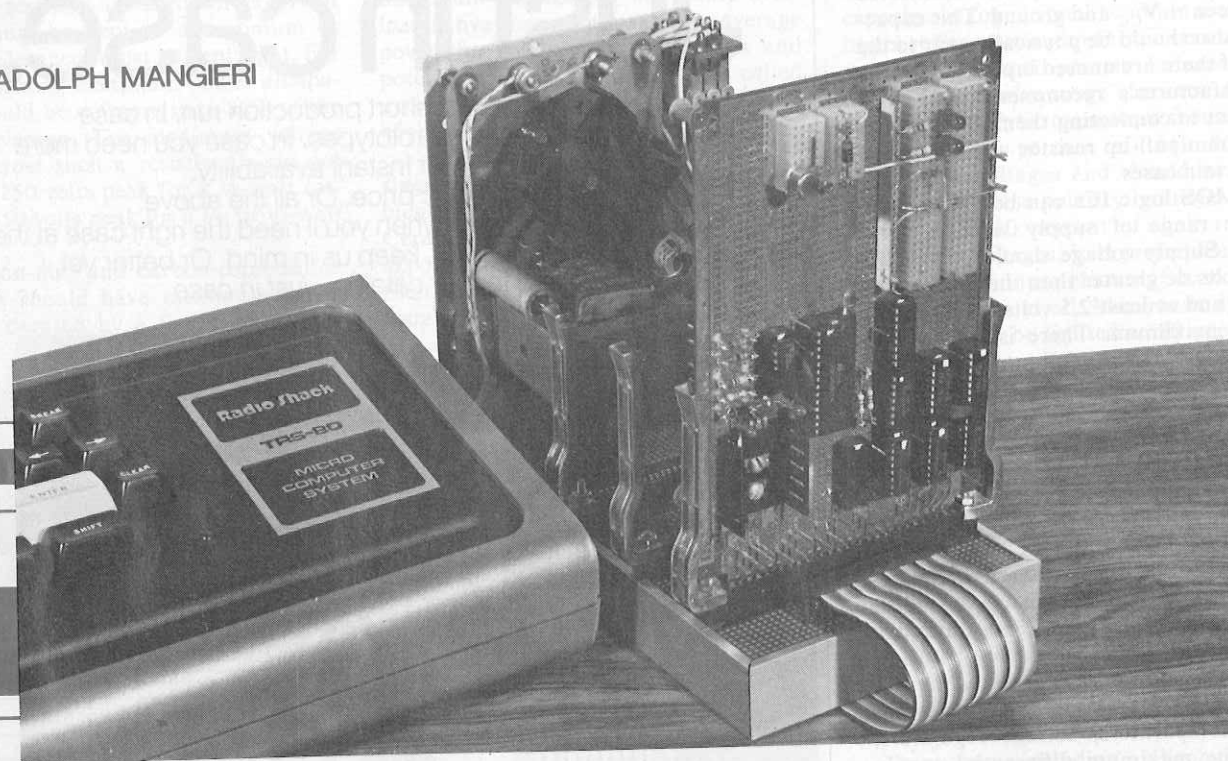

DIGITAL computers "speak and understand" only the binary language of electrical ones and zeros. Unfortunately, the binary language is not suitable for direct measuring of physical quantities such as voltage, pressure, temperature, light, or other continuously varying (analog) parameters. To utilize the digital computer in measurement and control systems, an analog-to-digital interface is required. Fortunately, such analog-to-digital converters (ADC) are now available at low cost.

Interfacing with the TRS-80 Model I microcomputer, the 8-bit, 8-channel ADC covered in this article includes a four-bit output port for controlling lamps, relays, and other devices. The output port is readily expandable to eight channels, thus providing 32 channels of control. Running in the TRS-80 TBUG monitor, the accompanying ma-

chine language program ANADIG shows how to structure a multichannel data-acquisition system. Several input and output circuits are detailed, including means to quantize the range of an input channel to output multiple decisions controlling a number of output circuit branches. The ADC accepts an input voltage and converts it to binary form for display or further processing by a computer. Common converter types include the costly high-speed 'flash' converter, the inexpensive but slow ramp converter, and the successive-approximation converter that provides excellent speed at relatively low cost. In all cases, the ADC seeks to match the level of an analog input signal with stepped and weighted reference voltages and generate a binary value when the match is found.


Considering first the successive ap-

proximation converter, Table I shows conversion of input signal of weight 67 in eight approximations taken in sequence. On the first comparison (bit D7), weight 128 is greater than 67 thus it is discarded by setting output bit D7 to zero. On trial two, weight 64 is less than 67 and is retained as a partial sum by setting bit D6 to one. The following comparisons through bit D2 are discarded because the partial sum would exceed 67. The remaining two trials bring the sum to exactly 67 and the corresponding data bits are set to one causing 67 to be converted to 01000011 or 43 hex. For an input signal of weight 255, the data bits are set to 11111111 yielding FF hex or full-scale. The converter resolves full-scale input of one part in 256.

The block diagram of Fig. 1 shows the internal circuit blocks of the eight-chan-

POPULAR ELECTRONICS

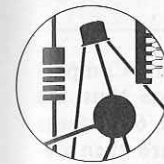Into electronics, amateur radio, or computers?



Looking for exciting projects, troubleshooting and repair tips, or hands-on do-it-yourself info? Find hundreds of time-and-money-saving ideas in the **ELECTRONICS BOOK CLUB**

Select 6 exceptional volumes for only **\$2.95** (total value up to \$113.70)

1982 Electronics Projects Calendar **FREE!**

1982 Electronics Projects Calendar FREE!

1250 List \$16.95
DIGITAL ELECTRONICS TROUBLESHOOTING

1265 List \$18.95
GIANT HANDBOOK OF 222 WEEKEND ELECTRONICS PROJECTS

1338 List \$19.95
BASIC ELECTRONICS THEORY

1250 List \$16.95
THE ILLUSTRATED DICTIONARY OF ELECTRONICS

1290 List \$15.95
IC TIMER HANDBOOK

1339 List \$13.95
EASY TEST INSTRUMENT PROJECTS

1070 List \$14.95
Digital Interfacing With An Analog World

1250 List \$16.95
MASTER HANDBOOK OF ELECTRONIC TABLES & FORMULAS

1275 List \$15.95
Artificial Intelligence

1076 List \$12.95
PRACTICAL ELECTRONICS MATH

1108 List \$11.95
THE A TO Z BOOK OF COMPUTER GAMES

1062 List \$12.95
49 MORE EASY-TO-BUILD ELECTRONICS PROJECTS

1347 List \$9.95
HOW TO TROUBLESHOOT & REPAIR ELECTRONIC CIRCUITS

1218 List \$16.95
103 PROJECTS FOR ELECTRONICS EXPERIMENTERS

1306 List \$15.95
HOW TO MEASURE ANYTHING WITH ELECTRONIC INSTRUMENTS

1251 List \$16.95
PLAYING THE STOCK & BOND MARKETS WITH YOUR PERSONAL COMPUTER

1233 List \$14.95
AC/DC ELECTRICITY & ELECTRONICS MADE EASY

1277 List \$19.95
HOW TO DESIGN/BUILD REMOTE CONTROL DEVICES

1337 List \$9.95
49 EASY-TO-BUILD ELECTRONIC PROJECTS

1229 List \$13.95
HOW TO DESIGN, BUILD & USE ELECTRONIC CONTROL SYSTEMS

1982 Electronics Projects Calendar FREE when you join!

Publisher's List \$5.95

7 very good reasons to try Electronics Book Club Blue Ridge Summit, PA 17214

- **Reduced Member Prices.** Save up to 75% on books sure to increase your know-how
- **Satisfaction Guaranteed.** All books returnable within 10 days without obligation
- **Club News Bulletins.** All about current selections—mains, alternates, extras—plus bonus offers. Comes 14 times a year with dozens of up-to-the-minute titles you can pick from
- **"Automatic Order"**. Do nothing, and the Main selection will be shipped automatically! But... if you want an Alternate selection—or no books at all—we'll follow the instructions you give on the reply form provided with every News Bulletin
- **Continuing Benefits.** Get a Dividend Certificate with every book purchased after fulfilling membership obligation, and qualify for discounts on many other volumes
- **Bonus Specials.** Take advantage of sales, events, and added-value promotions
- **Exceptional Quality.** All books are first-rate publisher's editions, filled with useful, up-to-the-minute info



ELECTRONICS BOOK CLUB
Blue Ridge Summit, PA 17214

Please accept my membership in Electronics Book Club and send the 6 volumes circled below, plus a free copy of the 1982 Electronics Projects Calendar I understand the cost of the books selected is \$2.95 (plus shipping/handling). If not satisfied, I may return the books within ten days without obligation and have my membership cancelled. I agree to purchase 4 or more books at reduced Club prices during the next 12 months, and may resign any time thereafter.

1062 1066 1070 1076 1097 1108 1128 1136
1218 1225 1229 1230 1233 1245 1249 1250 1251
1265 1277 1290 1306 1337 1338 1339 1347

Name _____ Phone _____

Address _____

City _____

State _____ Zip _____

(Valid for new members only. Foreign and Canada add 20%.)

PE-182

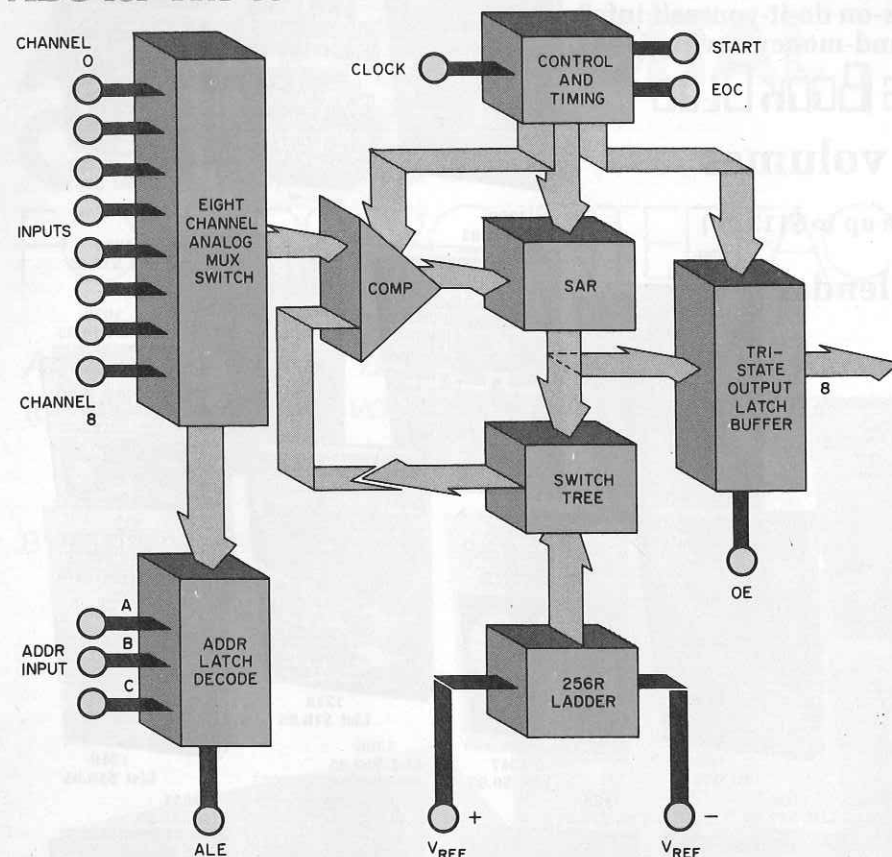


Fig. 1. Block diagram of the circuits contained in the AD0809 analog-to-digital converter used in the project.

nel converter used in this project. One of eight input signals is applied to one input of the comparator through a mux (multiplex) analog switch. The particular channel selected depends on the address bits applied to the address data latch decoder. Bit 000 selects input channel 0, bit 001 selects channel 1, and so forth up to channel 7 by bit 111.

A stable 5-volt reference is applied to a 256R resistor ladder network that supplies weighted reference voltages for comparisons. With the input signal present at one input of the comparator, a switch tree sequentially selects and applies weighted reference voltages to the other comparator input. The comparator output feeds into the successive approximation register (SAR) which performs logical decisions and assembles the binary output data in the Tri-State data-out latch and buffer. The ADC clock and timing and control circuits determine the sequence of events. Using this arrangement, at a clock frequency of 640 kHz, conversion takes place in 116 microseconds.

Figure 2 shows the ADC timing. With address bits and input signal present, address latch enable pulse (ALE) strobes the address bits into the address latch decode circuit. Pulse START initiates conversion and end-of-conversion pulse (EOC) goes low during conversion.

Following conversion, pulse EOC goes high and pulse output enable (OE) is applied to enable the data onto the bus for acceptance by the computer.

For comparison, a six-bit parallel flash converter includes a resistor ladder supplying 63 reference voltages each connected to one input of 63 comparators. The input signal connects to the

Table 1
EXAMPLE OF SUCCESSIVE APPROXIMATION

Bit	Weight	Comparison	Bit	Sum
D7	128	128 > 67	0	0
D6	64	64 < 67	1	64
D5	32	32 + 64 > 67	0	64
D4	16	16 + 64 > 67	0	64
D3	8	8 + 64 > 67	0	64
D2	4	4 + 64 > 67	0	64
D1	2	2 + 64 < 67	1	66
D0	1	1 + 66 = 67	1	67

other input of all comparators. Comparisons take place all at once thus the name "flash" converter. The 63 outputs of the comparator string are then decoded by extensive and complex logic to form the equivalent binary output. However, an eight-bit flash converter requires 255 comparators! Costly to manufacture, the flash converter is usually limited to six bits or less.

The ramp ADC technique uses a digital-to-analog converter (DAC) and a computer program to generate a staircase voltage ramp of 256 steps for use by the eight-bit converter. The stepped output of the DAC and the input signal connect to comparator inputs, and on each successive voltage step, the computer program checks comparator output and advances to the next step if the match is not found. Two hundred and fifty-five comparisons are required to reach full-scale for eight-bit conversions. Though relatively slow, ramp-conversion techniques offer advantages through software control.


Circuit Operation. As shown in the schematic of Fig. 3, clock generator IC8 is a 555 timer operating at approximately 100 kHz. Input channels 0 and 1 are the only ones used at this time, with the remaining 6 input channels grounded. A zener diode (D2, D3) and a capacitor (C5, C6) protect the active CMOS input channels.

When the program ANADIG issues an OUT instruction to port address FB (decoded by IC5), the instruction transmits channel address bits on data lines D0, D1, and D2. Thus IC5 in conjunction with the OUT signal activates IC6A pulsing ALE and START inputs with the address latched into the ADC. A time delay in the program allows time for completion of the conversion. The program then issues an IN instruction to port address FB causing IC6B to activate OE (output enable) and placing the converted data on the data bus as input to the computer.

A program task subroutine then processes the data and makes a decision for use by output port, IC7. The task decision is output to port address FB decoded by gate IC4 and enabling IC7. Data bits D0 through D3 are transmitted to IC7 and determine the output of four data latches used to control external indicator lamps or relays.

In the case of an external transistor driver (Q1), zener diode D4 protects the circuit in the event of failure of the transistor. Voltage regulator IC11 supplies five volts to the circuit.

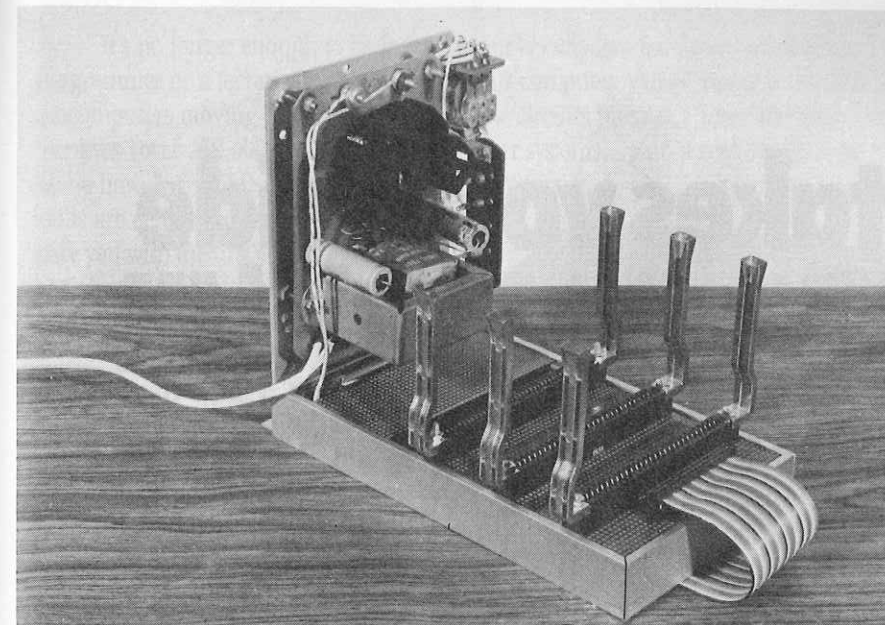Additional input channels may be connected to IC9 as required. Additional output channels are created by adding another 74LS75 (IC7) and connecting



The system is assembled on an aluminum frame with power supply and card guides.

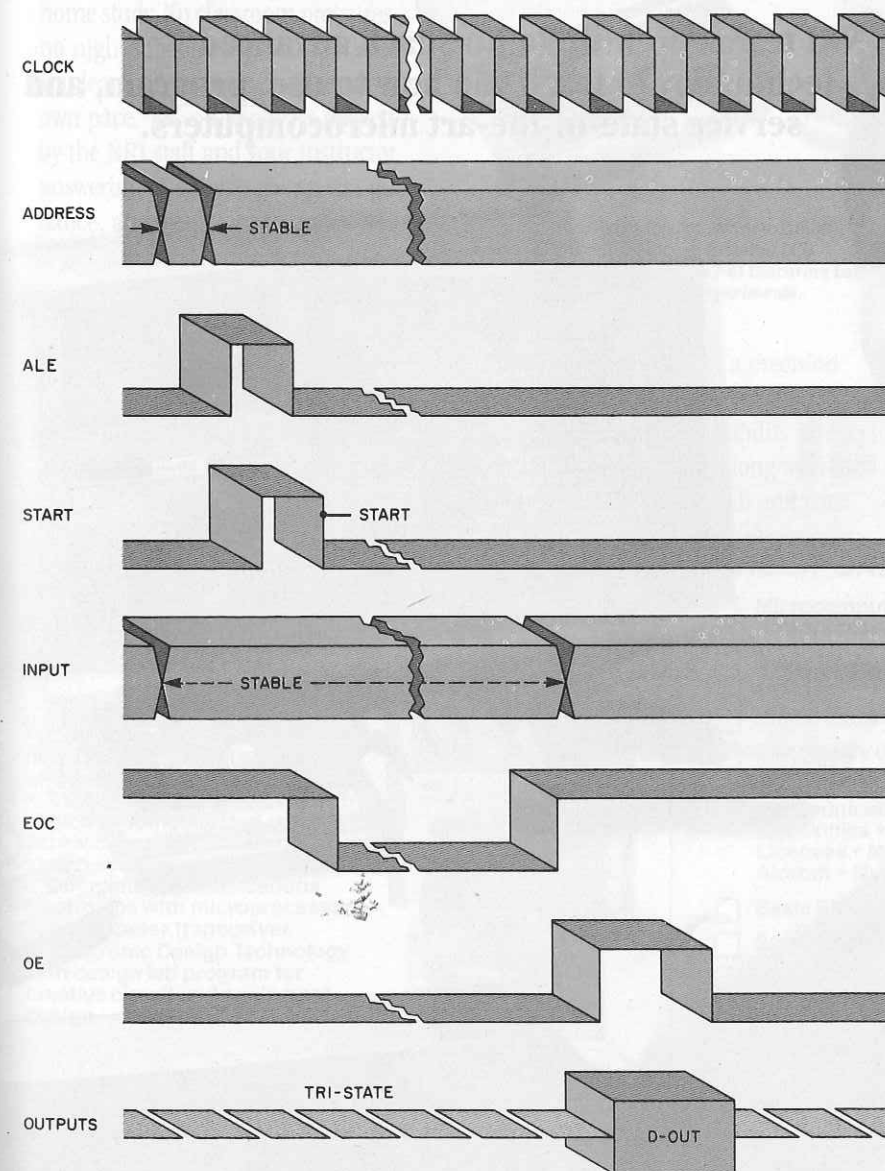


Fig. 2. Timing diagram of the analog-to-digital converter IC.

device pins 4 and 13 to pin 10 of IC6C. Data lines D4 through D7 are passed through the spare buffers of IC3 to the inputs of the second data latch.

Construction. The circuit was assembled on a Vector 4494 ANY-DIP plug card and wire wrapped. Install IC1, IC2, IC3, and IC10 in the socket row near the card fingers. Install IC4, IC5, and IC6 in the second socket row and place IC7, IC8, and IC9 in the third row. Experimentation with assorted input and output circuits can be facilitated by installing pairs of Vector T66-96 and T66-32 Klip Bloks and two T45-24 Klip Buses on the upper portion of the card as shown. The plug-board system shown consists of three Vector R644-3 44-contact card receptacles and three pairs of BR27D card guides installed on the 51X aluminum frame. Install two rows of T46-5-9 board pins with pin faces aligned on perfboard at one end forming a male IDC connector. Use a 40-line IDC cable disconnect at the plug board system. A Jameco No. JE210 5-to-15-volt adjustable regulated power supply set for 12-volts powers the circuit. Do not run the TRS-80 5-volt supply to the plug board system. As an alternative to the plug board system, assemble the circuit on Vector 8002 or 8004 Circboards for wire wrapping and install the card in the 51X aluminum frame.

Checkout. With integrated circuits removed and ribbon cable disconnected from the computer, power the voltage regulator and check voltage distribution at the pertinent socket pins. Check voltages at the far end of the cable and be certain that supply voltages do not feed back to the computer. Install the integrated circuits taking usual precautions when handling the CMOS converter chip. Energize the circuit and verify presence of clock pulses at pin 3 of IC8 using either a counter or oscilloscope. With power off, make connections to the computer and verify proper operation of the computer. Look for shorted bus lines if the computer fails to function.

Connect the input test circuit shown on the schematic diagram to the input of channel zero. Jumper channel-one input to channel-zero input. Enter and load program ANADIG into memory using the TRS-80 T-BUG monitor and break the looping program by inserting STOP code CD 91 40 at address 4A27H. Set test potentiometer R6 to its ground end, and run the program. Both LED1 and LED2 should turn off. Verify that data input buffer memory location 4A00H and 4A01H hold data 00 and that output buffer 4A08H holds 00. Set the test potentiometer to five volts and observe that both LEDs glow. Verify that chan-

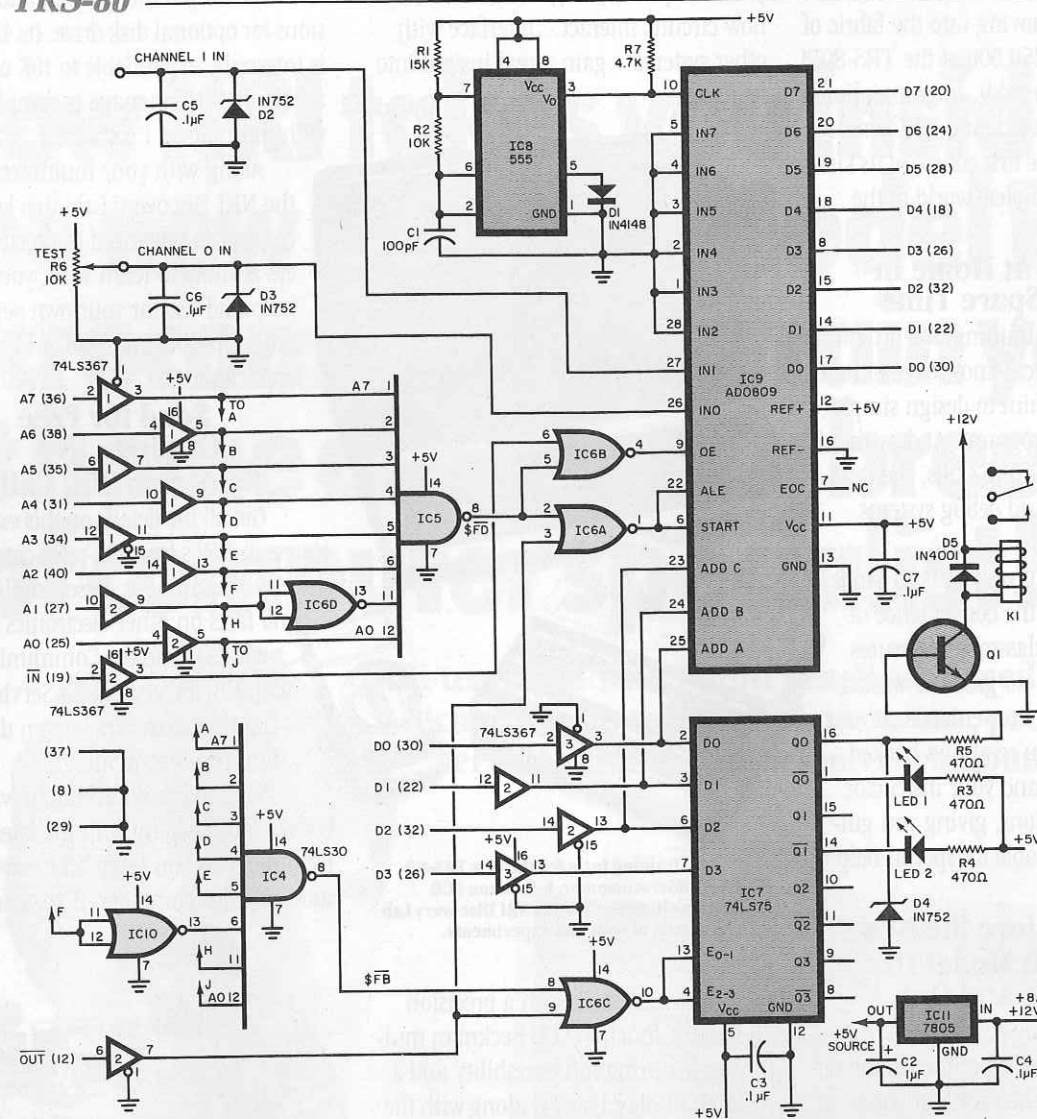


Fig. 3. A 555 clock generator, IC8, operates at approximately 100 kHz. Input channels 0 and 1 are the only ones used in this application.

PARTS LIST

- C1—100-pF ceramic capacitor
C2—1.0- μ F, 35-V tantalum electrolytic
C3 through C7—0.1- μ F, 15-V disc capacitor
D1—1N4148 switching diode
D2,D3,D4—1N752 5.6-V zener diode
D5—1N4001 rectifier
IC1,IC2,IC3—74LS367 three-state hex buffers
IC4,IC5—74LS30 8-input NAND gate
IC6,IC10—74LS02 quad 2-input NOR gate

- IC7—74LS75 4-bit data latch
IC8—555 timer
IC9—ADC 0809 eight-bit, eight-channel
ADC (available from Jameco Electronics,
1355 Shoreway Rd., Belmont, CA
94002)
IC11—7805 5-V, 1-A voltage regulator
K1—12-V relay
LED1, LED2—Light-emitting diode (XC-
526R or equiv.)
Q1—2N3053, RS-276-2030 npn transistor
R1—15-k Ω , 1/4-W resistor

- R2—10-k Ω , 1/4-W resistor
R3,R4,R5—470- Ω , 1/4-W resistor
R6—10-k Ω potentiometer
R7—4.7k Ω , 1/4-W resistor
Misc: Vector 4494 plug board; 51X aluminum frame; R644-3 44-contact card receptacles (3); BR27D card guides (6); T46-5-9 board pins; perfboard; 28-pin DIP socket; 16-pin DIP sockets (4); 14-pin DIP sockets (4); T49 Klip-Wrap posts; T66-96, T66-32 Klip Bloks (pairs); T45-24 Klip Bus (2); ribbon cable and connectors; wire; etc.

nels zero and one data buffers hold data FF or 255 while outport buffer 4A08H now holds 03. Vary *R6* slowly about the trip points. Notice that LED1 flickers and relay *K1* chatters at the trip point. Notice that the turn-on and turn-off points of *LED2* differ slightly and with no flicker. This is the result of dead-band or hysteresis built into the task program of channel one.

Software. Use program ANADIG shown here for initial experiments with multichannel data acquisition and processing and write your own programs for specific applications. The looping main program RUN performs initializations, issues channel addresses, and CALLS subroutine START which initiates A/D conversions followed by subroutines TASK0 and TASK1 which control the

relay output. Memory locations 4A00H through 4A07H respectively store input data for channels zero through seven. Location 4A08H holds the output byte common to all output channels.

Tracing through a typical program run, index register IX is initialized to point to the input data buffer. The output byte is arbitrarily cleared to 00. Channel zero address 00 is first loaded

ANADIG TEST PROGRAM

```
00100 ;FILENAME - ANADIG
00110 ;BY ADOLPH A. MANGIERI 4/81
00120 ;CHAN BUFFER - 4A00H THRU 4A07H
00130 ;OUTPORT BUFFER - 4A08H
```

LA00	00140	ORG	LAOOH	
0009	00150	DEFS	9	;BUFFERS
LA09 DD21004A	00160	LD	IX,LAOOH	;POINTER
LA0D DD360800	00170	LD	(IX/8H),OOH	;CLR BUFFER
LA11 3E00	00180	LD	A,OOH	;CHAN 0
LA13 CD7A4A	00190	CALL	START	;START A/D
LA16 DD7700	00200	LD	(IX/0),A	;SAVE DATA
LA19 GD9D4A	00210	CALL	TASKO	;DO TASK 0
LA1C 3E01	00220	LD	A,01H	;CHAN 1
LA1E CD7A4A	00230	CALL	START	;START A/D
LA21 DD7701	00240	LD	(IX/1),A	;SAVE DATA
LA24 GDBD4A	00250	CALL	TASK1	;DO TASK 1
LA27 18E8	00260	JR	LOOP1	;LOOP
0051	00270	DEFS	81	;SPACE
LA7A C5	00280	FUSH	BC	;SAVE
LA7B D3FD	00290	OUT	(OFDH),A	;START A/D
LA7D 062F	00300	LD	B,2FH	;TIME DELAY
LA7F 10FE	00310	DJNZ	LOOP2	;LOOP2
LA81 DBFD	00320	IN	A,(OFDH)	;GET DATA
LA83 C1	00330	POP	BC	;RESTORE
LA84 C9	00340	RET		;RETURN
0018	00350	DEFS	24	;SPACE
LA9D F5	00360	PUSH	AF	;SAVE
LA9E E5	00370	PUSH	HL	;SAVE
LA9F D5	00380	PUSH	DE	;SAVE
LA00 2600	00390	LD	H,OOH	;CLEAR H
LA02 1600	00400	LD	D,OOH	;CLEAR D
LA04 2E7C	00410	LD	L,7CH	;TRIP POINT
LA06 B7	00420	OR	A	;CLEAR CARRY
LA07 DD5E00	00430	LD	E,(IX/0)	;GET DATA
LA0A ED52	00440	SBC	HL,DE	;COMPUTE
LA0C FAF54A	00450	JP	M,SET0	;GO IF NEG
LA0F DDCB08B6	00460	RES	0,(IX/8)	;RES BIT 0
LA03 1804	00470	JR	LDPORT	;EXIT
LA05 DDCB08C6	00480	SET0	SET	0,(IX/8H)
LA09 DD7E08	00490	LDPORT	LD	A,(IX/8H)
LA0C D3FB	00500	OUT	(OFBH),A	;SEND DATA
LA0E D1	00510	POP	DE	;RESTORE
LA0F E1	00520	POP	HL	;RESTORE
LA00 F1	00530	POP	AF	;RESTORE
LA01 C9	00540	RET		;RETURN
0019	00550	DEFS	25	;SPACE
LA0B F5	00560	PUSH	AF	;SAVE
LA0C E5	00570	PUSH	HL	;SAVE
LA0D D5	00580	PUSH	DE	;SAVE
LA0E 2600	00590	LD	H,OOH	;CLEAR H
LA00 1600	00600	LD	D,OOH	;CLEAR D
LA02 2E7E	00610	LD	L,7EH	;HI LIMIT
LA04 DD5E01	00620	LD	E,(IX/1H)	;GET DATA
LA07 B7	00630	OR	A	;CLEAR CARRY
LA08 ED52	00640	SBC	HL,DE	;COMPUTE
LA0A FAF64A	00650	JP	M,SET1	;SET BIT 1
LA0D 2E7A	00660	LD	L,7AH	;LO LIMIT
LA0F ED52	00670	SBC	HL,DE	;COMPUTE
LA01 F2FC4A	00680	JP	P,RES1	;JP IF POS
LA04 180F	00690	JR	EXIT	;TO EXIT
LA06 DDCB08CB	00700	SET1	SET	1,(IX/8H)
LA0A 1804	00710	JR	OUTPRT	;SET BIT 1
LA0C DDCB08BE	00720	RES1	RES	1,(IX/8H)
LA00 DD7E08	00730	OUTPRT	LD	A,(IX/8H)
LA03 D3FB	00740	OUT	(OFBH),A	;SEND DATA
LA05 D1	00750	EXIT	POP	DE
LA06 E1	00760	POP	HL	;RESTORE
LA07 F1	00770	POP	AF	;RESTORE
LA08 C9	00780	RET		;RETURN
0000	00790	END		
0000	TOTAL ERRORS			
OUTPRT	LA00			
EXIT	LA05			
RES1	LA0C			
SET1	LA06			
LDPORT	LA09			
SET0	LA05			
LOOP2	LA7F			
TASK1	LA0B			
TASK0	LA9D			
START	LA7A			
LOOP1	LA11			
RUN	LA09			

into register A and subroutine START is CALLED. Routine START loads the address into the converter and starts A/D conversion. After a time delay set by byte 2F at address 4A7EH, the program returns to RUN with converted data in register A. Program RUN stores the data at address 4A00H and CALLS TASK0. Subroutine TASK0 fetches the stored input data and subtracts it from trip point 7C (124) located at address 4AA5H. If the result is negative, bit B0 of the output byte is set to one or otherwise set to zero. The output byte is then transmitted to the relay port data latch. Bit B0 now as data bit D0 may alter the status of output channel zero. The next program module of RUN addresses itself to channel one and TASK1 in a similar manner.

Subroutine TASK1 includes an upper trip point 7E (126) at address 4AE3H and a lower trip point 7A at address 4AEEH. When the converted input falls between these limits, bit B1 of the output data byte is left unchanged. This introduces hysteresis much like a Schmitt trigger and prevents repetitive operation of mechanical relays and solenoids when the input levels hover near the trip points. The trip points and dead-band are readily altered to suit the application. Use the TRS-80 TBUG machine language monitor to enter the object code. No changes are required for entry into either Level I or Level II machines. Alternatively, enter the source code or assembly listings using the TRS-80 Editor/Assembler EDTASM. Once the code is entered, make a tape copy using TBUG. Minor program changes are best entered manually using the TBUG. For major alterations, restructuring, or relocation of code, use EDTASM which markedly reduces the effort.

Input and Output Circuits. Input circuit Fig. 4A uses a thermistor for sensing temperature or a light-dependent resistor for sensing light levels. Resistor *Ra* can be a potentiometer for calibration or setting of trip points. The sensor and pot can be interchanged. It is best to include RC filtering in the input circuit to remove noise and ac components which affect conversion. Try 100,000 ohms for *Rb* and 0.1 μ F for *Ca* or higher values if the RC time constant is not objectionable. Figure 4B shows two potentiometers of a joystick having two outputs which feed into two channels of the ADC, with the game program processing the converted data.

Low-level voltages from devices such as a photovoltaic cell or thermocouple can be amplified by an op amp such as the LM324 as shown in Fig. 4C. Stage gain or scaling depends on the ratio of

TOLL FREE: (800) 221-8180
IN NEW YORK CALL: (212) 732-8600

"WE'RE NO. 1 & TRYING HARDER!"

THIS MONTH'S SUPER SPECIALS!

VIDEO and AUDIO

VIDEO RECORDER

- PANASONIC PV-1470 (VHS Recorder).....\$189
- SONY VCR-200 (VHS Recorder).....\$179
- SONY S-5000 (Beta Recorder).....\$179
- JVC HR-7300 (VHS Recorder).....\$179
- PANASONIC PV-4510 (Port VHS).....\$195
- RCA VCR-170 (Port VHS).....\$195
- JVC HR-2200 (Port VHS).....\$189

STEREO-TO-GO

- SONY WALKMAN II (Cass Stereo).....\$129.95
- KUICHO (Cass Stereo).....\$149.95
- AWA C54-1 (Cass Stereo).....\$149.95
- SONY SRF-40 (FM Stereo).....\$149.95
- PANASONIC RC-33 (Cass Stereo).....\$149.95
- TOSHIBA K151 (Cass Stereo).....\$149.95

HI-FI

- PIONEER SX-5 (Receiver).....\$229.95
- PIONEER SX-7 (Receiver).....\$249.95
- TECHNICS SL-303 (Turntable).....\$109.95
- DUAL 62255 (Turntable w/Car).....\$109.95
- TEAC V9 (Cassette Deck).....\$109.95
- AKAI GXF-90 (Cassette Deck).....\$139.95
- TECHNICS RS-250 (Cassette Deck).....\$149.95

COLOR T.V.

- SONY KV-1221R (12" Remote).....\$149
- SONY KV-1515 (15" Screen).....\$179
- SONY KV-1745R (17" Remote).....\$199
- SONY KV-1945R (19" Remote).....\$199

VIDEO ACCESSORIES

- ROBIN BLK ERASER.....\$29.95
- TELEADAPTER TE-200.....\$29.95
- VIDEO DUST COVER.....\$29.95
- VIDEOCRAFT DETAILER.....\$29.95

HEADPHONES

- SONY MDR-31 (Micro).....\$34.95
- SONY MDR-31 (Micro).....\$34.95
- SONY MDR-31 (Micro).....\$34.95
- SONY MDR-31 (Micro).....\$34.95
- SONY MDR-31 (Micro).....\$34.95

ELECTRONICS

CALCULATORS

- CASIO VL-80 (Financial Calc).....\$39.95
- CANON F100 (Printer, Elec. Display).....\$49.95
- TI-59 (Programable).....\$79.95
- HP-36C (Financial Print).....\$49.95
- PANASONIC JE-8336 (Clock Calc).....\$49.95

ANSWERING MACHINES

- CODE-A-PHONE 1550 (w/Telephone).....\$229
- PANASONIC KXT-4530 (Remote w/Vol).....\$335
- RECOR-800 (800).....\$199
- PHONEMATE 900 (Autoscan).....\$199

SCANNERS

- BEARCAT TRIN SCAN (Aircraft Trans).....\$129
- BEARCAT ALERT (Weather Cond).....\$39
- BEARCAT 300 (2100 frequencies).....\$369

WATCHES

- CASIO CA-70 (Calculator, Game).....\$39.95
- CASIO S-300 (Stopwatch, Quartz).....\$29.95
- CASIO C-701 (Calculator).....\$49.95
- CASIO F-82 (Stopwatch, Alarm).....\$24.95

CAR STEREO

IN-DASH CASSETTE

- PIONEER ES-5100 (Digital, RIB).....\$209.95
- SANYO FC-12 (Digital Display).....\$149.95
- CLARION CLA-8550R (RIB, Auto Rev).....\$179.95
- SONY XR-77 (Rear, Auto, Cass).....\$299.95
- JENSEN RE-512 (Push Button, Air).....\$245.95

CAR SPEAKERS

- JENSEN J-1031 (6x9 Inch).....\$39.95/PAIR
- JENSEN J-1201 (6x9 Inch).....\$69.95/PAIR
- PIONEER 16-16 (6x9 Inch).....\$139.95/PAIR
- PANASONIC EAB-920 (6x9 Inch).....\$109.95/PAIR
- SONY XS-66 (6x9 3 Way).....\$109.95/PAIR

RADAR DETECTORS

- RUZZBUSTER ELITE.....\$119.95
- RUZZBUSTER (Remote Wireless).....\$134.95
- RUZZBUSTER (Superhet).....\$199.50
- FOX VXBEL.....\$109.50
- FOX REMOTE.....\$109.50
- RADAR INTERCEPT (Superhet).....\$199.50

BLANK CASSETTES

AUDIO

MINIMUM ORDER 12 TAPES

- AMPEX Metal C-60.....\$2.99
- BASE P-60 (C-60).....\$2.75
- FUJI EX-100 (C-60).....\$2.99
- SCOTCH Highlander C-60 3/4".....\$2.99
- SCOTCH Master C-60.....\$3.25
- SCOTCH Master C-60 2 For.....\$4.49
- MANICORE 1/2 Inch C-60.....\$2.99
- SONY UX1 C-60.....\$2.75
- SONY TC-C-60.....\$2.75
- TDK D-60.....\$2.99
- TDK D-90.....\$2.99
- TDK SA-C-60.....\$2.99
- TDK MA-C-60 (Metal).....\$2.99
- TDK SAV-C60.....\$2.99
- MAXELL UD-60 (LD).....\$2.99
- MAXELL UD-60 (LD).....\$2.99
- MAXELL UD-60 (LD).....\$2.99
- MAXELL UD-60 (LD).....\$2.99
- MAXELL UD-60 (LD).....\$2.99

VIDEO

WE CARRY VIDEO TAPES BY AMPEX, BASE, FUJI, JVC, MAXELL, MEMOREX, PANASONIC, RCA, SCOTCH, SONY AND TDK.

- ALL BETA L-500.....\$10.95
- ALL BETA L-750.....\$12.95
- ALL VHS L-120 (Eagle).....\$12.95
- MATEL Interdiction Game.....\$229.50
- ATARI Video Game CX-2600.....\$139.95
- ATARI Space Invaders.....\$24.95
- ATARI Asteroids.....\$29.95
- ALL MATEL GAME CARTRIDGES AVAILABLE.....\$24.95
- DISCHARGER D-4 System.....\$9.95
- AMPEX T-120.....\$12.95
- AMPEX L-500.....\$9.95
- FUJI T-120.....\$13.95
- FUJI T-90.....\$12.95
- BASE L-500 (Pure Chromium).....\$9.95
- BASE L-120 (Pure Chromium).....\$13.95
- MAXELL LCL-10 (Beta Clean).....\$16.95
- TDK T-120.....\$14.49
- TDK HGH-120.....\$19.95

WE STOCK B&W, COLOR VHS, VHS AND BETA VIDEO RECORDERS AND HOME MOVIES FROM ALL MAJOR HOLLYWOOD STUDIOS. SEND FOR FREE CATALOG!

REMEMBER: J&R'S POLICY IS TO MEET OR BEAT ANY PRICE

HOW TO ORDER BY MAIL: FOR PROMPT AND COURTEOUS SHIPMENT, SEND MONEY ORDER, CREDIT CARD, CASHIER'S CHECK, MASTERCARD, VISA. (Include card number, expiration date and signature) DO NOT SEND CASH, PERSONAL AND BUSINESS CHECKS MUST CLEAR OUR BANK BEFORE PROCESSING. SHIPPING AND INSURANCE CHARGE IS 4% OF TOTAL ORDER WITH A \$3.95 MINIMUM CHARGE. NEW YORK STATE RESIDENTS MUST ADD SALES TAX. ALL MERCHANDISE IS BRAND NEW, FACTORY FRESH AND 100% GUARANTEED.

23 PARK ROW, Dept PE, NEW YORK CITY, 10038

SEND FOR FREE 200 PAGE AUDIO/VIDEO CATALOG

245

246

247

1000