

Radio-Electronics

FOR MEN WITH IDEAS IN ELECTRONICS


IT'S EASY TO INSTALL BURGLAR ALARMS - MATV - PA - INTERCOMS

Experiments With Diode Switching

Don Lancaster's Logic Demonstrator

Amplified Car Radio Antennas

Build IC Pocket Calculator

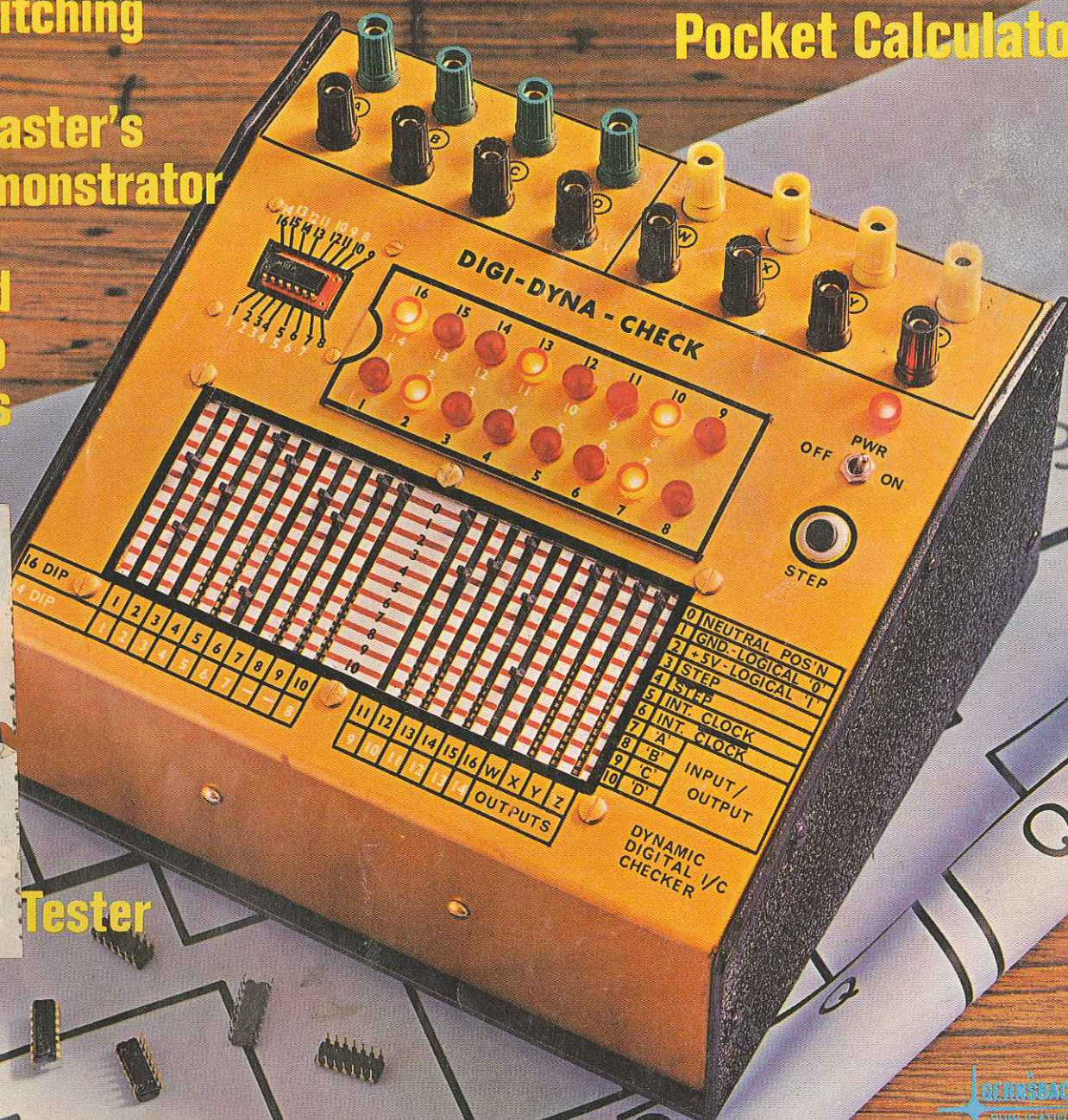

Tester




625672 JNK BU 482R94 DEC72 1 A
 05 4
 ROBERT J JENKINS
 BX 482
 VIAN OK 74962

connected to the correspondingly numbered pins of a 16-pin DIP (see Fig. 2) IC test socket and to sixteen lamp-driver assemblies used to monitor logic levels present at all sixteen IC pins simultaneously. The remaining four sliders, marked W, X, Y, and Z in Fig. 1, are wired to four similarly marked 5-way binding posts. Six of the matrix positions are connected internally to ground (logical 0), +5 volts (logical 1), the two complementary "step" functions, and the two complementary "clock" functions. The remaining four matrix positions are brought out to 5-way binding posts marked A, B, C, and D. This provides a 4 X 4 matrix (ABCD by WXYZ) that can be used for making a variety of special test connections, both internal and external to the DIGI-DYNA-CHECK.





Two power supplies are built into the checker. A regulated, highly filtered 5-volt supply capable of delivering up to 1 amp, continuously, is used to power the internal step and clock circuits (Fig. 4), and to supply V_{cc} and logic 1 level voltage to the integrated circuit under test. The regulated supply can also be used to provide power to a board containing many IC's for in-circuit tests. A filtered, but unregulated 5-volt supply provides power to the lamps and their

- PARTS LIST**
 All resistors 1/2-watt 10% unless noted
 R1—150 ohms
 R2—220 ohms
 R3, R4—100 ohms
 R5—100 ohms, Trimpot
 R6, R7, R8, R9, R10, R12, R14—100 ohms, 1/4 watt
 R11, R13, R15 thru R30—22,000 ohms, 1/4 watt
 C1—6000 μ F, 15V, electrolytic
 C2, C3—0.01 μ F, 100V
 C4—1000 μ F, 15V, electrolytic
 D1, D2, D3—1N914 or 1N4148
 D4, D5—1N4001 or similar (1A, 50V)
 Rectifier Bridge—full wave, 1A, 100V PIV
 IC1—SN-7400 (quad 2-input NAND gates)
 BP1 thru BP16—5-way binding posts, insulated
 LM1 thru LM7—4V, 50mA miniature lamp assembly
 Q1—TIP-3055
 Q2 thru Q36—2N5129
 Matrix Switch (S1 thru S20)—20-pole 10-position (Part C10-42A, Cherry Electric Co., 1650 Old Deerfield Road, Highland Park, Ill. 60035)
 S21—spst miniature toggle
 S22—spdt miniature toggle
 Miscellaneous parts:
 16-pin DIP test sockets (2)
 16-pin DIP test plug
 16-pin DIP test clip
 16-lead ribbon cable (2 1/2 feet)
 PC board
 Perf board with 0.1-inch hole spacing
 Heat sink for TIP-3055 transistor
 Case

FIG. 1 (top)—MATRIX SWITCH layout. See cover photo for 14- and 16-pin DIP settings. FIG. 3—POWER SUPPLY for 5 volts regulated to step and clock circuits and the IC under test. FIG. 7-b (right)—PARTS LAYOUT for lamp-driver board. The C-B-E terminals at right are for Q35 and Q36. Transistor pairs Q5—Q6 through Q33—Q34 are positioned from left to right.

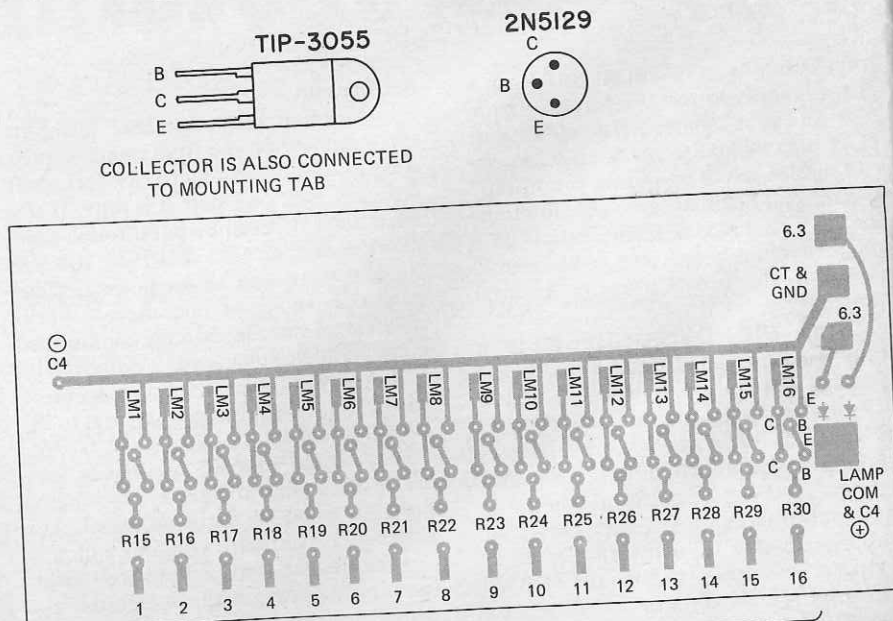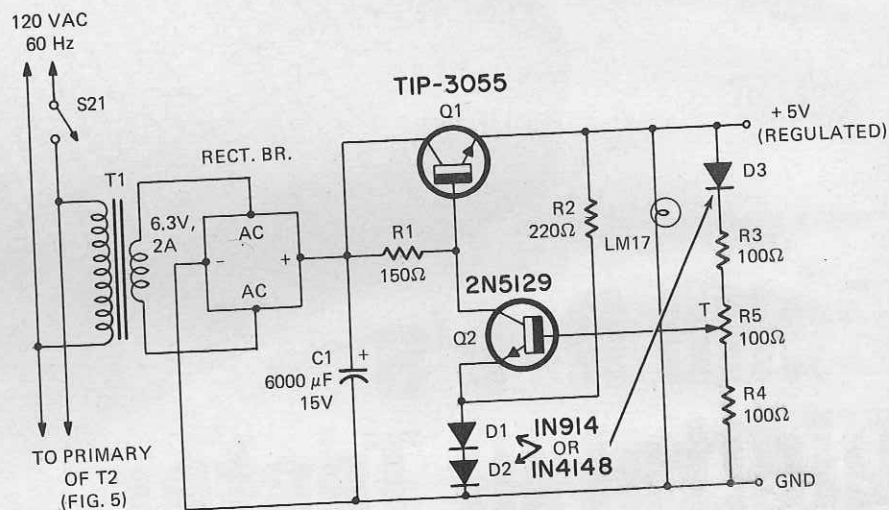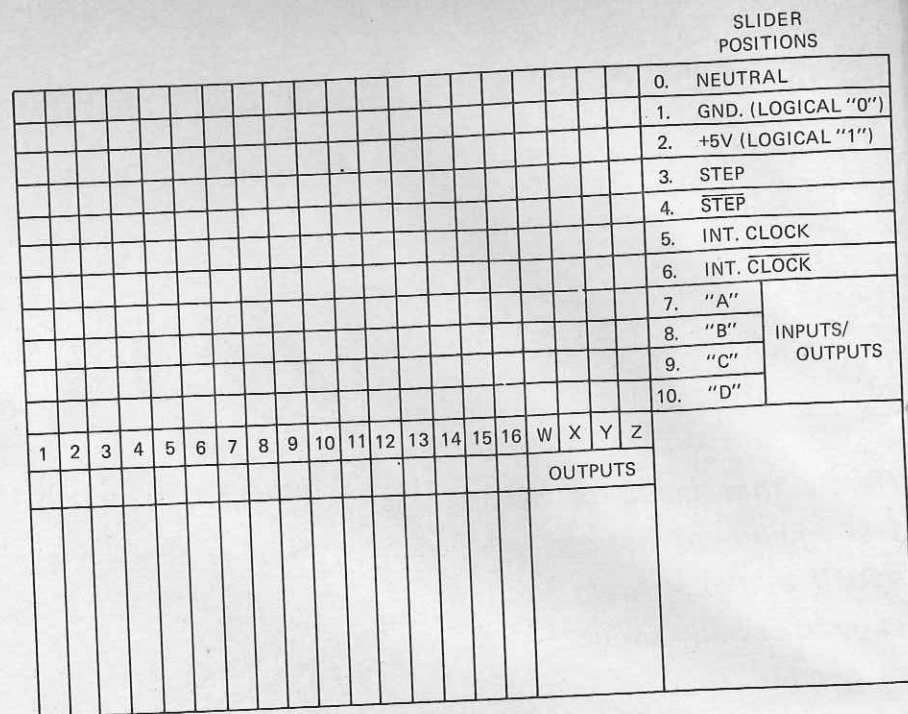

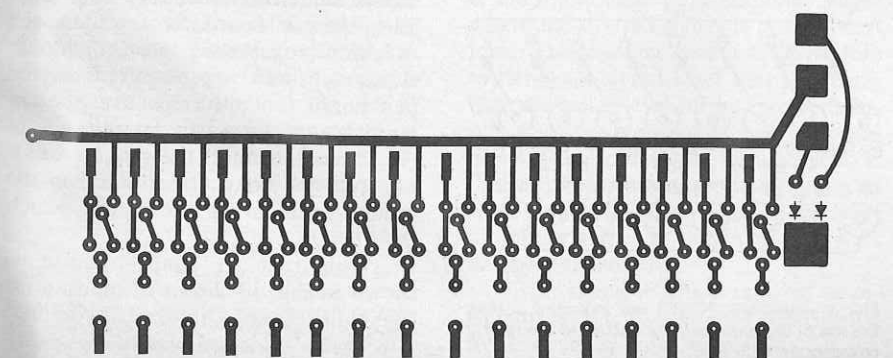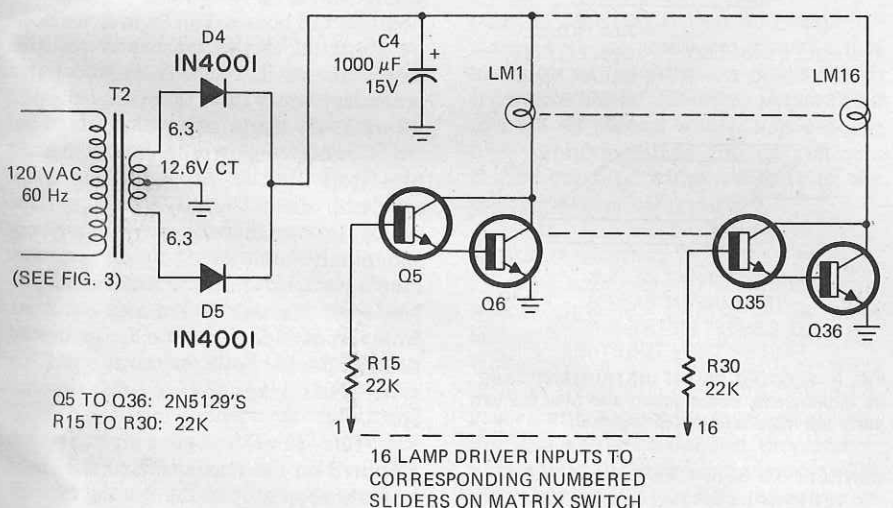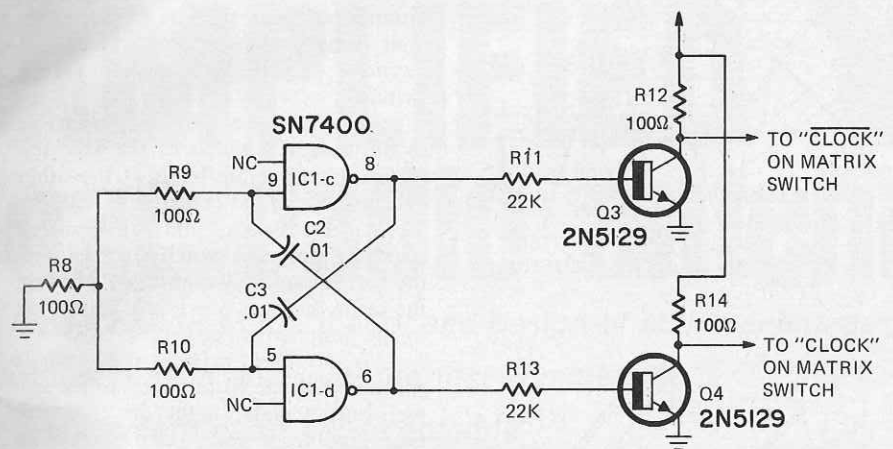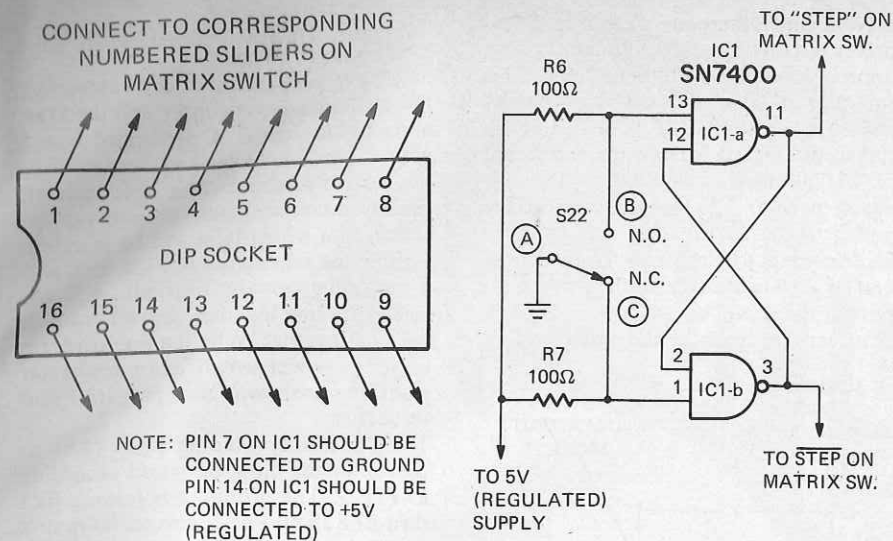THESE DRIVER INPUTS ARE CONNECTED TO THE CORRESPONDING NUMBERED SLIDERS ON THE MATRIX SWITCH.



associated driver circuits. This is shown in Fig. 5.

The stepping circuit is merely an electronic contact bounce eliminator. Solid metal switch contacts are inherently noisy and must be conditioned when used with high-speed solid-state circuits. An s.p.d.t. momentary pushbutton switch (S22 in Fig. 6) is connected to a basic NAND gate memory circuit. In the position shown, the output of IC1-a is at logical 0 level, while that of IC1-b is a logical 1. Noisy, multiple contacts with C, as the switch moves toward B, has no effect on the outputs; the gates cannot change state until gate 1-a input is at 0 level. This occurs only at the time when the switch first contacts B. The output of IC1-a then switches over to 1 and output of IC1-b switches over to 0. Once these levels have been established in the manner described, they are not affected by further "make" and "break" movements of the switch (contact bounce) at B. Complementary outputs are available from this circuit. The STEP output is initially at logical 0 and produces a fast rise transition to logical 1 and then rapidly back to 0 when the pushbutton is depressed and released. The converse is true for the STEP (called NOT STEP) output. Both of these complementary functions are useful for testing digital IC's.

The clock circuit shown in Fig. 4 is an astable multivibrator made up of the two remaining NAND gates of IC1 (an SN-7400). The values of the gate input-sinking resistors (R8, R9, and R10) were chosen to maintain the gate input levels near the logic threshold. In this way, as C2 and C3 charge and discharge, the gate input levels oscillate above and below the threshold level. This results in the gate outputs oscillating in a complementary manner. The frequency of oscillation is determined primarily by the values of C2 and C3 according to the equation

$$\text{Frequency} = \frac{1}{2(R8 + R9) \cdot C}$$

where $C = C2 = C3$ and $R9 = R10$. The component values shown in Fig. 4 result in a frequency of approximately 50 kHz. Some fine adjustment can be made by varying R8. A pair of transistor amplifiers (Q3 and Q4) is used at the complementary outputs to provide more than adequate power to drive sev-

FIG. 2 (top left)—IC SOCKET TERMINALS are wired to matrix switches on instrument panel. FIG. 4 (second from top)—INTERNAL CLOCK is a free-running multivibrator. FIG. 5 (third from top)—LAMP DRIVERS are Darlington pairs to reduce loading on IC under test. FIG. 6 (top right)—STEP SWITCH with electronics added to eliminate effects of contact bounce. FIG. 7-a (left)—FOIL PATTERN for lamp driver. Enlarge so foil is 7/8 inches across at widest point.

eral IC loads simultaneously. This is especially important where in-circuit testing is to be performed on a board that contains a multiplicity of IC's.

Sixteen lamp readouts continuously monitor the logic condition simultaneously at all pins of an IC under test. A voltage level above approximately 1.4 volts will cause a lamp to turn on, indicating a logical 1 level. Darlington-pair transistor amplifiers are employed as lamp drivers so that the IC under test cannot be overloaded by the lamp monitors. The selection of 1.4 volts as the threshold level permits the lamps to indicate properly logic levels for most RTL, DTL, TTL, and MOS digital integrated circuits. However, see the second article in this series for special precautions involving RTL IC tests. The lamp-driver circuits are shown in Fig. 5.

Mechanical construction

The author's prototype of the DIGI-DYNA-CHECK was assembled in the home-made sloping-front aluminum case shown in Fig. 8. Although case design and front-panel layout are not essential to the proper functioning of the tester, the arrangement shown offers convenience in use. Alternatively, a commercially available box of any design can be used, provided it is large enough to house all of the components.



Drill and punch the front panel to accept those components that will be mounted directly to it. These include the DIP test socket, the matrix switch, the readout lamps, pilot lamp and power switch, step button, and the 5-way binding posts. Rectangular openings can be cut out either with a nibbling tool or with a Bernz cutter. Several holes will also have to be drilled in the rear apron of the case to accommodate the line cord with its strain relief bushing, the two power transformers, and two pairs of L-brackets for the two circuit boards containing the lamp drivers, the 5-volt supplies, and the STEP and CLOCK circuits. The case can now be painted and lettering applied. Dry-transfer letters are particularly well suited for this job. It makes the checker more convenient to use if two different colors are used to number the test socket, lamp readouts, and matrix sliders to differentiate between the leads of 14-pin and 16-pin DIP integrated circuits as shown in the cover photo.

All components except the two circuit boards can now be mounted in the case.

Wiring the tester

The two circuit boards should be prepared and wired first. Then put them aside until all other wiring has been completed. Either copper-clad PC boards or perforated board construction can be used, as wiring layout is not critical. The foil pattern in Fig. 7-a corresponds to the schematic for the lamp

drivers. Since there are sixteen identical driver circuits involved, the handwiring approach would be tedious here. This foil pattern also includes the unregulated 5-volt supply of Fig. 5. The ac input to this board is from the secondary of T2, mounted at one end of the rear apron next to T1. Do not connect the power to this board until it is ready to be mounted to the case. Connect one end of a 16-lead cable to the sixteen inputs of the driver circuits on this board. Number the leads at the other end of

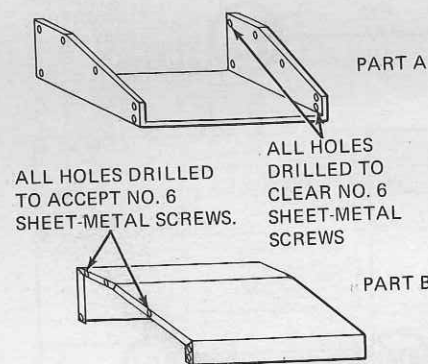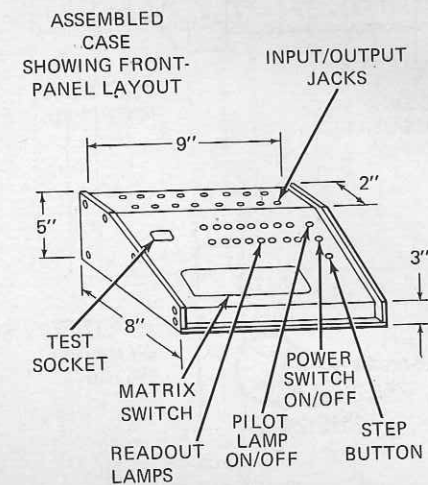

NOTE THAT PART B FITS INSIDE PART A. NO. 6 SHEET-METAL SCREWS FASTEN THEM TOGETHER.

FIG. 8—SLOPING-FRONT INSTRUMENT CASE, its dimensions, construction and how the two parts are fitted and joined together.

CONNECT TO CORRESPONDING MARKED TERMINALS ON MATRIX SWITCH

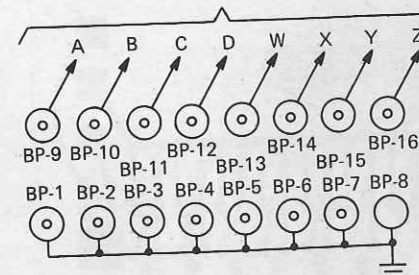


FIG. 9—BINDING POSTS are mounted across the top of the case and connected to the matrix circuitry as indicated.

this cable. They will be connected later to the matrix switch.

Next, prepare the board containing the regulated 5-volt supply and the STEP and CLOCK circuits. A perforated board with 0.1 inch hole spacings was used in the author's model. This hole spacing readily accommodates the pins on the socket into which IC-1 will be inserted. Follow the schematics in Figs. 2, 3, and 4, making certain that all +5-volt points are tied together, and all grounds are tied together. Wire the line cord, pilot lamp, power switch, and transformer primaries as shown. Now plug IC-1 into its socket.

The 5-way binding posts (BP1 to BP16) should now be wired according to Fig. 9. The ground bus joining BP1 thru BP8 should be connected to matrix switch position 1. The remaining eight binding posts can then be connected to their respective sliders (W thru Z) and positions (A thru D) on the matrix switch.

Connect one end of a 16-lead cable to the sixteen contacts of the DIP test socket. Number the leads at the other end of the cable to correspond with the socket contacts. This end will be wired later to the matrix switch together with the correspondingly numbered leads on the cable that was previously connected to the lamp driver board.

Wire the miniature lamps (mounted on the front panel) to the sixteen output pads on the driver board. One lead from each lamp should be connected to a common +5-volt tie point on the board. This board can now be mounted to the rear apron of the case with two L-brackets. Connect the secondary leads from T2 to the proper locations on the board.

Connect the two 16-conductor cables (from the DIP test socket and from the lamp driver board) to the matrix switch. Be sure that all leads go to correspondingly numbered sliders on the matrix switch. Thus, the lead from pin No. 1 on the test socket and the lead from input No. 1 on the lamp driver board should both be connected to slider No. 1 on the matrix switch, etc.

The perf-board can now be mounted on the rear apron of the case, just above and parallel to the driver board. Solder the secondary leads from T1 to the perf-board. Now, connect the +5-volt (regulated), ground, clock, clock, step, and step outputs from the perf-board to their respective position terminals on the matrix board.

Finally, connect the ground terminal from the lamp driver board to the ground terminal on the matrix switch (position 1).

Construct an adapter cable as shown in Fig. 10. This will be used for in-circuit testing of integrated circuits.

(continued on page 85)

AMPLIFIED car radio antennas

by GARY K. JOHNSON*

A description of the theory and design of active antennas with technical details of the first commercial development of an active antenna.

AT THE HIGH FREQUENCY ENGINEERING Institute of the Technical University of Munich, West Germany, experiments to integrate antennas with transistors have led to the development of a new type of transistorized receiving antenna. The director of this Institute, Prof. Dr. H. H. Meinke, prefers to describe the invention as an "Active Antenna". Active antennas have smaller dimensions and a better signal-to-noise ratio than (conventional) passive antennas of the same bandwidth. This article should give you a better understanding of how active antennas work.

The basic concept of active-antenna design is to combine an active device (transistor) with an electrically short antenna. This concept gives a completely new dimension to the design of radiating structures and makes it possible to create extremely small antennas. The sensitivity limit of a receiving system depends on the noise produced in the first amplifying stage as well as how the antenna system, including lead-in and transformation cir-

cuits, is matched to the first amplifier stage. With an active antenna the first transistor in the receiving system is integrated with the antenna's elements. In this way a natural match between the first amplifying stage and the antenna can be obtained without disturbing the passive transmission parts.

Noise matching

The sensitivity of a receiving system is ultimately limited by its noise temperature (signal-to-noise ratio). Antenna gain, a figure of merit, is not a decisive factor in a receiving system because, with low noise level, amplification can easily be done in the receiver without any natural limitations. The most crucial point in a receiving system is the input stage (first amplifier stage) where the desired signal is at its lowest level. The antenna system must be able to deliver a signal level that is greater than the noise level of the receiver's input stage as well as its own internal noise. Therefore, signal-to-noise ratio is the main factor limiting the reception of weak signals and consequently the most important factor to be considered with an antenna system.

The signal-to-noise ratio of a receiving system is primarily determined by three main noise sources:


- 1. Antenna noise:** The passive antenna receives noise out of the surrounding space. This external atmospheric noise can be expressed as a noise temperature T_A .
- 2. Inter-network noise:** This is the network between the passive antenna and the input terminals of the first amplifying stage. This network has two effects:

- a. The signal is decreased by attenuation since resistance in transmission lines and matching networks is unavoidable.
- b. This resistance in transmission lines and the matching circuits is an additional source of noise.

- 3. Amplifier or transistor noise:** The first amplifier stage creates an internally generated noise. Transistor noise can be expressed as a noise temperature T_T .


The total system noise temperature would be simple to define if the only noise sources were in the receiver. Since there are three main sources of noise in a receiving system, the total noise is described by a total system noise temperature (T_S) in relation to the exit terminal of the passive antenna.

To reduce noise and increase the

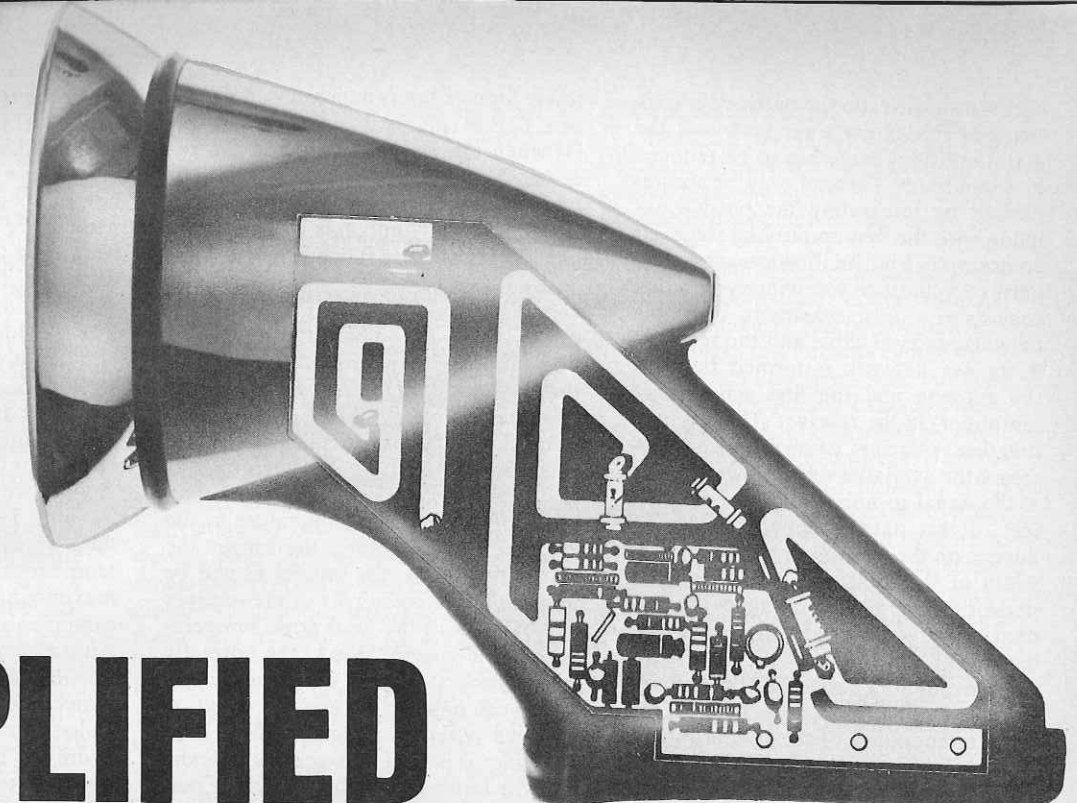

IT'S EASY TO ASSEMBLE A SCHOBER ORGAN!

CONSOLETTA II ORGAN
*\$1040

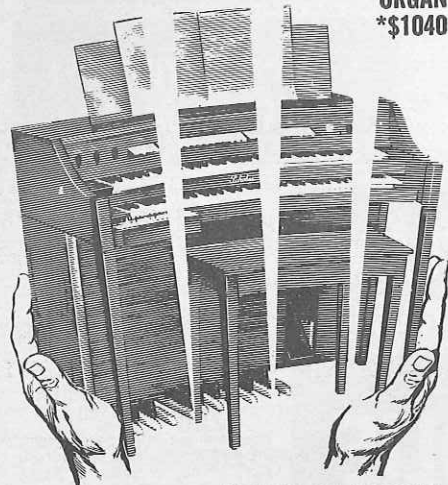

*Includes easy to assemble walnut console kit. Amplifier, speaker system, optional accessories extra.

You couldn't touch an organ like this in a store for less than \$1800—and there never has been an organ of the Console II's graceful small size with 22 such pipelike, versatile voices, five-octave big-organ keyboards, and 17 pedals! It sings and schmaltzes for standards, pops, old-time favorites, speaks with authority for hymns and the lighter classics, all with a range of variety and satisfying authenticity you've never found before in an instrument under church or theatre size. If you've dreamed of an organ of your own, to make your own beautiful music, even if your home or budget is limited, you'll get more joy from a Schober Console II than any other "home size" organ—kit or no kit.

You can learn to play it. And you can build it, from Schober Kits, world famous for ease of assembly without the slightest knowledge of electronics or music, for design and parts quality from the ground up, and—above all—for the highest praise from musicians everywhere.

Send right now for the full-color Schober catalog, containing specifications of all five Schober Organ models, beginning at \$499.50. No charge, no obligation. If you like music, you owe yourself a Schober Organ!

new lit

All booklets, catalogs, charts, data sheets and other literature listed here with a Reader Service number are free for the asking. Turn to the Reader Service card on page 111 and circle the numbers of the items you want. Then mail the postage-paid card.

SCIENCE, OPTICS & ELECTRONICS CATALOG, No. 722, lists 4,000 unusual bargains for hobbyists, experimenters, science and crafts enthusiasts, students, gardeners and workshop buffs. Everything from air pollution testing equipment to zoom binoculars, illustrated with charts and diagrams, including tools, games, puzzles, rockets, microscopes, telescopes, photographic attachments, black-light equipment, lighting products, and kits for youngsters to use for science-fair projects.—**Edmund Scientific Co.**, 380 Edscrop Bldg., Barrington, N.J. 08007.
Circle 45 on reader service card

OSCILLOSCOPES CATALOG, No. 5, 7/71, a 14-page test equipment booklet presents the line of oscilloscopes and a curve tracer. These scopes, with built-in TV field and line triggering, find special application in TV service. Single-trace, dual-trace, and dual-beam scopes are shown. Fully illustrated. List of Field Engineering offices where technical assistance may be obtained.—**Tektronix, Inc.**, P.O. Box 500, Beaverton, Ore. 97005.
Circle 46 on reader service card

TECHNIQUES FOR REPAIRING ELECTRONIC ASSEMBLIES, Bulletin No. 700-005. Most recent booklet in the series concerns "Notations on Solder Joint Removal, Conformal Coating Removal, Component Lead Forming". Highlighted are applications and illustrated procedures for the removal of specific types of solder joints and conformal coatings. This 24-page booklet is fully illustrated with photos and diagrams. Request on company letterhead.—**Pace Inc.**, 9329 Fraser St., Silver Spring, Md. 20910.
Circle 47 on reader service card

REPLACEMENT COMPONENTS CATALOG, No. 100, 1972. This fully illustrated 68-page catalog of replacement components for radio and TV includes resistors, fusing devices, circuit breakers, sockets, convergence controls, service accessories, electronic chemicals, audio cables, adapters for hi-fi and cassette tape recorders, battery holders and prototype kit components. Available free to qualified distributors, service technicians and experimenters.—**Workman Electronic Products, Inc.**, Box 3828, Sarasota, Fla. 33578.
Circle 48 on reader service card

Write direct to the manufacturers for information on item listed below:

REPLACEMENT PARTS CATALOG, four pages

NEW for '72



ENGINEERS TOOL KIT KE6

A complete service kit — for Security Installers, Data Terminal Repair, Business Machines, and Coin Operated Equipment Service — 10 different kits to choose from — 10 pc to 160 pcs kit — Custom Kits available to your specs from our inventory of 5,000 plus items —

184 PAGE
FREE
1972 CATALOG

TECHNI-TOOL, INC.
1216 ARCH ST., PHILA., PENNA.
ZIP CODE: 19107-(215) LO 8-4487

Circle 66 on reader service card

on solid-state replacement and renewal parts for color TV receivers including SOLID-TUBES, cartridges and multipliers. Lists solid state SOLID-TUBE high voltage rectifiers, focus rectifiers and damper diodes, silicon and selenium focus cartridges, diagrams showing dimensional drawings and socket connections for SOLID-TUBE solid state replacements of vacuum tubes with maximum ratings for pulse rectifier service.—**Electronic Devices, Inc. (EDI)**, 21 Gray Oaks Ave., Yonkers, N.Y. 10710.

ELECTRONICS CATALOG, 1971. 10,000 items described in this 64-page general catalog. Included are batteries, capacitors, controls, resistors, semiconductors, switches and timers plus new security systems, cassette recorders and cassette recording tapes. Available from authorized distributors.—**Mallory Distributor Products Co., Div. P. R. Mallory & Co.**, 101 South Parker, Indianapolis, Ind. 46201. R-E

IC TESTER (continued from page 36)

Testing

Plug the Digi-Dyna-Check into a 120-volt, 60-Hz supply and turn on the power switch. Adjust R5 on the perfboard to obtain exactly 5 volts at the output of the regulated power supply. This should be measured with a

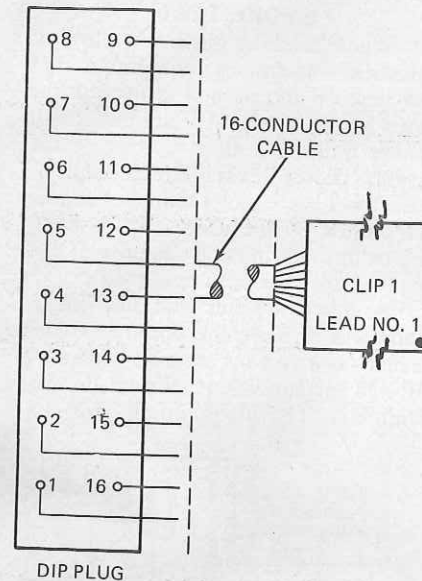


FIG. 10—ADAPTER CABLE consists of 16-pin plug and clamp and is used for in-circuit testing of DIP-type integrated circuits.

VTVM, an FET input voltmeter, or other similar high input-impedance device. With all matrix sliders in the neutral position, only the pilot lamp should be on. Move sliders 1 thru 20 to position 1 (ground). None of the lamps should light. All IC test socket pins and binding posts W thru Z should be shorted together and at ground level. (Check with an ohmmeter). Move all sliders to position 2 (+5V). All sixteen readouts should be on. All DIP test socket pins and binding posts W thru Z should be at +5-volts. Move all sliders to position 3 (Step). All socket pins should be at logical 0 together with binding posts W thru Z. Depressing the STEP button should cause all lamps to turn on and bring all socket pins and binding posts W thru Z to logical 1. Releasing the STEP button should return everything to their initial states. Move all sliders to position 4 (Step). Everything should behave as the inverse of that described for position 3. Move all sliders to position 5 (Clock). All lamps should glow at half brilliance due to the 50% duty cycle of the square wave clock output. A 50 kHz square wave should be present at all DIP test socket pins and at binding posts W thru Z. With all sliders at position 6 (Clock) you should see the inverse of that observed for position 5. Wave forms in positions 5 and 6 can be observed with a scope at binding posts W thru Z. Moving any of the

sliders to any of the four positions 7 thru 10 should connect their corresponding circuits to binding posts A thru D, respectively.

If everything described here checks out A-OK, you're ready to use your Digi-Dyna-Check to check IC's. R-E

BUILD A SOLID-STATE LASER


Our June cover feature presents complete construction details of a solid-state laser. It's both easy and inexpensive to build. If you've been waiting for a low-cost low-power "safe" laser to experiment with you won't want to miss the June issue of **Radio-Electronics**.

People In Trouble
Need Your
UNITED GIFT



If you don't do it,
It won't get done

TV TUNER SERVICE

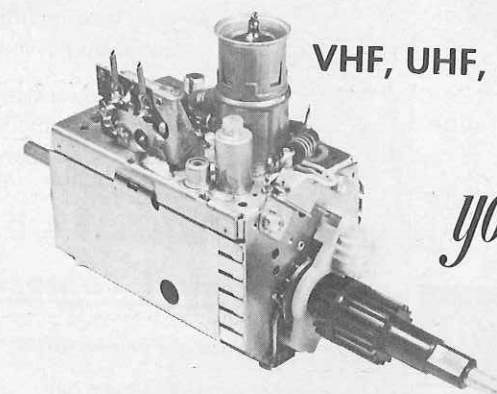

VHF, UHF, FM or IF-Subchassis...
... All Makes

you get...

Fast 8 hr. Service!

1 YEAR GUARANTEE



FIRST TO OFFER 365-DAY GUARANTEE!
COLOR—BLACK & WHITE—TRANSISTOR TUNERS—
ALL MAKES
GUARANTEED COLOR ALIGNMENT—
NO ADDITIONAL CHARGE

You owe it to yourself

to try P.T.S. We are the fastest growing, oldest and now the largest tuner service company in the world. Here is what you get.

1. Fastest Service—8 hr.—in and out the same day. Overnight transit to one of our six plants, for parts, tuners or IF-modules.
2. All tuners cleaned inside and out, repaired, realigned and air tested.
3. On IF-modules all stages checked, all traps set with high calibre test equipment.
4. Fine Quality! Your customers are satisfied and you are not bothered with returning your units for rework!
5. Lower Cost! Up to \$5.50 less than other tuner companies!
6. Friendly, helpful personalized service!

LIKE TO DO IT YOURSELF?

PTS makes all tuner parts available to you.

Send one dollar (redeemable) for our TUNER REPLACEMENT GUIDE AND PARTS CATALOG

- 60 pages of top information
- Blow-up of all tuners
- Largest exact tuner replacement guide
- Antenna Coil Replacement Guide
- Multi-fit Replacement Tuner Shaft Guide

We offer you finer, faster...

Precision
Tuner Service

VHF-UHF-FM \$9.95
UV-COMBO \$16.95
IF-MODULE \$12.50
Major Parts charged at Net Price

CUSTOMIZED REPLACEMENTS AVAILABLE FOR \$12.95 UP (NEW OR REBUILT)

For fastest service, send faulty unit with tubes, shields and all broken parts to:

PTS ELECTRONICS, INC.

HOME OFFICE—
SOUTHEAST—
WEST COAST—
EAST—
SOUTHWEST—
MOUNTAIN—

P.O. Box 272—Bloomington, Ind. 47401
P.O. Box 6771—Jacksonville, Fla. 32205
P.O. Box 41354—Sacramento, Calif. 95841
P.O. Box 3189—Springfield, Mass. 01103
P.O. Box 7332—Longview, Tex. 75601
P.O. Box 4145—Denver, Colo. 80204

Tel. 812/824-9331
Tel. 904/389-9952
Tel. 916/482-6220
Tel. 413/734-2737
Tel. 214/753-4334
Tel. 303/244-2818

Circle 67 on reader service card

MAY 1972 • RADIO-ELECTRONICS 85

RE-102

The Schober Organ Corp., Dept.
43 West 61st Street, New York, N.Y. 10023

Please send me Schober Organ Catalog.

Enclosed please find \$1.00 for 12-inch L.P. record of Schober Organ music.

NAME _____

ADDRESS _____

CITY _____ STATE _____ ZIP _____

Circle 65 on reader service card