
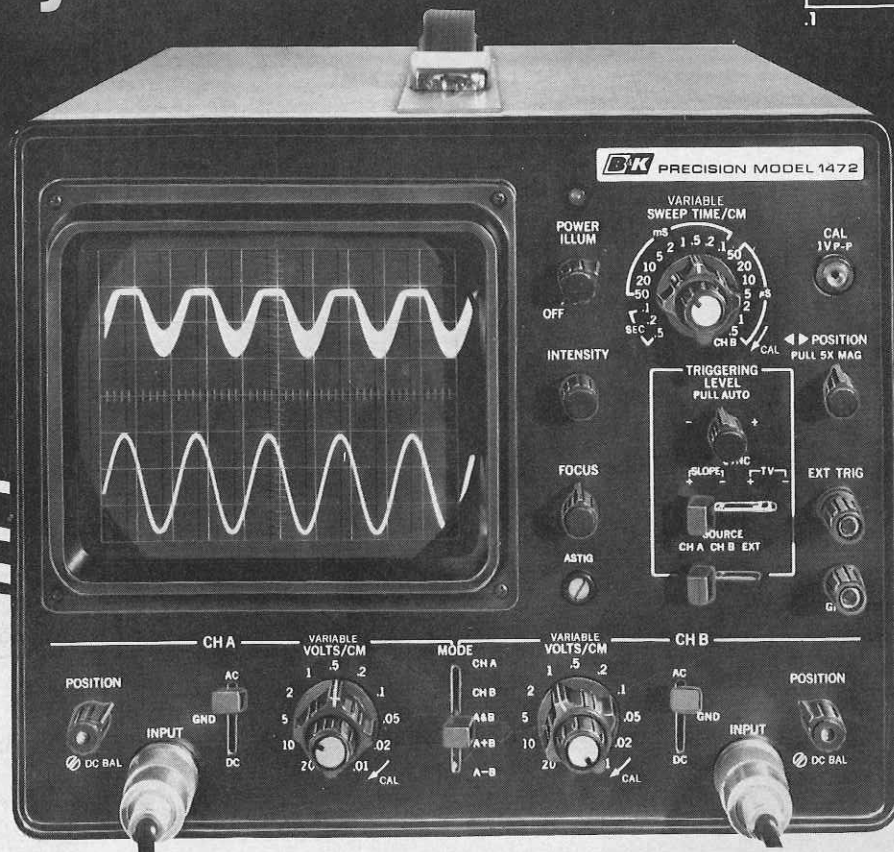


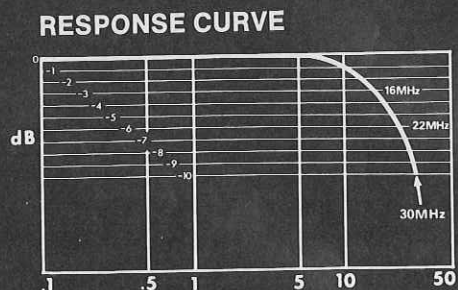Our reliable  
15MHz scope  
syncs to 30MHz



**B&K PRECISION**  
Model 1472 Dual Trace  
Oscilloscope: 27MHz modu-  
lated carrier and original  
audio displayed... \$599.00

Model 1472 Dual Trace Scope has reliable automatic sync and plenty of deflection for waveform analysis at frequencies far beyond its nominal range. Look at its actual, smooth roll-off curve and you can see how you can do an expensive scope's job with our far less costly but equally reliable, easy-to-use counterpart. Model 1472 lengthens the B&K-Precision complete line of 2 to 10MHz bandwidth scopes—a line of scopes that now outsells every other 10 to 15MHz scope because our users have discovered our reliability, performance and instant delivery from our distributors.

Model 1472 has 19 calibrated sweeps—.5 $\mu$ SEC/cm to .5SEC/cm and sweep to .1 $\mu$ SEC/cm with 5x and to 1.5SEC/cm with uncalibrated vernier. Deflection factor is 0.01V/cm to 20V/cm  $\pm$ 5% in 11 ranges plus fine adjustment. Regulation maintains calibration accuracies over 105-130VAC range. Rise time is 24nSEC, fast enough to check most digital logic circuitry, including CMOS. Automatic triggering is

obtained on waveforms with as little as 1cm deflection. Dual trace display has algebraic addition and subtraction and differential input capability. Mode automatically shifts between CHOP and ALTERNATE as you change sweep time, speeding set-up. Extremely flat in-band response is particularly useful for demanding applications like adjusting color video to close tolerances in TV broadcast studios.

Front panel X-Y operation uses matched vertical amplifiers, preserving full calibration accuracy for both amplitude and phase. The intensity modulation input (Z axis) is available for time or frequency markers. Bright blue P31 phosphor and variable illuminated graticule make any waveform easy to see.

**In Stock For Free Trial**  
Model 1472 or any B&K-Precision oscilloscope can be obtained from your local distributor for a free trial. You'll find the scope you need in stock today. Write for detailed specifications.

**B&K PRECISION**  
PRODUCTS OF DYNASCAN  
1801 W. Belle Plaine Avenue Chicago, IL 60613  
Circle 11 on reader service card

# IC Doorbell Plays Your Song

You can program your own tune into this device and connect it to your doorbell. It features a PROM with a 32-note capacity


by RALPH E. COUSINO

MUSIC CAN RECALL A PLEASANT MEMORY ESPECIALLY if it's your favorite melody. This article describes an electronic music box that you can build and program to play your favorite tune. Use it in place of your doorbell or as a wakeup alarm on your digital clock. The electronic music box can be used for any audible signalling application. It provides a full range of two octaves for a total of 24 notes including tremolo. Momentarily closing the start circuit, the unit plays its programmed tune, through a maximum of 32 notes, one at a time, with a hold of up to 4 beats-per-note. It automatically shuts off at the end.
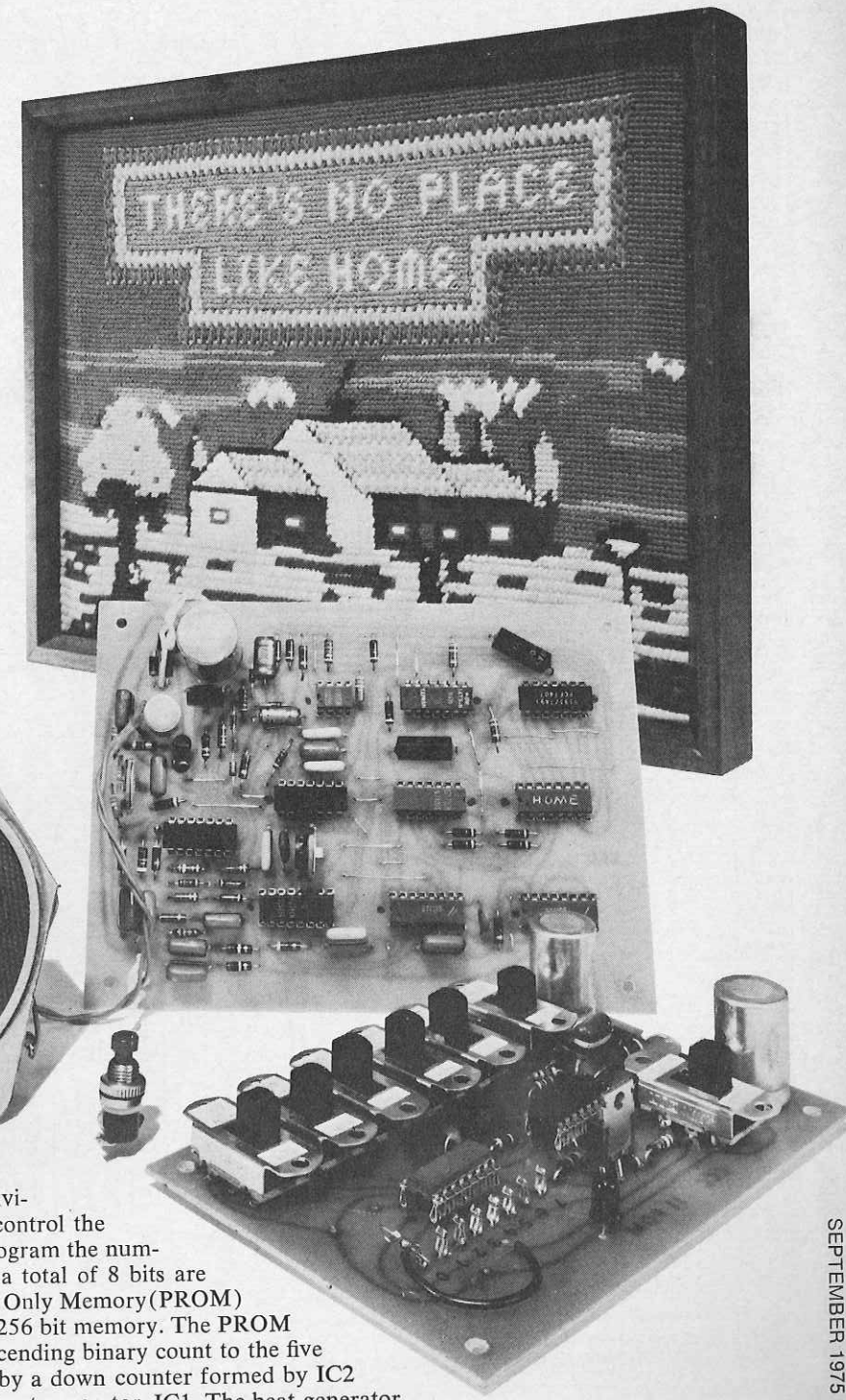
## Circuit operation

A complete schematic of the electronic music box is in Fig. 1. The twelve notes for one full octave are generated by frequency division of a master oscillator formed by IC10-b. This 21,560-Hz master oscillator is frequency modulated for tremolo by a phase shift oscillator using operational amplifier IC5-d. Frequency division of the master oscillator output is done by cascaded programmable counters IC8 and IC9. After division by IC8 and IC9, the narrow output pulse is fed to IC10-a to form a wider pulse. This pulse is connected to the clock input of J-K flip-flop IC3-b that divides the input frequency by two, if the clear input is high, thereby generating the next lower octave. The tone can be muted by driving the clear input of IC10-a low. This is done by making the four inputs to NAND gate IC7-b high.

Programming IC8 and IC9 for frequency division requires 5 bits. Another bit is required to control the frequency divider. Two more bits are used to program the number of beats a note should be held. Therefore, a total of 8 bits are required for each note. The Programmable Read Only Memory (PROM) IC6 provides an 8-bit by 32-word memory or a 256 bit memory. The PROM is stepped through each word by applying an ascending binary count to the five address lines. The ascending count is delivered by a down counter formed by IC2 and IC3-a. The address counter is clocked by a beat generator, IC1. The beat-generator



**PARTS LIST**

All resistors are 1/4-watt, 10%, unless noted

- R1, R12—6.8 megohms, 5%
- R2, R27, R28—100,000 ohms
- R3, R6, R16, R18, R21, R30, R31, R32, R33, R34, R35, R36, R37, R39—1,000 ohms
- R4, R5—330 ohms
- R7, R19, R20—10,000 ohms, 5%
- R8—500,000 ohms trimmer potentiometer
- R9—27,000 ohms
- R10, R11, R38—470,000 ohms, 5%
- R13—820,000 ohms, 5%
- R14, R24—4.7 megohms, 5%
- R15, R25—2.7 megohms, 5%
- R17—3.9 megohms, 5%
- R22—4,700 ohms
- R23—50,000 ohms trimmer potentiometer
- R26—2.2 megohms
- R29—33,000 ohms, 5%
- C1, C3, C11, C18—.047  $\mu$ F polyester film
- C2, C6, C7, C10, C13, C14, C15, C20—.1  $\mu$ F polyester film
- C4, C5—2  $\mu$ F, 10 volt electrolytic
- C8—220  $\mu$ F, 10 volt electrolytic

- C9—300 pF ceramic
- C12—.0047  $\mu$ F polyester film
- C16—2,200  $\mu$ F, 16 volt electrolytic
- C17, C19—20  $\mu$ F, 10 volt electrolytic
- IC1—555 timer
- IC2—7493 TTL
- IC3—7473 TTL
- IC4—7405 TTL
- IC5—3900 linear quad amplifier
- IC6—8223 PROM (un-programmed)
- IC7—7420 TTL
- IC8, IC9—74193 TTL
- IC10—74123 TTL
- D1, D2, D3, D4—1N4148
- D5—1N751A
- D6, D7, D8, D9—1N4002
- Q1—2N3394
- Q2—2N3638
- Q3—2N5296
- T1—117-volt primary, 6.3-volt @ 0.6A secondary
- F1—1/4-amp fuse

The following parts may be ordered from Cousino Circuit Company, 3313 Brace Street, Burbank, CA 91504

- #K11-EMB—Kit of all items in Electronic Music Box parts list, except miscellaneous items, fuse and transformer. Includes PC board and un-programmed PROM. \$36.95 postpaid within USA.
- #KHS11-EMB—Same as #K11-EMB except PROM is pre-programmed with "Home Sweet Home" melody. \$39.95 postpaid within USA.
- #11-EMB—Drilled glass epoxy printed circuit board for Electronic Music Box. \$6.95 postpaid within USA.
- #K11-PGM—Kit of all parts in parts list for PROM Programmer except miscellaneous items. Includes printed circuit board and programming data for several melodies. \$21.95 postpaid within USA.
- #11-PGM—Drilled glass epoxy printed circuit board for PROM Programmer. \$5.95 postpaid within USA. California residents add sales tax.

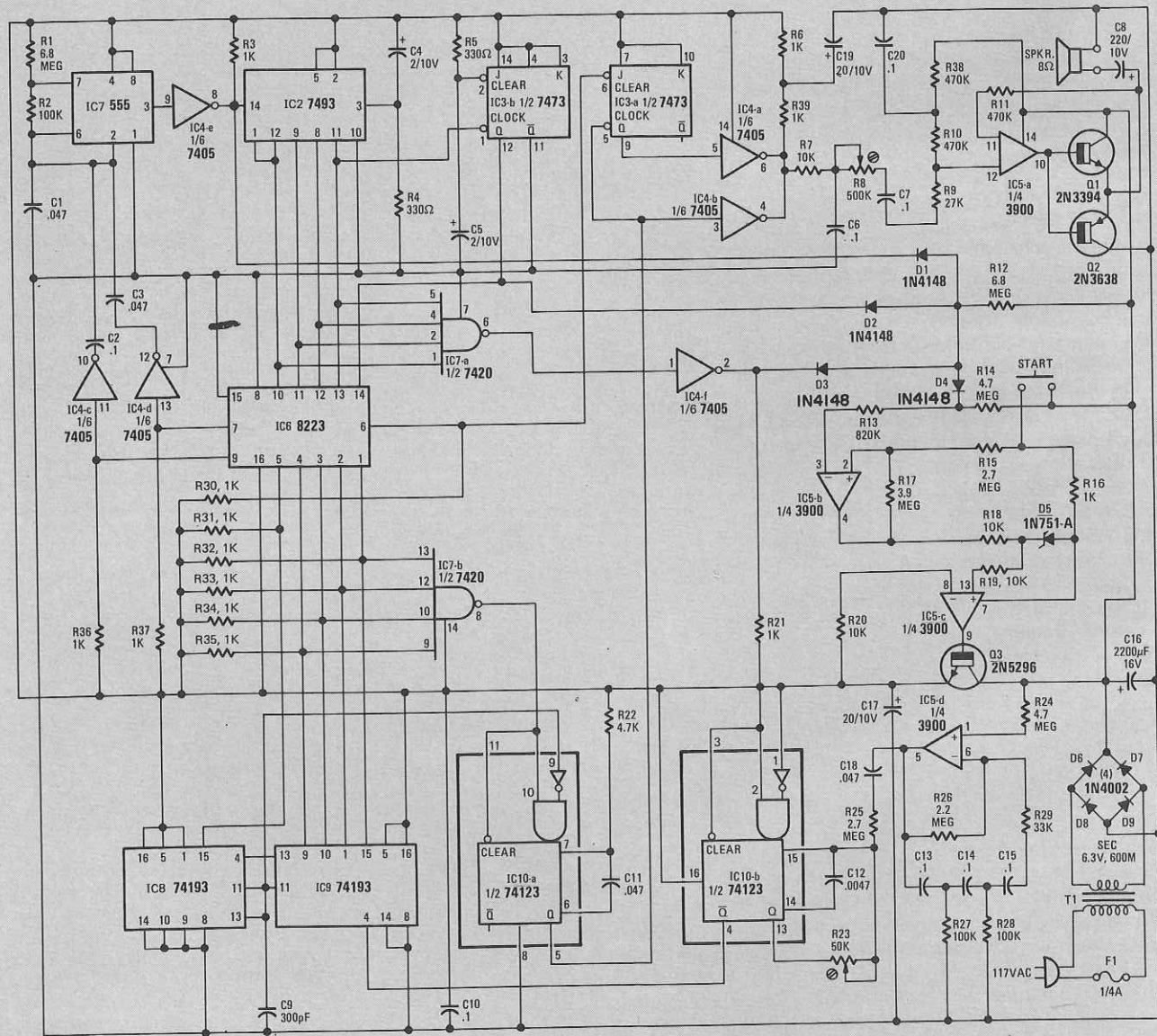


FIG. 1—ELECTRONIC MUSIC BOX schematic diagram.


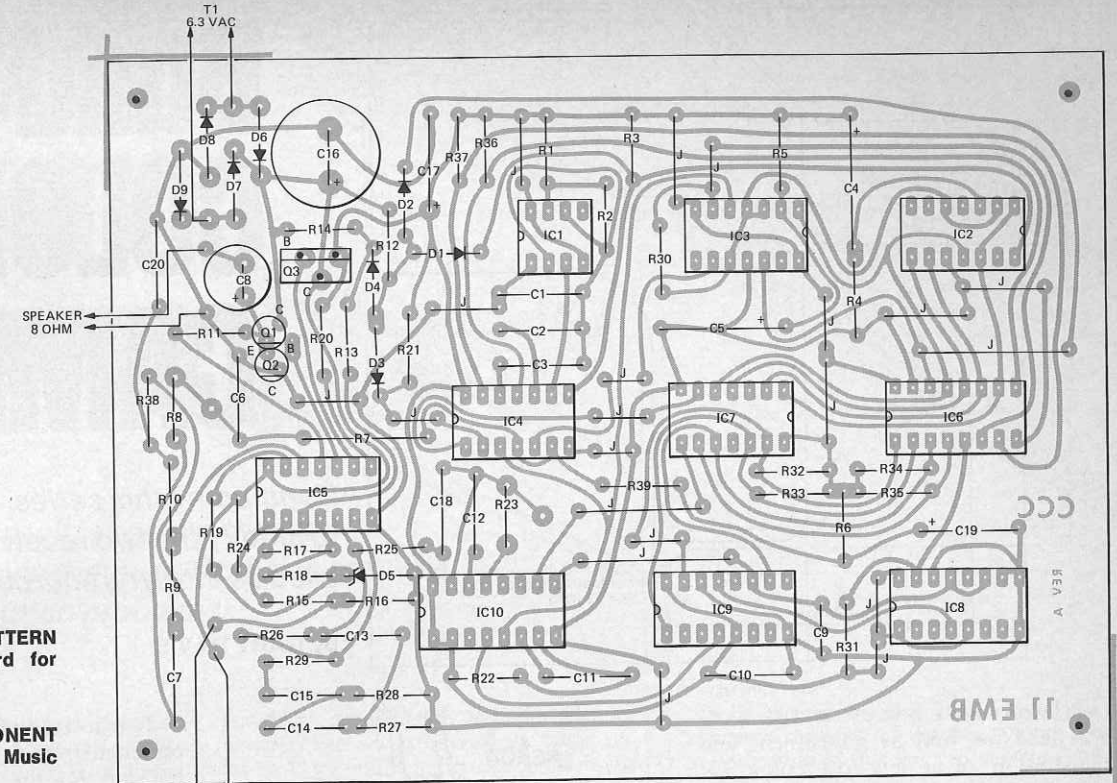


FIG. 2 (below)—FOIL PATTERN of printed circuit board for Electronic Music Box.

FIG. 3 (right)—COMPONENT LAYOUT for Electronic Music Box.

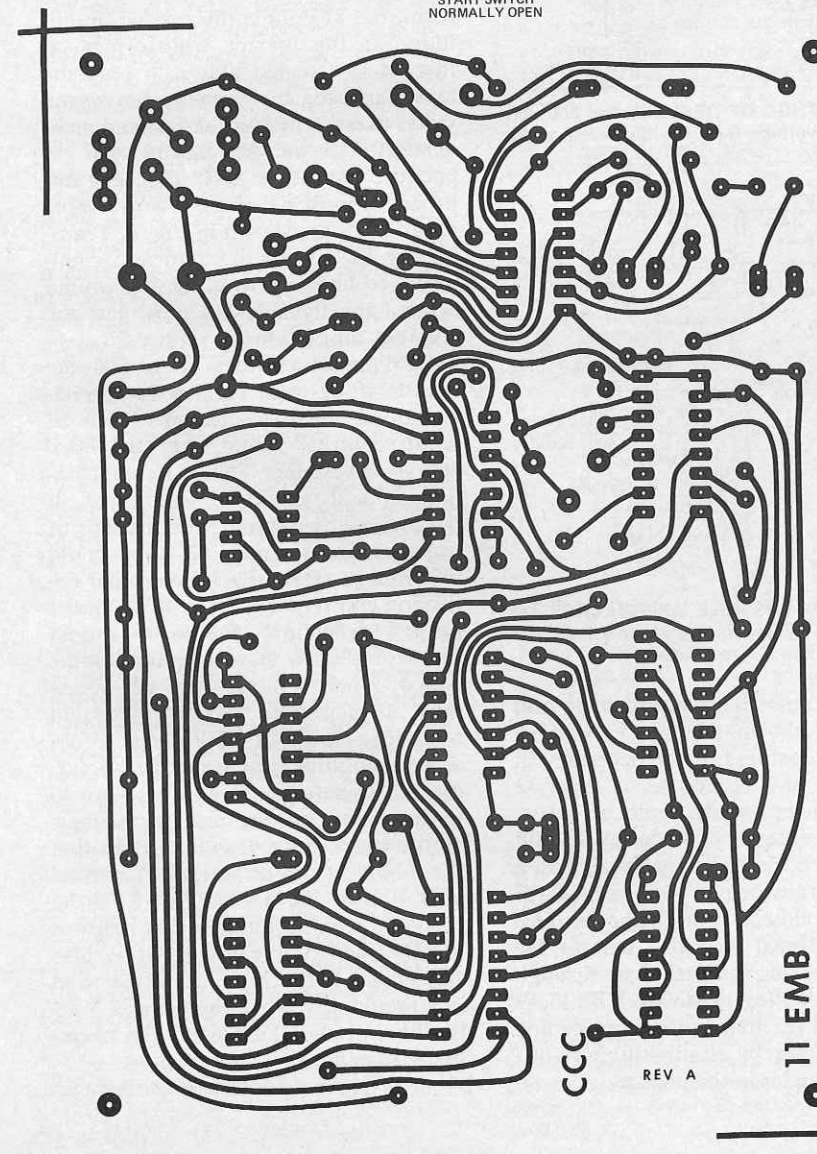

rate is controlled by capacitors C1, C2 and C3. These capacitors are grounded by IC4-c and IC4-d depending upon PROM programming. This controls the duration of time each note is held.

Inverters IC4-a and IC4-b provide an output pulse whether frequency divider IC3-b is enabled or not. This pulse is delayed by R7 and C6, and fed to operational amplifier IC5-a through a volume control R8. This amplifier drives a complimentary transistor pair that is coupled to the output speaker by C8.

Voltage for all IC's is supplied by the regulator consisting of transistor Q3 and operational amplifier IC5-c. The operational amplifiers are connected to the unregulated input voltage and are therefore always on. Operational amplifier IC5-b is connected as an R-S flip-flop. Closing the start circuit drives the output of IC5-b high turning on the voltage regulator supplying 5 volts to the IC's. When the program is finished, all address lines of the PROM go high. The address lines on IC7-a with inverter IC4-f reverse bias diode D3. This along with D2 reverse biased plus the positive going beat pulse on diode D1, causes the IC5-b flip-flop to reset, shutting the unit off.

**Construction**

In view of the circuit complexity, printed-circuit boards are a must. The PC board layout is shown in Fig. 2 and component location is detailed in Fig. 3. Insert and solder components and jumpers as shown using care to observe the polarities of diodes and capacitors.

(continued on page 104)

