

NEW DBX SYSTEM — PLL FOR CB

\$1.00 ■ APR. 1977

# Radio-Electronics




THE MAGAZINE FOR NEW IDEAS IN ELECTRONICS

build this  
**2650 COMPUTER**  
on one board

experiment with  
**FUNCTION GENERATOR**  
new Exar IC

for your phone :  
**BUILD TELESWITCH**  
and turn things on

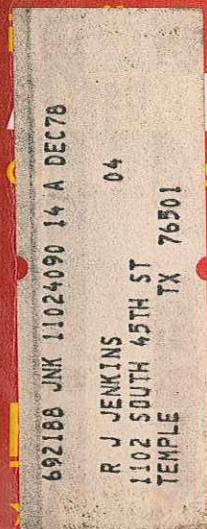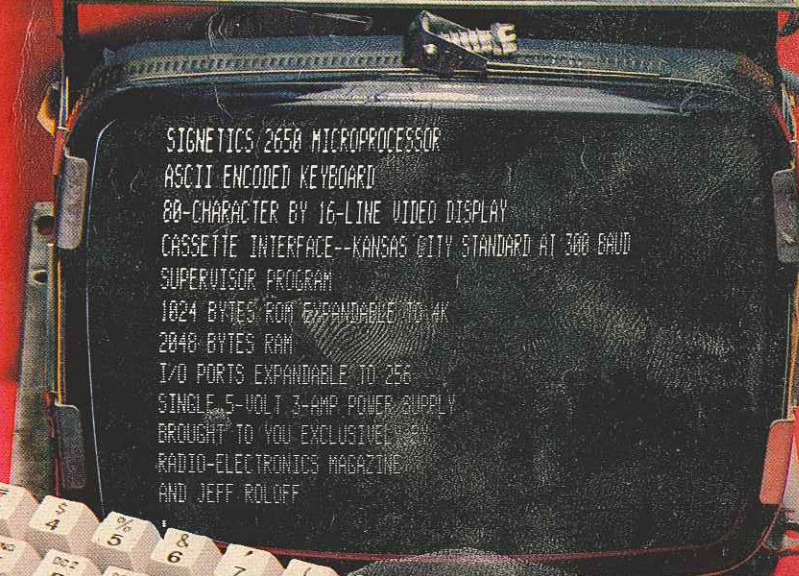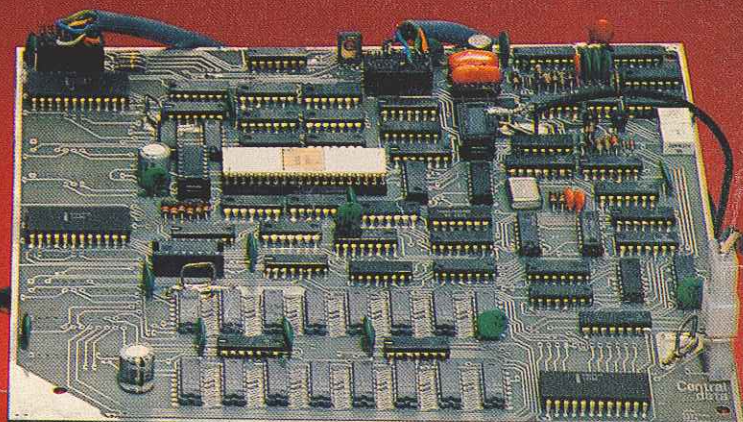IC data sheet :  
**RETICON SAD-1024**  
bucket-brigade



IA TOWERS

sy

er Korner

- ★ Jack Darr's Service Clinic
- ★ Lab-Tested Hi-Fi Reports
- Yamaha CT-800 Tuner & Kenwood KR7600 Receiver
- ★ State-Of-Solid-State ★ Equipment Reports ★ Reader Questions

GERNSBACK PUBLICATION

# C & S MARKETING ASSOCIATES

You will never need crystals again with the Bearcat 101 Scanner  
**BEARCAT 101 SPECIFICATIONS**




FREQUENCY RANGE	
LOW BAND	30-50MHz
HIGH BAND	148-174MHz
UHF BAND	450-470MHz
"T" BAND	470-512MHz
HAM BAND	146-148MHz

**MAXIMUM USABLE FREQUENCY RANGE**  
 All of the above plus UHF frequencies from 416 to 450MHz.

SIZE	9" W x 3 3/8" H x 7 1/4" D
WEIGHT	6 lbs. 4 oz.
POWER REQUIREMENTS	117 v ac, 30 w
AUDIO OUTPUT	3W RMS
ANTENNA	Telescoping (supplied)
SENSITIVITY	.6uv for 20 db s/n ratio on L and H Bands. U Bands slightly less.
SELECTIVITY	Better than -60db @ 25kc
SCAN RATE	20 channels per second
JACKS	External antenna and speaker
FRONT PANEL FEATURES	<ul style="list-style-type: none"> <li>Squelch Control</li> <li>Volume Off/On Control</li> <li>Combined Man/Scan Channel Select Switches</li> <li>Light Emitting Diode Channel Indicators</li> <li>Channel Lock-Out Program Switches</li> <li>Program Ready Switch</li> <li>Program Enter Switch</li> </ul>

**SUGGESTED LIST PRICE**  
 \$349.95

**OUR PRICE**  
 \$309.95

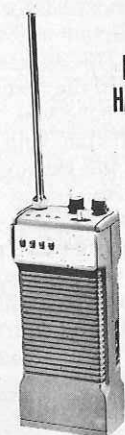

**BEARCAT HAND-HELD**

**SUGGESTED RETAIL PRICE**  
 \$129.00 WITHOUT CRYSTALS

**OUR PRICE**  
 \$129.00 WITH CRYSTALS OF YOUR CHOICE

SPECIFICATIONS	
Size:	2-3/4"W x 6-5/16"H x 1-1/2"D
Weight:	12 ozs.
Power Requirements:	6 Vdc (4 penlight batteries) 5 Vdc (4 Nickel Cadmium batteries) 6 Vdc external power
Audio Output:	0.3W maximum
Antenna:	Telescoping antenna and wire antenna (both supplied) Optional rubber antenna can also be used.
Sensitivity:	0.6 microvolt for 20 dB quieting, typical
Channels:	Up to 4 crystal-controlled channels may be scanned automatically or selected individually or any combination.
Frequency Range:	Low band 30-50 MHz; total spread 8 MHz High band 150-174 MHz; total spread 10 MHz
Scan Rate:	Approximately 8 channels per second
Crystals:	Miniature plug-in type A-135 for easy user installation
Accessories supplied:	Telescoping antenna for both bands, convenient wire antenna
Panel Features:	Squelch control/Volume on-off control/Combined Automatic-Manual-Channel Select switch/4 Channel switches/4 L.E.D. channel indicators/Antenna jack/External antenna jack/Forward facing 2" speaker

Certified under FCC Regulations, Part #15

# COMPUTER PROJECT

## Build 2650-Based Microcomputer System



Part I. Built on a single printed-circuit board, this 2650 microcomputer contains a video and cassette tape interface and resident supervisor program. Add a keyboard, video monitor, cassette tape recorder and power supply for a complete working system

### JEFF ROLOFF

AN EASY-TO-USE COMPUTER SYSTEM MUST have essentially four major sections. There is, of course, the actual processing section that usually (at least for small users) contains a microprocessor IC. There must also be input and output sections so that the processor can communicate with the outside world. The last section that is essential for a computer's operation is the memory. This is used to store programs and data, and it can be either a memory that needs to be accessed very quickly when running a program or a memory used to store information for long periods of time, such as cassette tape.

The 2650 computer project presented here has all of the above circuits mounted on a single printed-circuit board. In addition, there is a versatile supervisor program that allows you to easily create your own programs. The heart of the unit is the Signetics 2650 microprocessor. Basically, it is a simple to use microprocessor with a powerful instruction set. The input device can be any ASCII-encoded keyboard, which simply hooks to an input port of the computer. The output device is a high quality 80-character by 16-line video display generator which is fully controlled by the processor. There are also parallel input and output ports (one each) to allow you to communicate with any other peripheral device, such as a line printer or a floppy disc. The

### SPECIFICATIONS

#### DISPLAY GENERATOR

**Display Format:** 16 lines of 80 characters. User programmable character generator selected by setting bit 6 of the stored data to logic-1 level. Bit 7 available for any special user application.

**Method of Accessing:** The processor writes correct RAM location to place a character on the screen.

**Output:** Composite video, 1 volt P-P nominal, 75 ohms, 7.1 Mhz.

**Cursor:** Written by processor just like any other character. Supervisor uses a square dot centered in character field.

**Screen Blanking:** During horizontal or vertical retrace, between character lines and whenever the processor is accessing the display memory.

**Display Addressing:** Starts (upper left hand corner) at address H1000, and ends at H14FF. As addresses are incremented, the display position moves downward.

**Additional User RAM:** A total of 768 bytes starting at address H1500. Actually a part of the display memory, but this is transparent to the user.

#### PROCESSOR

**Type:** Signetics 2650 microprocessor.

**Buffering:** All processor signals buffered for TTL fan-out of 10.

**Memory:** 1K bytes of PROM which contains supervisor program. 768 bytes of RAM unused by display is available for user programs. PROM is on-board expandable to 4K bytes.

**Control Lines:** Pause and stop-clock lines allow single stepping of programs. Disable-lines for address data, and control buses to allow DMA (Direct Memory Access) or dual processor operation.

#### CASSETTE INTERFACE

**Recording Format:** 300 baud, 1200/2400-Hz Kansas City Standard.

**Output Voltage:** 100 mV P-P.

**Misc. Size:** 8 1/2-inch square printed-circuit board.

**Power Consumption:** 3 amps at 5 volts.



**VOLKSMETER!**

**THE LM-40** With Rechargeable Batteries & Charger Unit **\$190**  
 0.1% Accuracy

Full four digits.  
 Less than 2" high.  
 Automatic zeroing.  
 Automatic polarity.  
 Low power: <3W.  
 MOS/LSI construction.  
 Low, low price.

### TEXAS INSTRUMENTS CALCULATORS

SR-52	\$199.95
SR-56	89.95
SR-51-II	59.95
PC-100	169.95

### HEWLETT-PACKARD CALCULATORS

HP-97	675.00
HP-67	399.95
HP-25C	180.00
HP-25	132.00
HP-21	72.00



**Only \$195**  
 With Rechargeable NiCad Batteries & Charger Unit.

- Small and RUGGED—ideal for field use.
- 1 Hz resolution on low range.
- Overload protection.
- Large 7-digit LED display.
- 10 Hz to 60 MHz frequency \* range.
- C-MOS construction.
- 30 mV sensitivity—Amateur and CB frequencies.

Ideal for audio, broadcast, amateur, CB and industrial frequencies.

#### NEW!!

The FM-7 frequency range can be extended to 512 MHz with our new SC-5 Prescaler

Non-Linear Systems, Inc. 25th Year of Progress

To order call TOLL FREE 1-800-251-6771. In Tenn. call 615-528-6502  
 POST OFFICE BOX 165, Algood, Tennessee 38501  
 Shipping pre-paid on all orders  
 Circle the reader service card for our FREE catalog

CIRCLE 27 ON FREE INFORMATION CARD

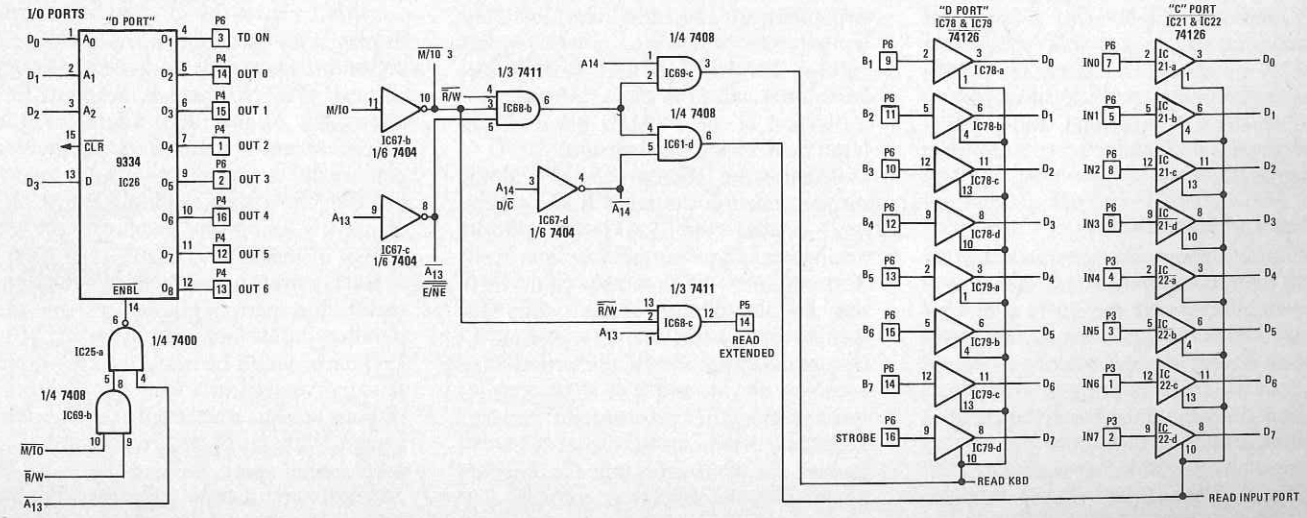
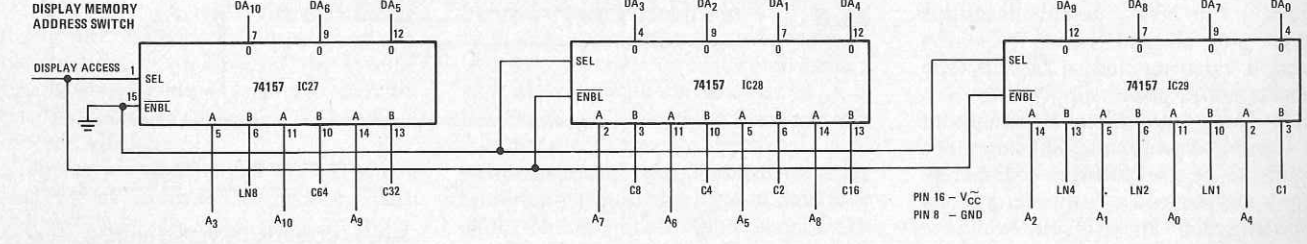
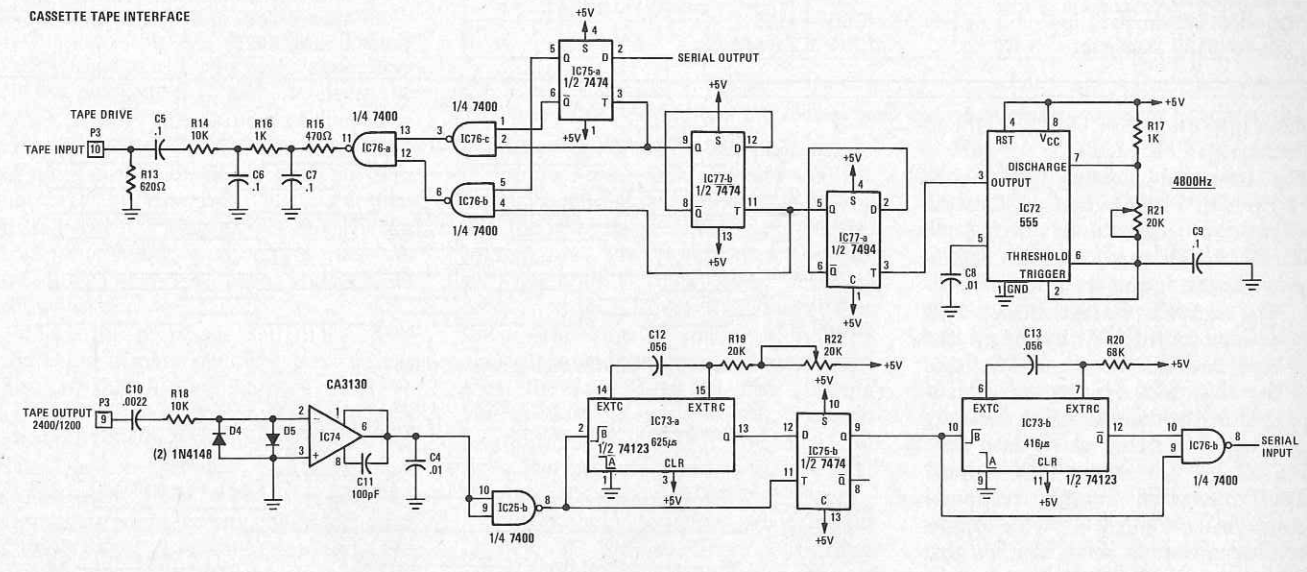
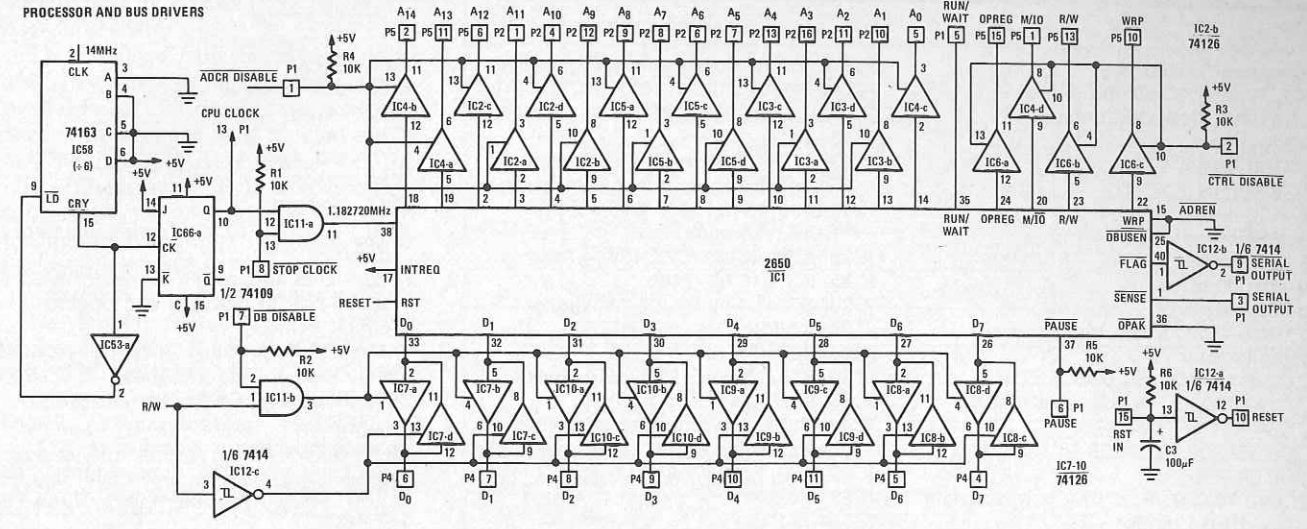
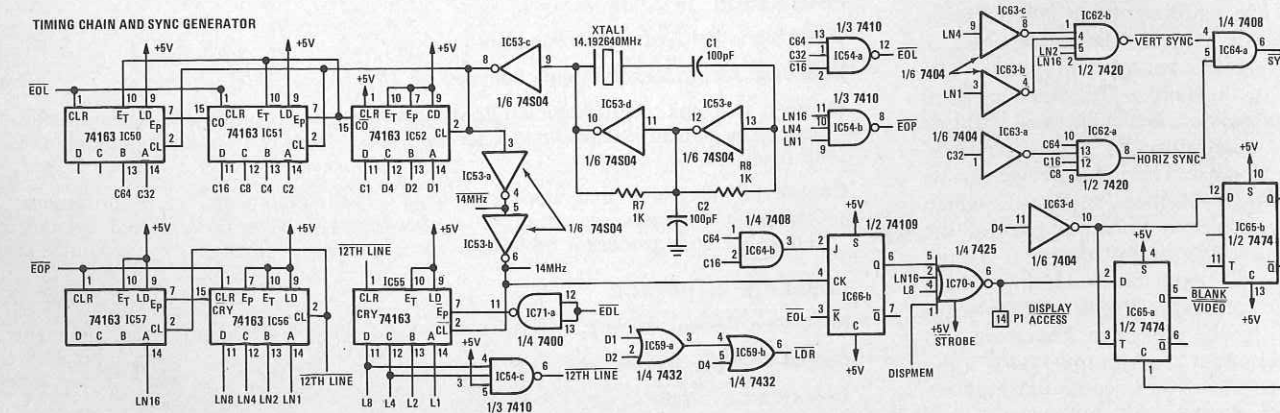
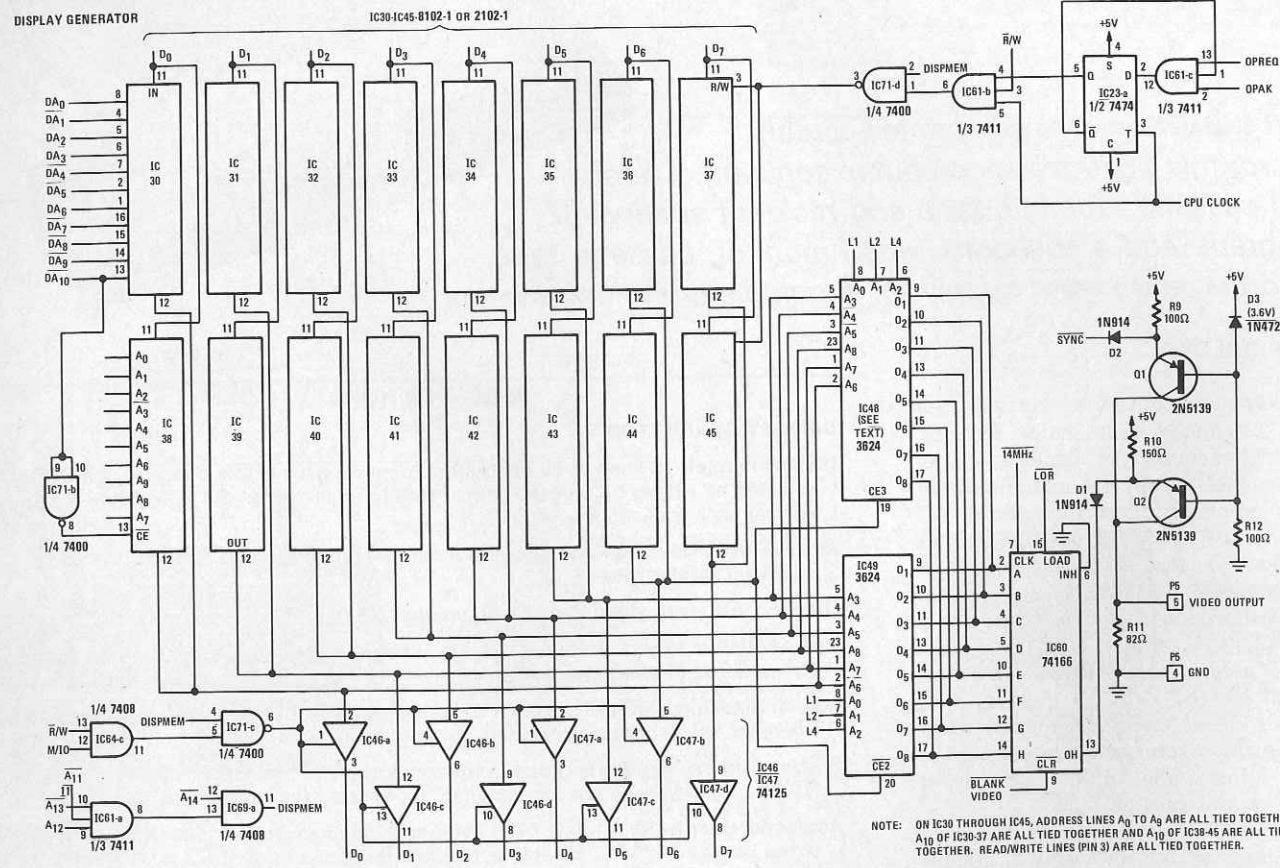
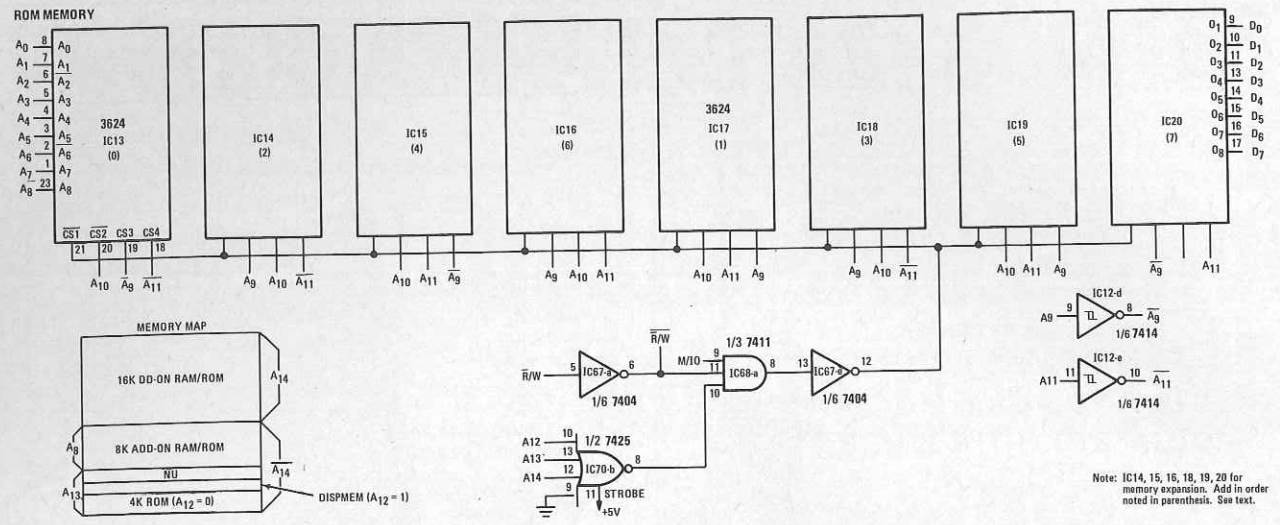


FIG. 1—COMPLETE SCHEMATIC of 2650-based microcomputer. All circuitry, including cassette-tape interface and video display generator, mount on single PC-board. Connection to peripheral devices is made via six IC sockets.

**All resistors** 1/4 watt, 5%.  
 R1-R6, R14, R18—10,000 ohms  
 R7, R8, R16, R17—1000 ohms  
 R9—330 ohms  
 R10—150 ohms  
 R11—82 ohms  
 R12—100 ohms  
 R13—620 ohms  
 R15—470 ohms  
 R19—20,000 ohms  
 R20—68,000 ohms  
 R21, R22—20,000-ohm trimmer potentiometer  
 C1, C2, C11—100 pF, disc  
 C3, C14—100  $\mu$ F, 16 volt, electrolytic  
 C4, C8—0.01  $\mu$ F, disc  
 C5, C6, C7, C9, C15—C29—0.1  $\mu$ F, disc  
 C10—0.0022  $\mu$ F  
 C12, C13—0.056  $\mu$ F,  $\pm$ 10% polyester film  
 D1, D2—1N914 diode  
 D3—1N4729 Zener  
 D4, D5—1N4148 diode  
 Q1, Q2—2N5139 transistor

**PARTS LIST**

IC1—2650 microprocessor (Signetics)  
 IC2-IC10, IC21, IC22, IC78, IC79—74126  
 IC11, IC64, IC69—7408  
 IC12—7414  
 IC13, IC17—3624, pre-programmed PROM containing supervisor program  
 IC14-IC16, IC18-IC20, IC48—3624, PROM (see text)  
 IC23, IC24, IC65, IC75, IC77—7474  
 IC25, IC71, IC76—7400  
 IC26—9344, 4-bit by 2-bit multiplier (Fairchild)  
 IC27-IC29—74157  
 IC30-IC45—2102-1, RAM (Signetics)  
 IC46, IC47—74125  
 IC49—3624, pre-programmed PROM character generator, upper case  
 IC50-IC52, IC55-IC58—74163  
 IC53—74S04  
 IC54—7410  
 IC59—7432  
 IC60—74166  
 IC61, IC68—7411  
 IC62—7420  
 IC63, IC67—7404  
 IC66—74109  
 IC70—7425  
 IC72—555, timer  
 IC73—74123  
 IC74—CA3130  
 XTAL1—14.192640 MHz series-resonant crystal  
 MISC.—One 40-pin DIP socket for IC1, six 16-pin DIP sockets and printed-circuit board.  
 The following parts may be ordered from: Central Data Company, P.O. Box 2484, Station A, Champaign, IL 61820.  
 IC49—3624, pre-programmed PROM character generator, upper case, \$27.  
 IC13, IC17—3624, pre-programmed PROM containing supervisor program, \$27 each.  
 PC board, predrilled and etched, \$30.  
 An assembled and tested microcomputer board, \$325.

number of ports can be easily expanded to 256.

The on-board memory consists of 1024 bytes of PROM used to store the supervisor program along with 2048 bytes of RAM used for the video-display generator and for program storage. The external storage device is a cassette-tape recorder. An on-board cassette-tape interface IC is provided that uses the 1200/2400 Hz, 300-baud standard to store the data. When the cassette interface is not being used, data lines are available for serial I/O (Input/Output) data transfer. The computer operates off of a single +5-volt supply. When it comes right down to it, all that you need to get rolling in microcomputers is the board described in this article, plus an ASCII-encoded keyboard, a video monitor, a cassette-tape recorder and a power supply.

Something more should be said about the supervisor program at this time since it pulls all of the hardware together to form a simple to use computer system. The program allows you to have cassette-tape input or output to or from any memory block (in a standard format, in any length that you want), display or change memory, set a software breakpoint (stop) address, inspect and set the CPU registers, and jump to any memory location to execute your program.

**Theory of operation**

Figure 1 shows the schematic for the 2650 microcomputer system. Because of the architecture of the 2650 microprocessor, the Processor and Bus Drive circuit is very simple. All of the output lines of the 2650 are buffered by tri-state buffers, and the data bus is buffered in both directions, with only one set of buffers being enabled at a time.

Figure 2 shows the timing relation-

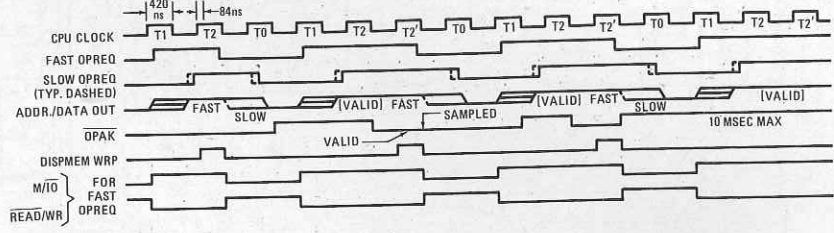


FIG. 2—2650 MICROPROCESSOR timing relationships.

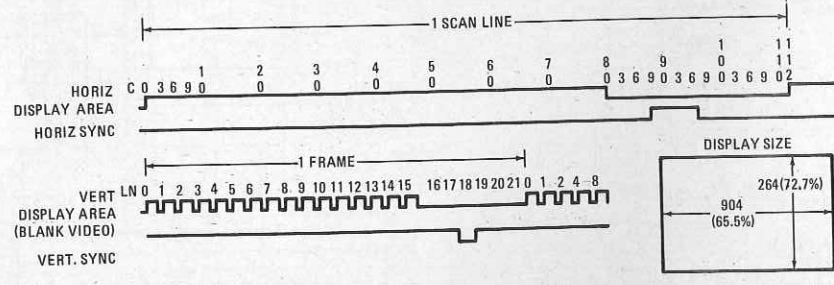


FIG. 3—TIMING DIAGRAM of horizontal, vertical and sync signals supplied to video monitor.

ships for the 2650 microprocessor. Note that both OPREQ (operation request) and the address lines become stable somewhere in an interval of about 600 ns, depending on the individual 2650, the temperature and the power supply voltage. The 1.18 Mhz TTL clock for the 2650 is derived from the output which is a division of the 14-MHz master oscillator used in the display unit.

Because the microprocessor and the display unit use the same RAM (unless you expand the RAM), a priority arrangement for the memory had to be devised. Since the processor could be in the middle of an access when the display needs the memory again, the display checks to see if the processor is accessing RAM, and if it is, the display waits. After the processor is finished accessing the memory, the processor is locked out from accessing the memory again until the display is through. The

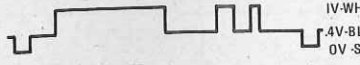


FIG. 4—COMPOSITE VIDEO SIGNAL supplied to video monitor.

display releases the memory to the processor whenever it is doing inter-line or vertical blanking, which accounts for about 53% of the time. Therefore, the processor runs at about half-speed when continually accessing the display memory, which is very seldom. When the display is using the memory, pin 36 (OPAK) of the 2650 is high.

Data is transferred between the processor and peripheral devices via the parallel input and output ports. The keyboard should be hooked to the input port by connecting it to the correct pins of plug P6. The data from the keyboard is read by the READ DATA command. The other input port is read by a READ CONTROL command. The bit settable

output port is accessed by the WRITE DATA instruction.

The Timing Chain and Sync Generator circuit divides the 14 Mhz clock in several stages to form the various signals needed to interface with a video monitor. Derived from these divisions of the master clock are the signals HORIZONTAL SYNC, VERTICAL SYNC, and BLANK VIDEO (composite blanking). Figure 3 shows the relation between the vertical and horizontal timing and the sync pulses.

The Display Memory circuit consists of sixteen 2102-1 RAM IC's and up to two 3624 PROM's. The 3624 PROM's are used for both the character generators and the supervisor program (as opposed to 1702's) so that the whole system could run off of a single supply. The use of PROM's for character generators also allows you to create your own characters, symbols or limited graphics. If bit 6 of the ASCII data is low, it selects one of the character generators (IC49), while if it is high it selects the other (IC48). The outputs of the character generators are fed into a parallel-to-serial converter where they are sent out at a 14 Mhz rate. They are then mixed with the sync pulses to form the composite video signal that is sent to the monitor. The video output voltages are shown in Fig. 4.

Since the processor and the display share the display memory, the address lines of the display memory must be switched between the processor address bus and the display timing generator. The Display Memory Address Switch circuit does this. When the Display Generator is not writing characters (and therefore not accessing memory), the DISPLAY ACCESS line is low, which selects the processor address bus to be gated to the RAM. When the display is not blanking the video, however, the Timing Chain and Sync Generator circuit selects the addresses for the RAM in an ordered fashion.

There is a special pattern by which the display accesses the RAM. This pattern allows all locations of memory not used by the display section (there are 768 of these bytes) to be confined to one memory block, not just several bytes here and there scattered throughout memory. A memory map for the display is shown in Fig. 5. When the address of the RAM is incremented, the

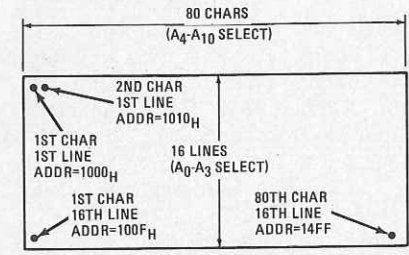


FIG. 5—RANDOM ACCESS MEMORY is simultaneously used for the video display and program storage.

PIN NO.	P1	P2	P3	P4	P5	P6
1	ADDR DISABLE	A <sub>11</sub>	IN6	OUT 2	M/I/O	GND
2	CTRL DISABLE	GND	IN7	+5V	A <sub>14</sub>	OUT 3
3	SERIAL INPUT	+5V	IN5	GND		TD-ON
4		A <sub>10</sub>	IN4	D <sub>7</sub>	GND	+5
5	RUN/WAIT (OUT)	A <sub>0</sub>		D <sub>6</sub>	VIDEO OUT	IN1
6	PAUSE	A <sub>6</sub>		D <sub>0</sub>	A <sub>12</sub>	IN3
7	DB DISABLE	A <sub>5</sub>		D <sub>1</sub>	+5V	IN0
8	STOP CLOCK	A <sub>7</sub>	GND	D <sub>2</sub>	+5V	IN2
9	SERIAL OUT	A <sub>8</sub>	TAPE RECORDER EARPHONE	D <sub>3</sub>	GND	B <sub>1</sub>
10	RESET OUT (SQUARED)	A <sub>1</sub>	TAPE RECORDER MICROPHONE	D <sub>4</sub>	WRP	B <sub>3</sub>
11	+5V	A <sub>2</sub>		D <sub>5</sub>	A <sub>13</sub>	B <sub>2</sub>
12	+5V	A <sub>9</sub>		OUT 5		B <sub>4</sub>
13	CPU CLK	A <sub>4</sub>	GND	OUT 6	$\bar{R}/W$	B <sub>5</sub>
14	DISPLAY ACCESS	+5		OUT 0	READ EXTENDED	B <sub>7</sub>
15	RESET IN	A <sub>9</sub>		OUT 1	OPREQ	B <sub>6</sub>
16		A <sub>3</sub>		OUT 4	$\bar{A}_{13}$	STROBE

FIG. 6—PIN CONNECTIONS of DIP sockets used to connect microcomputer to external devices.

character on the video display moves down one line. When it gets to the bottom line, the next character is on the top line, one character to the right of the present one. Therefore, when the display memory is filled, every memory location from address 1000 to 14FF is filled with data. If you wish to write characters across a line, you must increment the address by 16, thus moving you to the right one position. So from locations 1500 to 17FF you may put your own programs and data, just as if the video display wasn't there.

It may help to show what would happen if the memory addressing scheme was worked out another way. If the addresses were incremented as the characters were being printed on a line, then addresses 80 to 127 would be left unused, along with 207 to 254 and so on to form 16 groups of 48 characters each. All of these groups are separated by 80 characters, and programs cannot be written in them unless they are less than 49 bytes long! The addressing format can be ignored by someone programming the unit, for it is transparent to the programmer. It was thought that it would be appropriate, however, to bring it out here for a more hardware oriented person.

The PROM memory consists of up to eight 3624 4K-bit PROM's that are selected as a function of the upper six address lines. The first two IC sockets (IC13 and IC17) on the PC board are usually filled with the supervisor program. It should be pointed out that would allow the board to have a special purpose such as an intelligent terminal or a process controller. These programs could either replace the supervisor program or be added to the empty sockets.

The last circuit is the Cassette Interface, which connects to the serial input and output pins of the 2650 processor. The modulator consists of an oscillator and gating circuitry to allow either 1200 or 2400 Hz go to the tape recorder's microphone jack. The demodulator consists of a limiter (IC74) and two Monostable Multivibrators (IC73-a and IC73-b). The output of monostable IC73-a goes low if the input frequency is not fast enough to keep retriggering it (somewhere between 2400 and 1200 Hz). This output is latched by IC75-b, and the other monostable (IC73-b) takes care of bias and distortion problems. This output is sent to the serial input (sense) line of the 2650.

**Installation**

Connecting the circuit board to external devices is accomplished through the use of DIP plugs and sockets. Figure 6 shows the pin connections of these sockets.

Connection to your video monitor is made using plug 5, pins 4 and 5. Pin 4 is the ground, and pin 5 is the 1 volt P-P composite-video signal. Plug 6 is used to connect to your keyboard. The pin numbers that correspond to the ASCII data bits can be found in Fig. 6.


The strobe signal must be low going, and should ideally be active as long as the key is depressed. Note that the supervisor program will not accept a very short strobe pulse, since the software is used to detect the strobe. If your keyboard strobe is small (less than 1 ms), you can add the circuit shown in Fig. 7 to be sure that the program will catch every keypress.

Most keyboards have a strobe that lasts as long as a key is depressed, so it is then simply a matter of hooking up the

continued on page 90
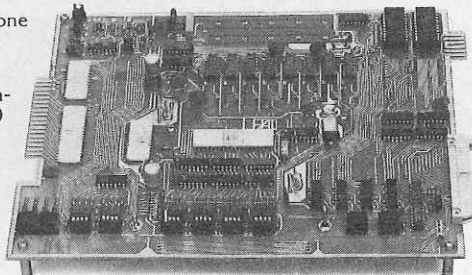
## If you want a microcomputer with all of these standard features...

- 8080 MPU (The one with growing software support)
- 1024 Byte ROM (With maximum capacity of 4K Bytes)
- 1024 Byte RAM (With maximum capacity of 2K Bytes)
- TTY Serial I/O
- EIA Serial I/O
- 3 parallel I/O's
- ASCII/Baudot terminal compatibility with TTY machines or video units
- Monitor having load, dump, display, insert and go functions



- Complete with card connectors
- Comprehensive User's Manual, plus Intel 8080 User's Manual
- Completely factory assembled and tested—not a kit
- Optional accessories: Keyboard/video display, audio cassette modem

interface, power supply, ROM programmer and attractive cabinetry... plus more options to follow. **The HAL MCEM-8080. \$375**

## ...then let us send you our card.

HAL Communications Corp. has been a leader in digital communications for over half a decade. The MCEM-8080 microcomputer shows just how far this leadership has taken us... and how far it can take you in your applications. That's why we'd like to send you our card—one PC board that we feel is the best-valued, most complete



microcomputer you can buy. For details on the MCEM-8080, write today. We'll also include comprehensive information on the HAL DS-3000 KSR microprocessor-based terminal, the terminal that gives you multi-code compatibility, flexibility for future changes, editing, and a convenient, large video display format.

**HAL Communications Corp.**  
Box 365, 807 E. Green Street, Urbana, Illinois 61801  
Telephone (217) 367-7373

## Want to cut out a career as a two-way radio technician?

MTI offers the only training for professional FM two-way radio available. Qualified technicians are employed in government, industry, and public service. But training is your key.

You could cut out a career as a two-way radio technician by cutting out this coupon. We'll send you information on how you can learn more about this specialized field, at home.

Name \_\_\_\_\_

Address \_\_\_\_\_

City/State/Zip \_\_\_\_\_

I am a veteran or serviceman on active duty. **DD3**




formerly

**MOTOROLA TRAINING INSTITUTE**

College Hill, Summerdale, Pennsylvania 17093

CIRCLE 26 ON FREE INFORMATION CARD

## NEW! D.V.M. KIT

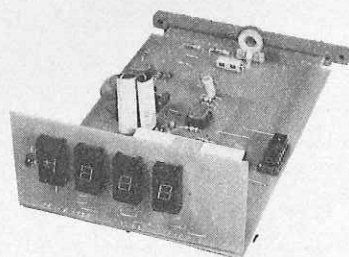

### Convertible into Multimeter

**KIT FEATURES** BASIC 2 RANGE D.V.M. ACCURATE TO 1%. CIRCUITS FOR ADDITIONAL VOLTAGE RANGES, OHMS, D.C. CURRENT, AND A.C. VOLTS CAN BE ADDED. PARTS MOUNT ON EDGE CARD CONNECTOR P.C. BOARD. DISPLAY BOARD HAS EASY TO READ 1/3" LED'S AND CAN BE REMOTE MOUNTED.

**KIT CONTAINS** • 2 P.C. Boards • Signal Converter • Digital Processor • Op. Amp • Inverter • 3-Drivers • 4-LED Displays •

**Basic D.V.M. Kit \$39.90**  
(POWER SUPPLY NOT INCLUDED)

Send Check Or Money Order. Add \$1 for Postage and Handling in U.S. N.J. Residents Add 5% Tax.

**J. B. Electronics Inc.**  
Box 321  
Short Hills, N.J. 07078

of the output signal are typically 250 ns and 50 ns, respectively, when pin 11 is loaded by 10 pF.


Figure 8 shows a simple add-on buffer stage that can be used to provide a low-impedance variable-amplitude squarewave output signal. The circuit is a simple complementary emitter-follower that is driven directly from the pin-11 squarewave output of the IC. Short circuit output protection is provided by the 47-ohm resistors (R5 and R6) in series with the transistor emitters. The output level is fully variable from maximum to zero using LEVEL potentiometer R7. The output signal is referenced to zero volts (ground) and can be used to drive high- or low-impedance external loads.

*continued next month*

### BUILD A COMPUTER


*continued from page 35*

wires to the correct pins of the DIP plug. If you have a keyboard with tri-state outputs, they can be always enabled. Then their outputs can be wired to the inputs of the on-board buffers as in a normal keyboard.

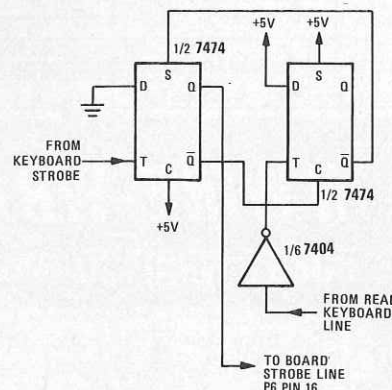

**FIG. 7—DURATION OF STROBE pulse from keyboard is increased using this add-on circuit.**

To hook up your cassette-tape unit, you use plug 3 of the board. Pin 10 is for the record jack and pin 9 is for the earphone jack. Pin 14 of plug 3 can be used to turn off and on the tape recorder (using the auxillary control line) by simply hooking up a relay and switching transistor to the circuit as shown in Fig. 8. You may need to adjust the volume and tone controls on the

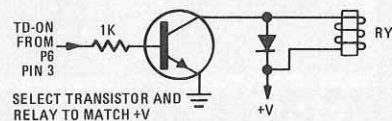

**FIG. 8—AUTOMATIC CASSETTE TAPE operation is obtained by adding driver transistor and relay.**

tape recorder in order to get perfect data storage (no errors on loading).

*continued next month*

# next month

MAY 1977

### ■ Build A Programmable Frequency Divider

IC's and printed-circuit board construction make it easy to duplicate this valuable test instrument.

### ■ Build A CB Preamp

Improve your CB reception. Add this inexpensive preamp. You'll be surprised at the difference it makes.

### ■ ABC's Of Room Equalization

A new easy way to match your listening room to your hi-fi gear.

### ■ Build A Speaker Phone

Hands off talking and listing when you use your telephone is the purpose of this device.

### ■ Heath's New Programmable Color TV Kit

Set up the evenings programs and the set takes care of itself—it changes channels and reorients the antenna rotator.

### ■ WARC '79

A report on the pending World Administrative Radio Conference and its potential effects on you.

### PLUS

Jack Darr's Service Clinic



All About Function Generators

Lab Tested HI-FI Reports

Komputer Korner
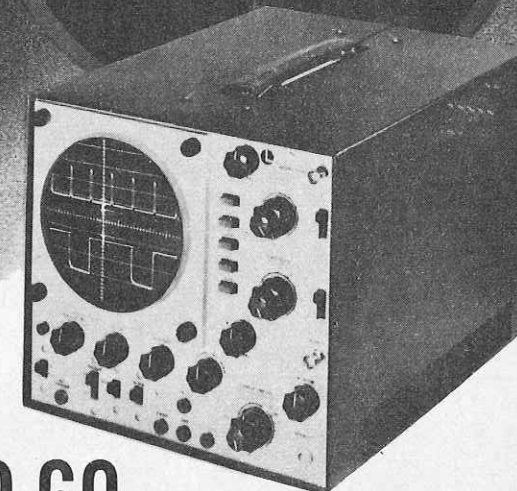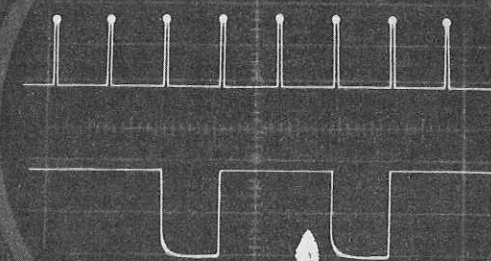
# the bright one

new phosphor picture tube with twice the brightness



## TO-60 automatic dual-trace triggered-sweep oscilloscope

P-31 phosphor CRT has double the brightness for bright displays even in high speed dual-trace modes. Bandwidth: DC to 15 mhz. Unique features for the industry's greatest value are: • Automatic Triggering • Automatic Astigmatism • Automatic Horizontal Sweep • Automatic Horiz/Vert. TV Triggering provides positive display on composite video signals. Vertical sensitivity: .01 volts/cm to 20 volts/cm in 1-2-5 step sequence. Horizontal Sweep Speeds: .2 sec/cm to .5μ sec/cm in 1-2-5 step sequence. Has 5X magnifier at all sweep speeds. External Horiz. Amp. Bandwidth: DC to .5 mhz; Sensitivity: .5 volts/cm. Calibrated Test Signal: 1 volt P-P square wave. Power: 105-125 volts, 60 cycles, 65 watts

Model TO-60 Less Probes. Net ..... \$489.50

TO-55 automatic single-trace triggered sweep oscilloscope. Features same as TO-60 except Vert. Bandwidth is DC to 10 mhz.

Model TO-55 Less Probes. Net ..... \$379.50

For the "bright one," see your distributor, or write:



**LECTROTECH, INC.**

5810 N. Western Avenue, Chicago, Illinois 60659

Area (312) 769-6262

CIRCLE 62 ON FREE INFORMATION CARD