

Radio-Electronics

THE MAGAZINE FOR NEW IDEAS IN ELECTRONICS

SOLAR TRACKING SYSTEM

A guide to building a system that controls solar energy panels so they track the sun.

WIRE WRAP JUNGLE

New construction technique combines PC and wire-wrap assembly to get the best of both worlds.

AUDIO TEST STATION

Construction details for a high-quality audio test instrument that combines several important test instruments into a single cabinet.

CASES AND CABINETS

A roundup of commercially available off-the-shelf enclosures that add a professional look to your projects.

PLUS:

- ★ Two Hi-Fi Test Reports From R-E's Audio Lab
- ★ New IHF Amplifier Standards
- ★ Jack Darr's Service Clinic
- ★ State-Of-Solid-State
- ★ Computer Corner
- ★ Hobby Corner
- ★ CET Test

Build A Pro Quality
STRING SYNTHESIZER
It's A Bargain



GERNSBACK PUBLICATION



692108 JNK 11024090 14 A DEC81
R J JENKINS
1102 SOUTH 45TH ST
TEMPLE TX 76701
02

PAGE 97 FOR
BY ALLOWANCE PLAN

computer corner

8085 A look at one memory IC that is among the 8085 family of devices.

J. TITUS, C. TITUS, D. LARSEN AND P. RONY

IN A PREVIOUS COLUMN (JANUARY 1979), we described the new Intel 8085 microprocessor IC. This is an upgraded type of 8080 microprocessor, since it has features that are not found on the 8080 device. One of the advantages in using the 8085 is the availability of "family" devices that can be used with little or no additional external logic. This makes the 8085 and its family ideal for small controllers, instruments and games, where ex-

*This article is reprinted courtesy American Laboratories. Dr. Rony, Department of Chemical Engineering, and Mr. Larsen, Department of Chemistry, are with the Virginia Polytechnic Institute & State University. Both Mr. J. Titus and Dr. C. Titus are with Tychon, Inc.

pansion and the ability to run large programs such as BASIC may not be required.

This month we will describe one of the 8085-family devices, the 8155 read/write memory.



8155 RAM

The 8155 read/write memory IC contains 256 bytes of memory, which is probably more than enough for a small system. In most cases, the read/write memory will be used for temporary storage of data or results, as well as register and address information. The 8155 is also bus-compatible with the 8085 system through the use of the bidirectional address-data bus and standard control sig-

nals. In this case, only the $\overline{IO/\overline{M}}$, \overline{RD} and \overline{WR} signals are necessary for memory control. The ALE, CLOCK and RESET signals from the 8085 are also provided for internal control of the IC.

The 8155 has some I/O lines—in fact, there are two 8-bit I/O ports and one 6-bit I/O port. The two 8-bit I/O ports can be operated in either the input or output mode; individual bits cannot be selected. These two ports are called ports A and B. The 6-bit I/O port (port C) can be operated in several ways, but these are beyond the scope of this article. Let us just say that these operations allow the I/O ports to perform in a manner similar to that provided by the mode 1 and mode 2 operation of the 8255 programmable peripheral interface.

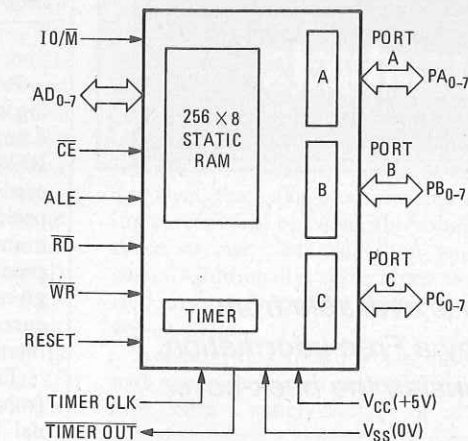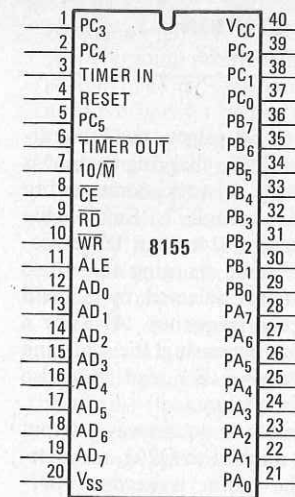The 8155 read/write memory also contains a 14-bit programmable counter, re-



Control Bits		Mode Of Operation
M2	M1	
0	0	Output a logic 0 during the second half of the count.
0	1	Output a squarewave, same as 00 above, but reload and restart the count at the end of each count sequence.
1	0	Output a single short pulse at the end of the count sequence.
1	1	Output a single pulse at the end of the count, but reload and restart the count at the end of each count sequence.

ferred to as a timer. The timer uses either the 8085's clock output or an externally applied clock signal. The timer's output is available as a pin on the 8155 IC, and it can be used several ways, depending on your requirements. It could be connected to the Serial Input Data (SID) pin 5 to be sensed by the RIM instruction, or connected to one of the 8085's interrupt pins (RST 7.5, for example) so that the end of the timer's period could be detected via an interrupt. The timer's output is fairly flexible, being programmed to operate in one of four ways:

Control bits M2 and M1 are the most significant ones in the 16-bit value programmed into the counter. Since the counter is only 14-bits-long, the control bits are not included in the count itself, but are used by the control logic to determine the counter-output state when the count has been finally decremented to zero. Whenever a new 14-bit count value is reprogrammed into the counter, these two control bits must also be included in the new 16-bit word.

The 8155 read/write memory also has an internal control register that is loaded with an 8-bit byte that is used to determine operation of the I/O ports and the 14-bit counter.

R-E

make more money with RCA SKs...

... and your customers will really appreciate your reliable service.

You eliminate costly call backs because: with RCA SKs you know you're using the best. RCA guarantees it. We'll replace any defective SK within one year of purchase by the dealer. We can afford to make this offer because our malfunction rate is one of the lowest in the industry — less than one percent.

With RCA SKs you know your customer is getting the right semiconductor. Our SK line includes over 900 replacement transistors, rectifiers, thyristors, integrated circuits and high voltage triplers that meet or exceed the OEM standards for the 150,000 domestic or foreign semiconductors our SKs can replace.

You save time because you'll identify the exact SK you need quickly in RCA's easy-to-use Replacement Guide with complete installation data. And on every SK package you'll find all the necessary technical specifications, physical characteristics and terminal diagrams.

All hardware, when needed, is also included right in the SK package which saves you extra trips back to the truck or back to the shop.

You make more money because: you can work faster, more efficiently with RCA SKs. And you virtually end costly call-backs which means a lot more satisfied customers as well.

For details on how to order, see your RCA SK Distributor. Or contact RCA Distributor and Special

Products Division, Deptford, N.J. 08096, Attention: Sales Promotion Services.



RCA

SK Solid State Replacement