

Try this exciting new hobby!

Build your own electronic concert organ. It's easy. No technical knowledge required. Just follow the clearly pictured instructions of the famous Wersi do-it-yourself system. Choose from seven different models. Send \$2.00 (refundable) with coupon for colorful 104 page catalog.

WERSI



Wersi Electronics, Inc.
Dept. 42,
1720 Hempstead Road
Lancaster, PA 17601

Enclosed is \$2.00 for my copy of your 104 page catalog.

Name _____
Address _____
City _____ State _____ Zip _____

CIRCLE 28 ON FREE INFORMATION CARD

FREE SWTP

CATALOG

Audio-Computers
Instruments
Kits & Assembled

COMPUTER
PRODUCTS
CATALOGUE



Southwest Technical Products Corporation
219 W. RHAPSODY
SAN ANTONIO, TEXAS 78216

CIRCLE 58 ON FREE INFORMATION CARD

COMPUTER CORNER

continued from page 87

Are there any other values that could have been used to program the real-time clock for a 20-ms interrupt? Actually, 200_{10} could have been loaded into the counters, and the MK5009 would have been programmed for 10-kHz operation (0.1-ms time interval). A value of 2000_{10} could also be used if the MK5009 is programmed for 100-kHz operation (0.01-ms time interval).

When the real-time clock interrupts the 8080, the 8080 services some peripheral devices and then clears the interrupt flip-flop (OUT 306). The count is then transferred from the latches to the counters when the OUT 303 instruction is executed. This must be done because the counters, after counting to zero, are next decremented to 11111111_{16} . Therefore, if the counters were not reloaded, the 8080 would be interrupted 4096 clock pulses later, rather than the count in the latches. After re-enabling the interrupt, the 8080 returns to the interrupted task.

Adding the three 4-bit counters to the real-time clock interface has increased its capabilities. Intervals of from $1 \mu\text{s}$ to 4.096×10^5 seconds can be timed.

Another real-time clock application is as a *time-of-day clock*. This type of clock is simply a peripheral device, or a series of memory locations, in which the current time of day is stored and updated. The time can be updated every second or $1/100$ second, depending on the hardware, software and uses of the clock.

One method of constructing a time-of-day clock would be to program the MK5009 for 1-Hz operation and then wire the output of the MK5009 to a *counter chain* or *divider chain*. These chains consist of a divide-by-10 counter and a divide-by-6 counter for seconds, a divide-by-10 counter and a divide-by-6 counter for minutes, and a divide-by-4 counter and a divide-by-6 counter for hours. Instead of using a divide-by-4 counter and a divide-by-6 counter for a 24-hour format, a divide-by-4 and a divide-by-3 counter could be used for a 12-hour format. The counter outputs could be wired through tri-state interface devices to the microcomputer's data bus. The microcomputer would then have to execute some accumulator I/O or memory-mapped I/O instructions to read the time from the time-of-day clock. By using this method, *no* interrupts are required and the software instructions for reading the time are very simple. Additional instructions could be added so that you can enter a time into the microcomputer via a CRT or teletypewriter. This time would then be written out to the time-of-day clock, so that it is programmed for the correct time when the microcomputer is started. This can only be done if programmable counters are used in the time-of-day clock interface. Of course, an MK5009 does not have to be used as a 1-Hz clock source. A 60-Hz signal could be derived from the 110- to 220-VAC power lines and then be divided by 60 before being applied to the counter chain.

R-E

TABLE 3

START,	*000 000	
	LXISP	/LOAD THE STACK POINTER WITH A
	STACK	/R/W MEMORY ADDRESS BECAUSE IN-
	0	/TERRUPTS CAN OCCUR.
	MVIA	/THEN LOAD THE A REGISTER WITH
	003	/0000 0011, TO PROGRAM THE MOST
	OUT	/SIGNIFICANT COUNTER WITH 0
	305	/WHEN THE MK5009 (1 KHZ).
	MVIA	/THEN LOAD THE A REGISTER WITH
	024	/00010100 SO THAT THE TWO LEAST
	OUT	/SIGNIFICANT COUNTERS ARE
	304	/LOADED WITH DECIMAL 20.
	OUT	/CLEAR THE INTERRUPT FLIP-FLOP
	306	
	OUT	/THEN TRANSFER THE CONTENT OF
	303	/THE LATCHES TO THE COUNTERS.
	EI	/ENABLE THE INTERRUPT AND
	.	/THEN EXECUTE THE REMAINDER
	.	/OF THE PROGRAM.
	.	
	*000 070	
RTCISS,	.	/THE REAL-TIME CLOCK INTERRUPTED
	.	/THE MICROCOMPUTER, SO SERVICE
	.	/SOME OF THE PERIPHERAL DEVICES
	OUT	/THEN CLEAR THE FLIP-FLOP THAT
	306	/CAUSED THE INTERRUPT AND
	OUT	/RELOAD THE COUNTERS WITH
	303	/THE CONTENT OF THE LATCHES.
	EI	/RE-ENABLE THE INTERRUPT
	RET	/AND RETURN TO THE TASK THAT
		/WAS INTERRUPTED.