

BUILD THIS

SPEECH SYNTEHSIZER

DAVID A. WARD

Computerized voice synthesizers are turning up everywhere. Perhaps you've heard one at the grocery store check-out stand, in an automobile, or from an educational toy. Other uses include text-to-speech converters for the visually impaired, talking clocks, calculators, radar detectors, chess and other games, blood-sugar and pressure-monitoring devices, and automotive test equipment.

It's a lot of fun experimenting with voice synthesizers; in fact, the author has built and experimented with four different voice synthesizer IC's, and has listened to at least ten different synthesizers in all.

So that you can share in the fun too, we'll present theory and construction details of a stored-word speech system that you can connect to any personal computer

having a parallel printer port. A simple BASIC program then uses LPRINT statements to create speech output. A number of terms relevant to electronics are included: ampere, kilo, milli, volt, circuit, connect, farad, hertz, meg, mega, micro, nano, ohms, pico, as well as letters of the alphabet, numbers, and numerous others. The project can be built for about \$75.

Speech systems

Most speech synthesis systems operate in one of two ways: the stored-speech method or the allophone method. The allophone method uses *allophones*, little chunks of sound that can be combined to form words. The stored-word system stores entire words and phrases.

Each system has advantages and disadvantages. Allophone synthesis can offer an unlimited vocabulary and yet require very little memory. However, allophone speech synthesis is usually artificial sounding, monotone, and difficult for the untrained ear to understand. Probably the best application for allophone synthesis is in converting text to speech. Text-to-speech conversion can be a great aid for the visually impaired, allowing them to operate word processors and other computer programs.

By contrast, a stored-word synthesizer can offer excellent speech quality with intonation or feeling. However, a stored-word system requires tremendous amounts of memory for just a few minutes of speech. Typically, that limits a stored-word system to a vocabulary of several dozen words. The best application for a stored-word synthesizer is one that requires the clearest possible speech and a limited vocabulary, such as in an automobile, or a supermarket check-out stand. A stored-word

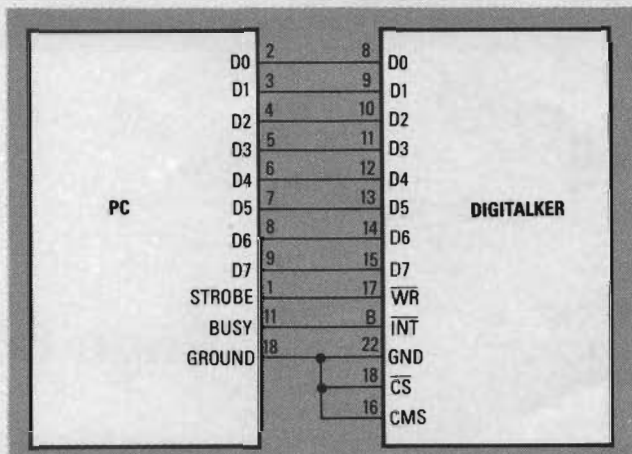


FIG. 1—THE PARALLEL PRINTER PORT of any personal computer can drive the Digitalker.

TABLE 1—WORD LIST (SSR1 AND SSR2)

THIS IS	48	IS	96
DIGITALKER	49	IT	97
ONE	50	KILO	98
TWO	51	LEFT	99
THREE	52	LESS	100
FOUR	53	LESSER	101
FIVE	54	LIMIT	102
SIX	55	LOW	103
SEVEN	56	LOWER	104
EIGHT	57	MARK	105
NINE	58	METER	106
TEN	59	MILE	107
ELEVEN	60	MILLI	108
TWELVE	61	MINUS	109
THIRTEEN	62	MINUTE	110
FOURTEEN	63	NEAR	111
FIFTEEN	64	NUMBER	112
SIXTEEN	65	OF	113
SEVENTEEN	66	OFF	114
EIGHTEEN	67	ON	115
NINETEEN	68	OUT	116
TWENTY	69	OVER	117
THIRTY	70	PARENTHESIS	118
FORTY	71	PERCENT	119
FIFTY	72	PLEASE	120
SIXTY	73	PLUS	121
SEVENTY	74	POINT	122
EIGHTY	75	POUND	123
NINETY	76	PULSES	124
HUNDRED	77	RATE	125
THOUSAND	78	RE	126
MILLION	79	READY	127
ZERO	80	RIGHT	128
A	81	SS(NOTE 1)	129
B	82	SECOND	130
C	83	SET	131
D	84	SPACE	132
E	85	SPEED	133
F	86	STAR	134
G	87	START	135
H	88	STOP	136
I	89	THAN	137
J	90	THE	138
K	91	TIME	139
L	92	TRY	140
M	93	UP	141
N	94	VOLT	142
O	95	WEIGHT	143
P	47		

NOTE 1: "SS" (#129) can be used to make singular words plural

TABLE 2—WORD LIST SSR5 AND SSR6

ABORT	0	FARAD	44	PER	88
ADD	1	FAST	45	PICO	89
ADJUST	2	FASTER	46	PLACE	90
ALARM	3	FIFTH	47	PRESS	91
ALERT	4	FIRE	48	PRESSURE	92
ALL	5	FIRST	49	QUARTER	93
ASK	6	FLOOR	50	RANGE	94
ASSISTANCE	7	FORWARD	51	REACH	95
ATTENTION	8	FROM	52	RECEIVE	96
BRAKE	9	GAS	53	RECORD	97
BUTTON	10	GET	54	REPLACE	98
BUY	11	GOING	55	REVERSE	99
CALL	12	HALF	56	ROOM	100
CAUTION	13	HELLO	57	SAFE	101
CHANGE	14	HELP	58	SECURE	102
CIRCUIT	15	HERTZ	59	SELECT	103
CLEAR	16	HOLD	60	SEND	104
CLOSE	17	INCORRECT	61	SERVICE	105
COMPLETE	18	INCREASE	62	SIDE	106
CONNECT	19	INTRUDER	63	SLOW	107
CONTINUE	20	JUST	64	SLOWER	108
COPY	21	KEY	65	SMOKE	109
CORRECT	22	LEVEL	66	SOUTH	110
DATE	23	LOAD	67	STATION	111
DAY	24	LOCK	68	SWITCH	112
DECREASE	25	MEG	69	SYSTEM	113
DEPOSIT	26	MEGA	70	TEST	114
DIAL	27	MICRO	71	TH (NOTE 2)	115
DIVIDE	28	MORE	72	THANK	116
DOOR	29	MOVE	73	THIRD	117
EAST	30	NANO	74	THIS	118
ED (NOTE 1)	31	NEED	75	TOTAL	119
ED (NOTE 1)	32	NEXT	76	TURN	120
ED (NOTE 1)	33	NO	77	USE	121
ED (NOTE 1)	34	NORMAL	78	UTH (NOTE 3)	122
EMERGENCY	35	NORTH	79	WAITING	123
END	36	NOT	80	WARNING	124
ENTER	37	NOTICE	81	WATER	125
ENTRY	38	OHMS	82	WEST	126
ER	39	ONWARD	83	SWITCH	127
EVACUATE	40	OPEN	84	WINDOW	128
EXIT	41	OPERATOR	85	YES	129
FAIL	42	OR	86	ZONE	130
FAILURE	43	PASS	87		

NOTE 1: "EDs" 31 and 32 work best with words that end with "T" or "D". "ED" 34 works best with words that end with soft sounds.

NOTE 2: "TH" (#115) can be added to words like; six, seven, and eight to make sixth, seventh, and eighth etc.

NOTE 3: "UTH" (#122) can be added to twenty, thirty, and forty to make twentieth, thirtieth, and fortieth, etc.

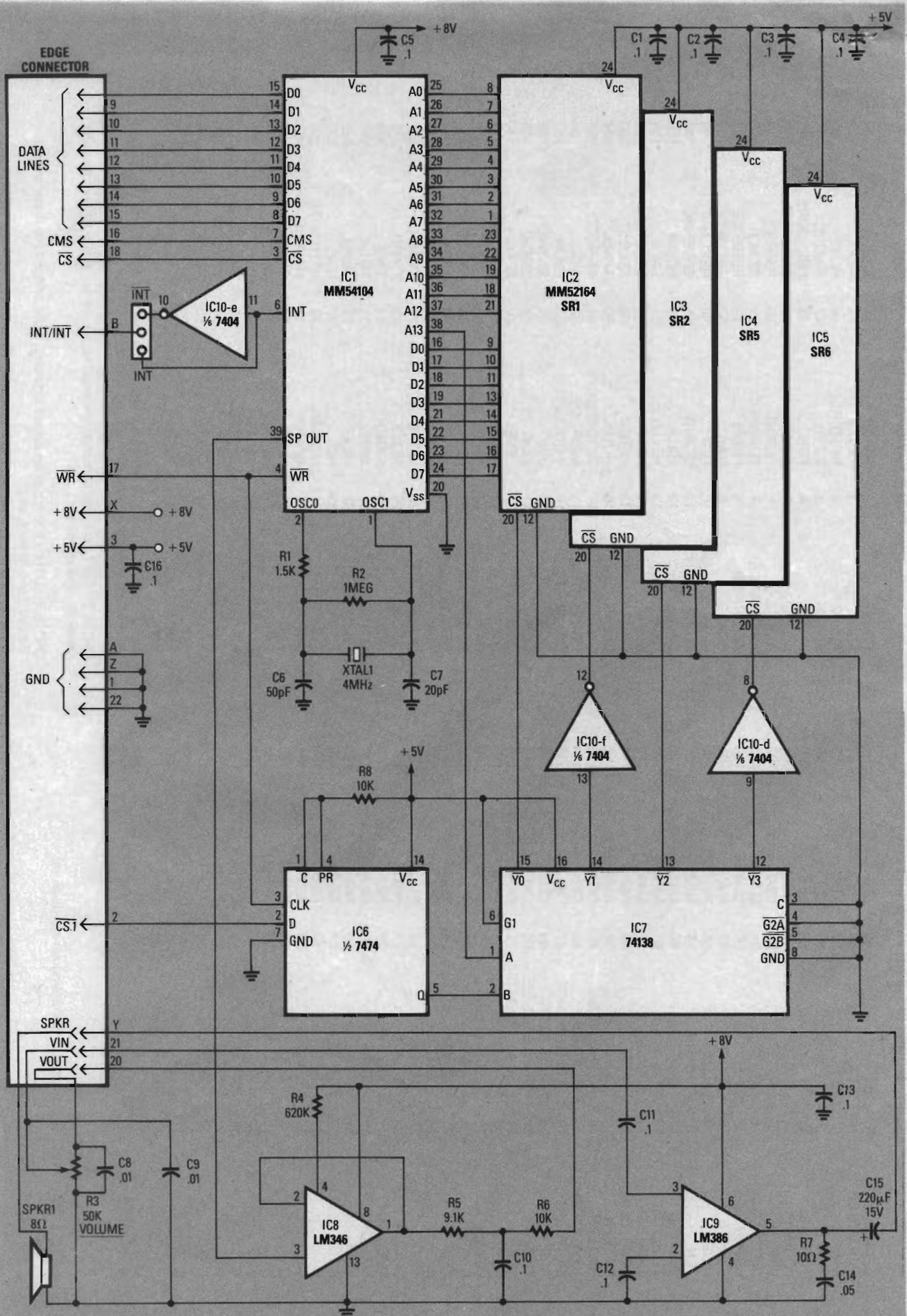


FIG. 2—SCHEMATIC DIAGRAM OF THE DIGITAL TALKER. The speech processor (IC1) reads data from the ROM's (IC2-IC5) and delivers speech output via pin 39.

synthesizer is useless for text-to-speech conversion because of the large amount of memory that would be required.

The Digitalker

National Semiconductor's Digitalker is a stored-word speech synthesis system that produces an exceptionally clear "voice." In fact, the Digitalker's quality exceeds Texas Instrument's *Speak & Spell* speech synthesizer. The Digitalker's voice has intonation or feeling, is not monotone, and even uses a female voice for the phrase "This is Digitalker."

The MM54104 SPC (Speech Processor Chip) is the heart of the Digitalker system. It's a 40-pin IC having 8 data lines (pins 8–15) that can be programmed manually with switches, or by connecting the device to a computer. For best results, a computer should be used to control the SPC so that sentences can be formed by stringing words together rapidly.

The SPC also has 14 ROM address lines (A0–A13, pins 25–38) that are to address ROM's containing speech data. Through those 14 address lines, the SPC can directly access 128K bits of speech data, which is good for about one minute of continuous speech. The SPC receives its data from the ROM's through eight data lines (pins 16–19 and pins 21–24). A number of other lines (pins 3, 4, and 7) are used for handshaking with a host computer, for connecting an external crystal oscillator (pins 1 and 2), and for speech output (pin 39)—which is connected to a filter and an audio amplifier. For more information on the SPC, see National's 1982 Linear Databook.

The right words

One key to a good stored-word speech-synthesis system is to choose the right words to store, convert them from an analog source, and then compress them into digital data suitable for the SPC.

National Semiconductor will convert analog tapes into custom digital data for customers, but that's an expensive proposition for hobbyists. However, the company has developed four general-purpose 64K-bit ROM's that contain data for 273 words, phrases, tones, and pauses. National's Linear databooks list several different ROM sets, but the SSR1, SSR2, SSR5, and SSR6 provide the best selection of words and are easy to obtain. The four ROM's together contain nearly two minutes of continuous speech; the words contained in each ROM set are shown in Tables 1 and 2.

Hooking it up

As shown in Fig. 1, the simplest way to use the Digitalker is to connect it to your computer's printer port. There are several advantages to doing so. First, handshaking between the computer and the Digitalker is automatic, so it isn't necessary to place timing loops in the software.

Second, most printer ports have a STROBE line that goes low when data at the port is valid. The strobe line can be connected to the SPC's \overline{WR} line. When it is asserted, the SPC reads the ROM data for the selected word over its eight data lines (D0–D8), and then delivers the word to the audio output (pin 39).

The SPC's INTR line (pin 6) goes high after the entire word has been pronounced. By connecting the INTR line (or, if necessary, the inverted \overline{INTR}) to the printer port's BUSY input,

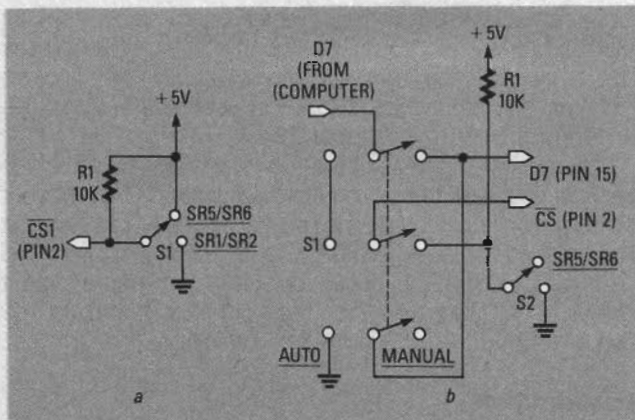


FIG. 3—ROM-SELECT CIRCUITS: Use the circuit shown in (a) to select between ROM sets manually. The circuit shown in (b) allows manual or automatic computer control, but only the first 128 words and phrases are accessible in the auto mode.

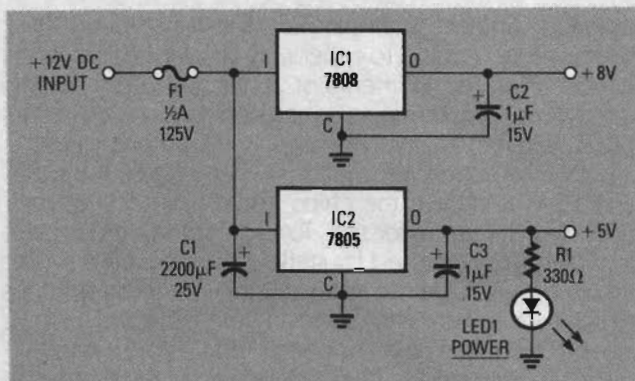


FIG. 4—POWER SUPPLY for the Digitalker. A +12-volt wall transformer provides the raw DC input.

the host computer will wait until each word has been spoken before sending more data to the SPC.

Two SPC pins provide options. First, \overline{CS} is the chip-select line; it must be grounded momentarily when the computer addresses the SPC. \overline{CS} is provided to allow the SPC to share the data bus with other devices.

Second, \overline{CMS} (command select) resets the interrupt and starts a speech sequence when it is low, and only resets the interrupt when it is high.

The PC board layout brings both \overline{CS} and \overline{CMS} out to the edge connector. For normal operation from a parallel-printer port, it's most convenient to ground both pins at the edge-card connector.

Now let's look at the circuit, shown in Fig. 2. The SPC's speech output drives IC8, which buffers the audio signal and drives a volume control. Final audio output is provided by IC9.

Flip-flop IC6 and 3-to-8 line decoder IC7 select the speech ROM's, depending on whether SPC address line AD13 is high or low, and on the state of the \overline{CS} signal (edge connector pin 2). AD13 picks the high or low ROM of a pair, and \overline{CS} picks one pair or the other.

There are several ways to select which ROM pair you want to use. If you have an extra output bit available on your PC (perhaps a bit from a second parallel port), you can program \overline{CS} directly. Otherwise, you can use a manual switch, as shown in Fig. 3-a.

A combination approach is shown in Fig. 3-b. With switch S1 in the Manual position, you can use S2 to switch

between ROM's. But with S1 in the Auto position, you can switch between ROM's using a single eight-bit port. The upper data bit (D7) provides the switching function, so only the first 128 words (0-127) in each ROM set will be accessible using that approach.

The power-supply schematic is shown in Fig. 4. An inexpensive wall transformer provides the raw DC power. Voltage regulators inside the project's cabinet provide the required voltages: +5-volts DC for the digital circuits, and +8-volts DC for the audio circuitry. The entire circuit draws about 300 mA when the volume is turned up, so use a +12-volt DC, 500-mA power supply.

Construction

PC board patterns are shown in PC Service. An etched and drilled PC board is also available from the source given in the Parts List. Figure 5 shows how the parts are mounted on the board. **Note:** six jumper wires must be soldered to the circuit board before the IC sockets are installed. An additional jumper must be soldered from the center INT terminal to either INT or $\overline{\text{INT}}$, depending on the handshaking requirements of your computer's parallel port. Most computers use an active-high busy signal, so try the INT setting first if you're not sure which one to use.

Observe normal precautions when handling the SPC and ROM IC's. Leave the chips in their protective "rugs" until they are ready for use. To protect the components against damage caused by static electricity, make sure to ground yourself before removing the IC's from their rugs, or when handling or moving the PC board.

After mounting all components, check your work carefully for solder bridges and cold joints. Fix any problems before applying power to the board.

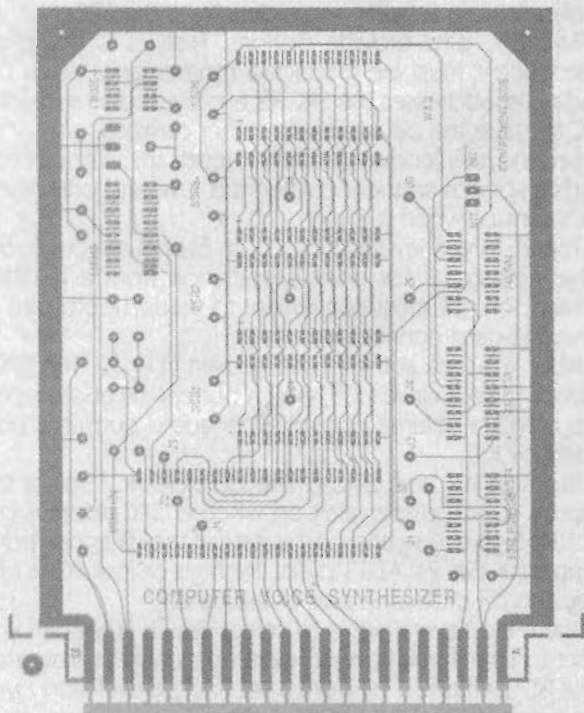


FIG. 5—PARTS LAYOUT: Note that six jumpers must be installed on the component side of the board before installing the IC sockets. (Sockets mount over five of the six jumpers.)

DIGITAL TALKER PARTS LIST

All resistors are 1/4-watt, 5% unless otherwise noted.

- R1—1500 ohms
- R2—1 megohm
- R3—50,000 ohms, potentiometer
- R4—620,000 ohms
- R5—9100 ohms
- R6, R8—10,000 ohms
- R7—10 ohms

All capacitors are rated 15 volts or higher

- C1—C5, C10—C13, C16—0.1 μF , ceramic disc
- C6—50 pF, ceramic disc
- C7—20 pF, ceramic disc
- C8, C9—0.01 μF , ceramic disc
- C14—0.05 μF , ceramic disc
- C15—220 μF , 15 volts, electrolytic

Semiconductors

- IC1—MM54104, speech processor
- IC2—MM52164-SSR1, speech ROM
- IC3—MM52164-SSR2, speech ROM
- IC4—MM52164-SSR5, speech ROM
- IC5—MM52164-SSR6, speech ROM
- IC6—7474, dual D flip-flop
- IC7—74138, 3-to-8 line decoder
- IC8—LM346, programmable op-amp
- IC9—LM386, audio power amplifier
- IC10—7404, hex inverter

Other components

- XTAL1—4.00 MHz crystal

POWER SUPPLY PARTS LIST

- R1—330 ohms
- IC1—7808 8-volt regulator
- IC2—7805 5-volt regulator
- C1—2200 μF , 25 volts, electrolytic
- C2, C3—1 μF , 15 volts, tantalum
- F1—fuse, 0.5 amp, 125 volts
- LED1—light-emitting diode

Note: An etched and drilled PC board is available for \$15.95 from David A. Ward, 2261 W. Skyview, Cedar City, UT 84720-2233. All orders add \$2.00 shipping and handling; Utah residents add 6% sales tax.

LISTING 1

```

10 REM This program will make the
20 REM Digitalker pronounce all words
30 REM in SSR1 and SSR2 (CS1 is low)
40 FOR X = 0 TO 143
50 LPRINT CHR$(X);
60 NEXT X
70 END

```

LISTING 2

```

10 REM This program will make the
20 REM Digitalker pronounce all words
30 REM in SSR5 and SSR6 (CS1 is high)
40 FOR X=0 TO 130
50 LPRINT CHR$(X);
60 NEXT X
70 END

```

LISTING 3

```

10 REM REAL TIME CLOCK PROGRAM
20 CLS
30 PRINT"HOW OFTEN DO YOU WANT THE TIME ANNOUNCED?"
40 PRINT:PRINT
50 PRINT"ENTER 1 FOR 1 MINUTE INTERVALS..."
60 PRINT"ENTER 5 FOR 5 MINUTE INTERVALS..."
70 PRINT"ENTER 30 FOR 30 MINUTE INTERVALS..."
80 INPUT", I
90 TIMES=TIMES
100 TS=LEFTS(TIMES,2)
110 T1$=MIDS(TIMES,4,2)
120 HS=LEFTS(TS,1)
130 H1$=RIGHTS(TS,1)
140 H=ASC(HS)
150 H1=ASC(H1$)
160 H=H-48
170 H1=H1-48
180 H=H*10
190 HT=H+H1
200 IF HT>12 THEN HT=HT-12:P=47:GOTO 220
210 P=32
220 IF HT=12 THEN P=47
230 IF HT=0 THEN HT=12:P=32
240 MS=LEFTS(T1$,1)
250 M1$=RIGHTS(T1$,1)
260 M=ASC(MS)
270 M1=ASC(M1$)
280 M=M-48
290 M1=M1-48
300 IF M=0 AND M1=0 THEN M=68:M1=68
310 IF M=0 AND M1>0 THEN M=46
320 IF M=1 AND M1=0 THEN M=10:M1=68
330 IF M=1 AND M1=1 THEN M=11:M1=68
340 IF M=1 AND M1=2 THEN M=12:M1=68
350 IF M=1 AND M1=3 THEN M=13:M1=68
360 IF M=1 AND M1=4 THEN M=14:M1=68
370 IF M=1 AND M1=5 THEN M=15:M1=68
380 IF M=1 AND M1=6 THEN M=16:M1=68
390 IF M=1 AND M1=7 THEN M=17:M1=68
400 IF M=1 AND M1=8 THEN M=18:M1=68
410 IF M=1 AND M1=9 THEN M=19:M1=68
420 IF M=2 THEN M=20
430 IF M=3 THEN M=21
440 IF M=4 THEN M=22
450 IF M=5 THEN M=23
460 IF M1=0 THEN M1=68
470LPRINT CHR$(0);CHR$(138);CHR$(67);CHR$(139);CHR$(67);
CHR$(96);CHR$(71);CHR$(HT);CHR$(69);CHR$(M);CHR$(M1);
CHR$(71);CHR$(P);CHR$(44);CHR$(71);CHR$(71);
480 PRINT TIMES
490 GOSUB 510
500 GOTO 90
510 IF I=1 THEN I=60
520 IF I=5 THEN I=300
530 IF I=10 THEN I=600
540 IF I=30 THEN I=1800
550 Z=TIMER
560 Y=TIMER
570 IF Y-Z<I THEN 560
580 RETURN

```

Making the connection

Connecting the Digtalker to your computer is as simple as plugging it into your computer's parallel printer port. For testing purposes, wire a ROM-select switch as shown in Fig. 3-a.

It's easy to program the Digtalker. For example, simply by typing

```
LPRINT CHR$(0);
```

the Digtalker will say the phrase "This is Digtalker" if \overline{CS} is low, or "abort" if \overline{CS} is high.

Listing 1 and Listing 2 are test programs that sequentially pronounce all words contained in the selected ROM set. Both programs were written in GW-BASIC; they were tested on a Kaypro PC.

More sophisticated applications are not difficult. For example, the author has written BASIC programs that do the following; announce the time from the computer's

real-time clock, pronounce the corresponding letter of the alphabet as a key is typed (great for a small child learning his ABC's), pronounce phone numbers as names are typed in, and prompt the user for input in various programs. The talking clock program is shown in Listing 3.

There are a couple of things to be aware of when programming the Digtalker. First, addressing a word with a number higher than that listed in the word lists will produce unintelligible speech, but will not damage the




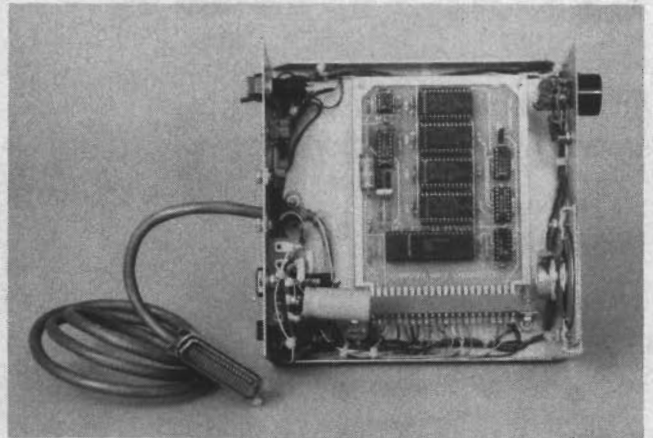
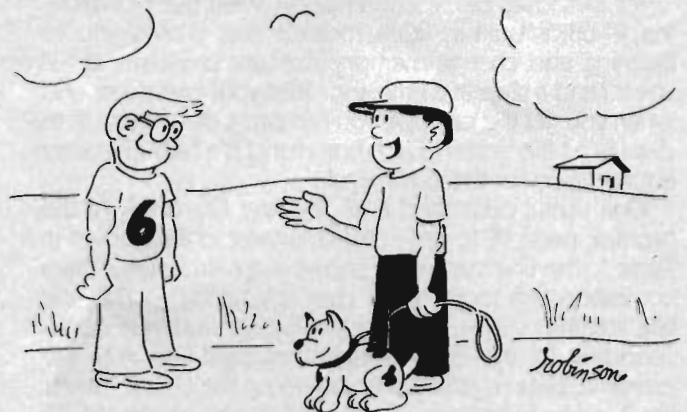
FIG. 6—THE ASSEMBLED SYNTHESIZER with its cover removed.

SPC or ROM chips. Second, the semicolons following the LPRINT statements are essential. If they are not present the Digtalker will pronounce *thirteen* and then *ten* after each word is spoken. That occurs because an ASCII 13 is a carriage return, and an ASCII 10 is a linefeed. The semicolon (;) eliminates the carriage return and linefeed.


Applications ideas

Computer voice synthesis can be a very natural way for computers to communicate with people. For example, a synthesizer could be used to warn a pilot that the plane's altitude is critically low, or that the fuel level is low. A visually impaired person could compose documents with a word processor, or compute math problems with a calculator.


Undoubtedly, there are many other uses for computerized voice synthesis in cash registers, automatic teller machines, emergency warning systems, automobiles, telephone systems, etc. Have fun finding them! 



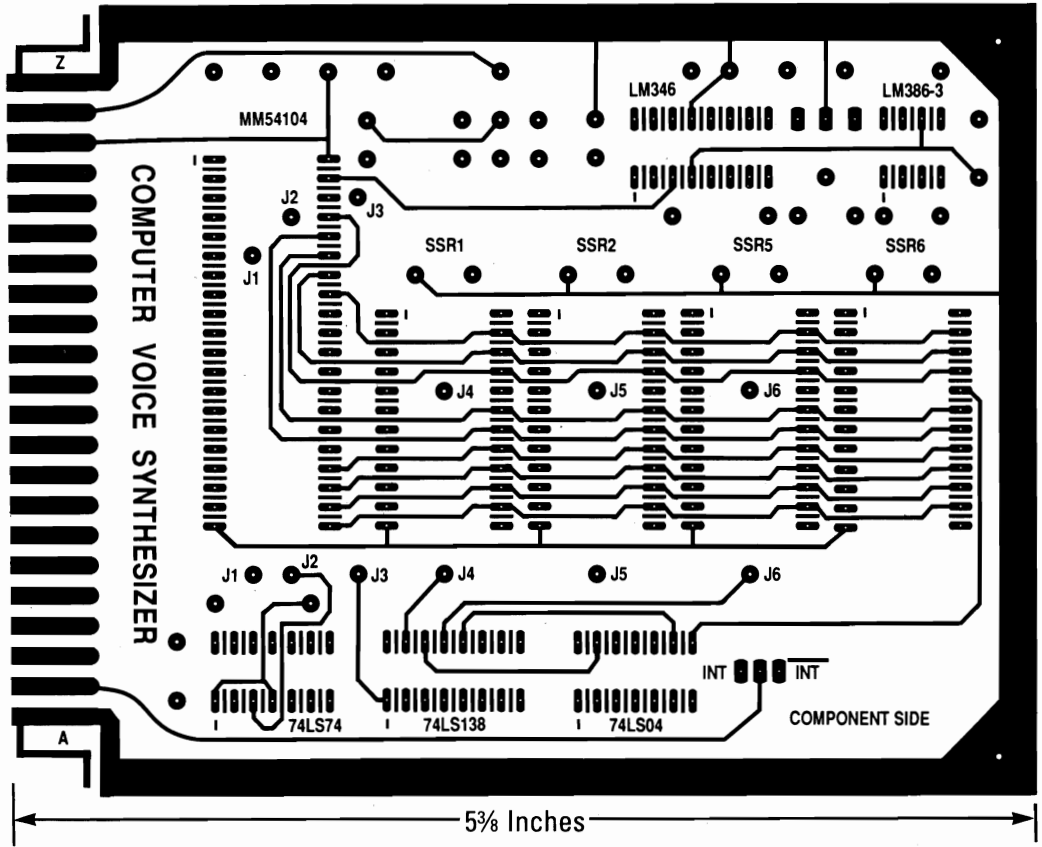"The man at the pet shop said he can store up to 20 separate commands."



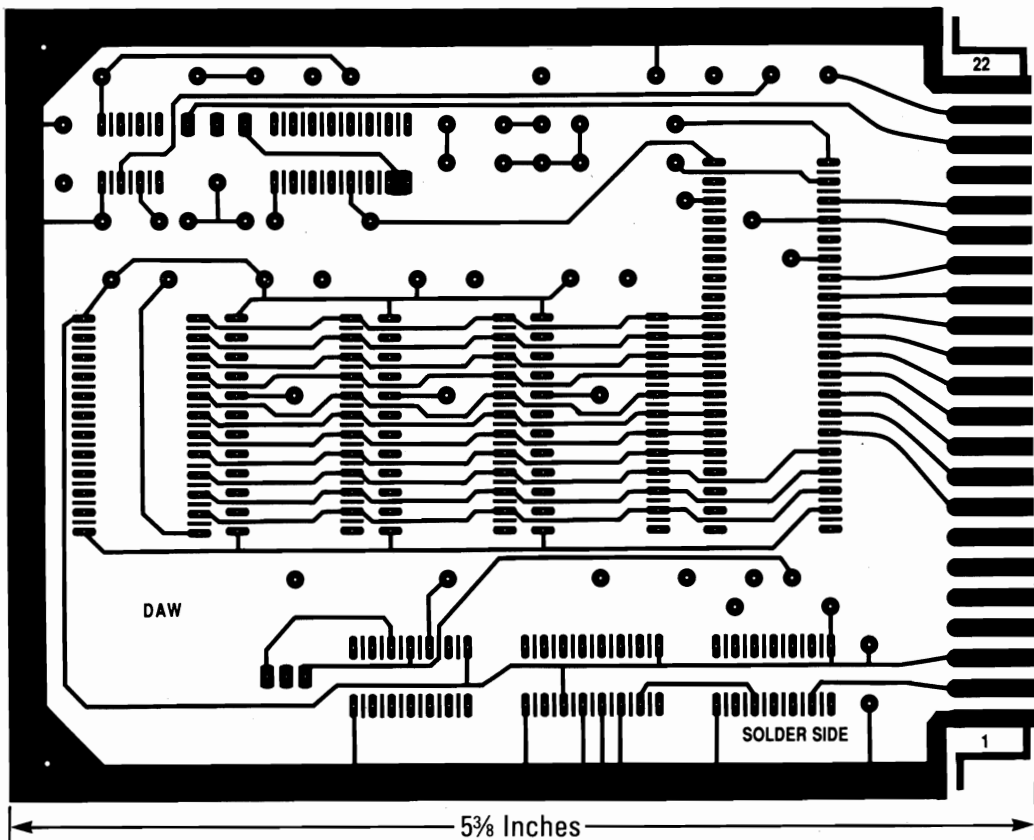THE COMPONENT SIDE of the voice-synthesizer board.



THE SOLDER SIDE of the voice-synthesizer board.